



**Maratha Vidya Prasarak Samaj's**

**Rajarshi Shahu Maharaj Polytechnic, Nashik**

**Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.**

**Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.**

---

*Subject: - Electrical Circuits (22324)*



# SYLLABUS

<b>Chapter No.</b>	<b>Name of chapter</b>	<b>Marks With Option</b>
<b>1</b>	<b>Single phase AC series circuit</b>	<b>22</b>
<b>2</b>	<b>Single phase AC parallel circuit</b>	<b>20</b>
<b>3</b>	<b>Three phase Circuits</b>	<b>20</b>
<b>4</b>	<b>Network reduction and principles of DC circuits analysis</b>	<b>16</b>
<b>5</b>	<b>Network Theorems</b>	<b>24</b>
<b>Total Marks :-</b>		<b>102</b>

# BOARD THEORY

# PAPER PATTERN

Q.1	Attempt any FIVE	5*2=10	
	Single phase AC series circuit		CO-324.01
	b) Single phase AC series circuit		CO-324.01
	c) Single phase AC parallel circuit		CO-324.02
	d) Three phase Circuits		CO-324.03
	e) Network reduction and principles of DC circuits analysis		CO-324.04
	f) Network Theorems		CO-324.05
	g) Network Theorems		CO-324.05
Q.2	Attempt any THREE 3*4=12		
	Single phase AC series circuit		CO-324.01
	b) Single phase AC parallel circuit		CO-324.02
	c) Three phase Circuits		CO-324.03
	d) Network reduction and principles of DC circuits analysis		CO-324.04
Q.3	Attempt any THREE 3*4=12		
	Single phase AC series circuit		CO-324.01
	b) Single phase AC parallel circuit		CO-324.02
	c) Three phase Circuits		CO-324.03
	d) Network reduction and principles of DC circuits analysis		CO-324.04
	e) Network Theorems		CO-324.05
Q.4	Attempt any THREE 3*4=12		
	Single phase AC series circuit		CO-324.01
	b) Single phase AC parallel circuit		CO-324.02
	c) Three phase Circuits		CO-324.03
	d) Network Theorems		CO-324.05
Q.5	Attempt any TWO 2*6=12		
	Single phase AC parallel circuit		CO-324.02





**Maratha Vidya Prasarak Samaj's**  
**Rajarshi Shahu Maharaj Polytechnic, Nashik**




**Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.**  
**Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.**

	b)	<b>Network reduction and principles of DC circuits analysis</b>	<b>CO-324.04</b>
	c)	<b>Network Theorems</b>	<b>CO-324.05</b>
<b>Q.6</b>		<b>Attempt any TWO 2*6=12</b>	
		<b>Single phase AC series circuit</b>	<b>CO-324.01</b>
	b)	<b>Three phase Circuits</b>	<b>CO-324.03</b>
	c)	<b>Network Theorems</b>	<b>CO-324.05</b>

# SAMPLE QUESTION PAPER
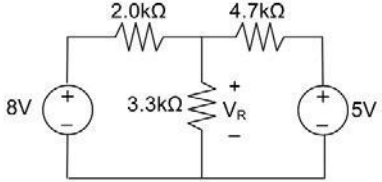
<b>Q.1</b>	<b>Attempt any FIVE</b>	<b>5*2=10</b>	
a)	Draw impedance triangle for R-C series circuit. Write nature of power factor of this circuit.		<b>CO-324.01</b>
b)	Define impedance and reactance related to single phase AC series circuit. Give the units of both.		<b>CO-324.01</b>
c)	Define admittance with unit.		<b>CO-324.02</b>
d)	Draw the sinusoidal waveform of 3-phase emf and also indicate the phase sequence.		<b>CO-324.03</b>
e)	Give four steps to solve mesh analysis.		<b>CO-324.04</b>
f)	State Superposition Theorem.		<b>CO-324.05</b>
g)	State the maximum power transfer theorem for DC circuit.		<b>CO-324.05</b>
<b>Q.2</b>	<b>Attempt any THREE 3*4=12</b>		
a)	Find active, reactive and apparent power and power factor of the A.C. Series circuit consisting of R=1 ohm, L=0.001 Henry and C= 1 microfarad supplied with 100 volt, 50 Hz power supply.		<b>CO-324.01</b>
b)	A voltage of $200 \angle 53^\circ$ is applied across two impedances in parallel. The values of impedances are $(12 + j16)$ and $(10 - j20)$ . Determine the kVA, kVAR and kW in each branch and power factor of the whole circuit.		<b>CO-324.02</b>
c)	A delta connected induction motor is supplied by 3-phase, 400V, 50Hz supply the line current is 43.3A and the total power taken from the supply is 24 kW. Find the resistance and reactance per phase of motor winding		<b>CO-324.03</b>
d)	Using mesh analysis find values of $V_R$ as shown in Figure No. 1		<b>CO-324.04</b>
	Fig. 1.		
<b>Q.3</b>	<b>Attempt any THREE 3*4=12</b>		
a)	A coil of resistance $50 \Omega$ and inductance of 0.1 H is connected in series with 100 mF capacitor. The combination is supplied with 230 V, 50 Hz		<b>CO-324.01</b>

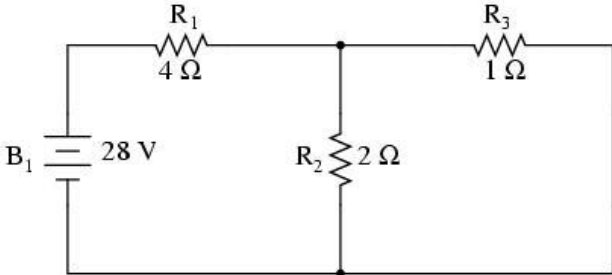		A.C. supply. Calculate voltage across each, current through the circuit, power factor and draw complete vector diagram.	
	b)	Two impedances $(12 + j16)$ and $(10-j20) \Omega$ are connected in parallel across a supply of $200\angle 60^\circ$ using admittance method calculate branch currents, total current and power factor of whole circuit.	<b>CO-324.02</b>
	c)	Give four advantages of polyphase circuits over 1-phase circuits.	<b>CO-324.03</b>
	d)	Give the expression for star to delta and delta to star transformation.	<b>CO-324.04</b>
	e)	Using Norton's theorem, find current through $1\Omega$ resistances in Figure No. 2.  <p style="text-align: center;">Fig.2</p>	<b>CO-324.05</b>
<b>Q.4</b>		<b>Attempt any THREE 3*4=12</b>	
	a)	An inductive coil $(10 + j40) \Omega$ impedance is connected in series with a capacitor of $100 \mu\text{F}$ across $230 \text{ V}$ , $50 \text{ Hz}$ , 1-Phase supply mains find : (1) Current through the circuit (2) P.F. of the circuit (3) Power dissipated in the circuit (4) Draw phasor diagram	<b>CO-324.01</b>
	b)	A coil having resistance of $5 \Omega$ and inductance of $0.2\text{H}$ is arranged in parallel with another coil having resistance of $1 \Omega$ and inductance of $0.08 \text{ H}$ . Calculate the current through the combination and power absorbed when a voltages of $100 \text{ V}$ , $50 \text{ Hz}$ is applied. Use impedance method.	<b>CO-324.02</b>
	c)	Each phase of a delta-connected load comprises a resistor of $50 \Omega$ and capacitor of $50 \mu\text{F}$ in series. Calculate the line and phase currents when the load is connected to a $440 \text{ V}$ , 3 phase $50 \text{ Hz}$ supply.	<b>CO-324.03</b>
	d)	Define duality of electric circuits and write duality of electrical elements.	<b>CO-324.05</b>
<b>Q.5</b>		<b>Attempt any TWO 2*6=12</b>	
	a)	A $100 \Omega$ resistor, $0.02 \text{ H}$ inductor and $1.2 \mu\text{F}$ capacitor are connected in parallel with a circuit made up of resistor of $110 \Omega$ and a capacitor of $2.4 \mu\text{F}$ . a supply of $230\text{V}$ , $50 \text{ Hz}$ is connected across the circuit. Calculate the current taken from the supply & phase angle of it.	<b>CO-324.02</b>

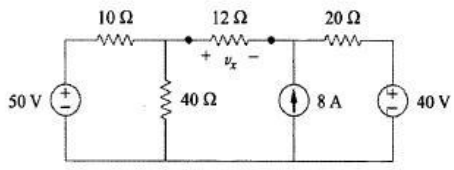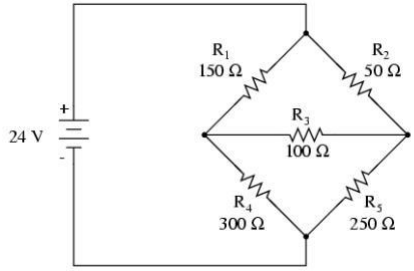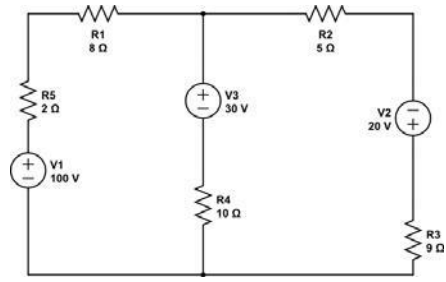b)	<p>Using source transformation, find the voltage across <math>12\ \Omega</math> (<math>v_x</math>), as shown in figure Fig.3</p> 	CO-324.04
c)	<p>Apply Thevenin's theorem to calculate current flowing through <math>R_5 = 250\ \Omega</math> resistor as shown in figure.4</p>  <p style="text-align: center;">Fig.4</p>	CO-324.05
Q.6	<p><b>Attempt any TWO <math>2*6=12</math></b></p>	
a)	<p>An a.c. series circuit has a resistance of <math>10\ \Omega</math>, an inductance of <math>0.2\ \text{H}</math> and a capacitance of <math>60\ \mu\text{F}</math>. Calculate: ( resonant frequency (current (power at resonance. Applied voltage is <math>200\ \text{V}</math>.</p>	CO-324.01
b)	<p>State relationship between line voltage and phase voltage, line current &amp; phase current in a balanced star connection. Draw complete phasor diagram of voltages &amp; current.</p>	CO-324.03
c)	<p>Apply Superposition theorem to calculate current flowing through <math>R_4 = 10\ \Omega</math> resistor as shown in figure.5</p>  <p style="text-align: center;">Fig.5</p>	CO-324.05



# CLASS TEST - I PAPER PATTERN

## Syllabus:-

Unit No.	Name of the Unit	Course Outcome (CO)
1	Single phase AC series circuit	CO-324.01
2	Single phase AC parallel circuit	CO-324.02

Q.1	Attempt any FOUR 4*2=8Marks	Course Outcome (CO)
	Single phase AC series circuit	CO-324.01
b)	Single phase AC series circuit	CO-324.01
c)	Single phase AC series circuit	CO-324.01
d)	Single phase AC parallel circuit	CO-324.02
e)	Single phase AC parallel circuit	CO-324.02
f)	Single phase AC parallel circuit	CO-324.02
Q.2	Attempt any THREE 3*4=12 Marks	
	Single phase AC series circuit	CO-324.01
b)	Single phase AC series circuit	CO-324.01
c)	Single phase AC series circuit	CO-324.01
d)	Single phase AC parallel circuit	CO-324.02
e)	Single phase AC parallel circuit	CO-324.02





## SAMPLE CLASS TEST - I PAPER

Q.1	Attempt any FOUR 4*2=8Marks	Course Outcome (CO)
	Draw voltage triangles for R-L and R-C single phase AC series circuits.	CO-324.01
b)	Define quality factor of series A.C. circuit.	CO-324.01
c)	Convert $Z = 6 + j8 \Omega$ in polar form.	CO-324.01
d)	Define admittance and conductance in relation with parallel circuits. Give formulas for the same.	CO-324.02
e)	Write properties of Parallel resonance.	CO-324.02
f)	Define Quality Factor for parallel resonance. Give equation of it.	CO-324.02
Q.2	Attempt any THREE 3*4=12 Marks	
	A resistance $60 \Omega$ and inductance of $0.5 \text{ H}$ is connected in series. The combination is supplied with $230 \text{ V}$ , $50 \text{ Hz}$ A.C. supply. Calculate voltage across each, current through the circuit, power factor and draw complete vector diagram.	CO-324.01
b)	A RC series circuit consisting of $R = 10 \Omega$ and $C = 100 \text{ mF}$ is connected across $200\text{V}$ , $50\text{Hz}$ AC supply. Find the value of current and power factor. What will be the value of current and power factor if the value of resistance is doubled?	CO-324.01
c)	Derive an expression for resonant frequency of a series RLC circuit.	CO-324.01
d)	Impedances $Z1 = (10 + j5) \Omega$ and $Z2 = (8 + j6) \Omega$ are connected in parallel across $V = (200 + j0)$ . Using the admittance method, calculate circuit current and the branch currents.	CO-324.02
e)	A coil having resistance of $5 \Omega$ and inductance of $0.2\text{H}$ is arranged in parallel with capacitor of $5\text{d}.0 \mu\text{F}$ . Calculate the current through the combination and power absorbed when a voltages of $100 \text{ V}$ , $50 \text{ Hz}$ is applied. Use impedance metho	CO-324.02



## CLASS TEST - II PAPER PATTERN


### Syllabus:-

Unit No.	Name of the Unit	Course Outcome (CO)
1	Three phase Circuits	CO-324.03
2	Network reduction and principles of DC circuits analysis	CO-324.04
3	Network Theorems	CO-324.05

Q.1	Attempt any FOUR 4*2=8Marks	Course Outcome (CO)
	Three phase Circuits	CO-324.03
b)	Three phase Circuits	CO-324.03
c)	Network reduction and principles of DC circuits analysis	CO-324.04
d)	Network reduction and principles of DC circuits analysis	CO-324.04
e)	Network Theorems	CO-324.05
f)	Network Theorems	CO-324.05
Q.2	Attempt any THREE 3*4=12 Marks	
	Three phase Circuits	CO-324.03
b)	Three phase Circuits	CO-324.03
c)	Network reduction and principles of DC circuits analysis	CO-324.04
d)	Network Theorems	CO-324.05
e)	Network Theorems	CO-324.05

## SAMPLE CLASS TEST - II PAPER

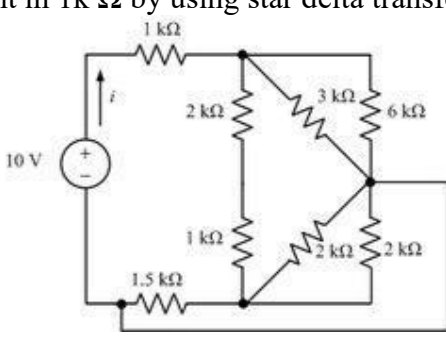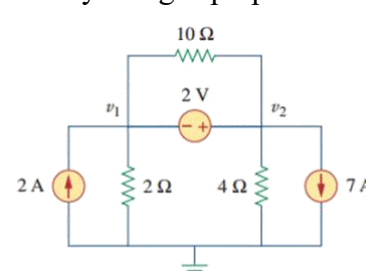		Course Outcome (CO)
<b>Q.1</b>	<b>Attempt any FOUR 4*2=8Marks</b>	
a)	Define line voltage and phase voltage	CO-324.03
b)	What do you mean by balanced load and balanced supply in relation with polyphase AC circuits?	CO-324.03
c)	Give four steps to solve nodal analysis.	CO-324.04
d)	How current source can be converted into equivalent voltage source?	CO-324.04
e)	State Reciprocity Theorem.	CO-324.05
f)	State Norton's theorem.	CO-324.05
<b>Q.2</b>	<b>Attempt any THREE 3*4=12 Marks</b>	
	Three coils each with a resistance of $10\ \Omega$ and inductance of $0.35\text{mH}$ are connected in star to a 3-phase, $440\ \text{V}$ , $50\ \text{Hz}$ supply. Calculate the line current and total power taken per phase.	CO-324.03
b)	Derive relation between line and phase voltages of star connection of 3ph load.	CO-324.03
c)	Find current in $1\text{k}\ \Omega$ by using star delta transformation. 	CO-324.04
d)	Find the current in $10\ \Omega$ by using superposition theorem. 	CO-324.05

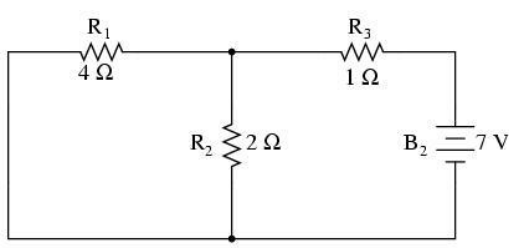e)	<p>Find maximum power in <math>R_1 = 4 \Omega</math> by using maximum power transfer theorem</p>  <p>The circuit diagram shows a 4 Ω resistor (R<sub>1</sub>) in series with a 2 Ω resistor (R<sub>2</sub>) in parallel. A 1 Ω resistor (R<sub>3</sub>) is in series with a 7 V DC source (B<sub>2</sub>) in parallel with R<sub>2</sub>.</p>	CO-324.05
----	---	-----------



**Maratha Vidya Prasarak Samaj's**

**Rajarshi Shahu Maharaj Polytechnic, Nashik**

**Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.**

**Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.**

# **COURSE OUTCOME (CO)**

**COURSE: - ELECTRICAL CIRCUITS (22324)**

**PROGRAMME: - ELECTRICAL ENGINEERING.**

<b>CO.NO</b>	<b>Course Outcome</b>
<b>CO-324.01</b>	Troubleshoot problems related to single phase A.C. series circuits.
<b>CO-324.02</b>	Troubleshoot problems related to single phase A.C. parallel circuits.
<b>CO-324.03</b>	Troubleshoot problems related to three phase circuits
<b>CO-324.04</b>	Use principles of circuit analysis to troubleshoot problems related to electric circuits
<b>CO-324.05</b>	Apply network theorems to troubleshoot problems related to electric circuits



# **SINGLE PHASE AC SERIES CIRCUITS**

Position in Question Paper

Total Marks-22

Q.1. a) 2-Marks.

b) 2-Marks.

Q.2. a) 4-Marks.

Q.3. a) 4-Marks.

Q.4. a) 4-Marks.

Q.6. a) 6-Marks.

## **Descriptive Question**

1. Define - frequency. State its relation with time period.
2. . If maximum value of a sine wave is 25A. Calculate its average value.
3. . Draw a power triangle and state the relation between its sides.
4. State the range of phase angle and hence pf for a series RC circuit.
5. In a series RL circuit  $V_R = 100V$  and  $V_L = 150V$ . Find equivalent voltage across the circuit.
6. An alternating current is given by  $i = 20 \sin (314t)$ . Find –Current at  $t = 0.0025$  sec at first instant. Time required to reach at 12A for first time.
7. A series circuit has a leading pf. Express it with circuit, waveform and phasor diagram.
8. In RLC series circuit  $R = 8W$ ,  $L = 0.42 H$  with an unknown capacitor. If the circuit is connected across 230V, 50 Hz, 1 $\phi$  AC. Calculate value of capacitor so that circuit resonates at supply frequency. Also calculate current and pf at this instant.
9. Define peak factor and form factor. State value of each for a pure sine wave.
10. A series RLC circuit consists of  $R = 20W$ ,  $L = 1H$  and  $C = 2500 \mu f$ . If it is connected across 230V, 1 $\phi$  AC. Calculate Q factor and resonant frequency.
11. Derive the condition for resonance in an RLC series circuit. Also derive the equation for Q factor.
12. State nature of pf for any two conditions in RLC series circuit. Draw phasor diagram for each.





## MCQ Question

(Total number of Question=Marks\*3=22\*3=66)

Note: Correct answer is marked with **bold**.

- Instantaneous voltage is the product of resistance and \_\_\_\_\_ current in a resistive circuit.
  - Instantaneous**
  - Average
  - RMS
  - Peak
- Find the value of the instantaneous voltage if the resistance is 2 ohm and the instantaneous current in the circuit is 5A.
  - 5V
  - 2V
  - 10V**
  - 2.5V
- The power for a purely resistive circuit is zero when?
  - Current is zero
  - Voltage is zero
  - Both current and voltage are zero
  - Either current or voltage is zero**
- The correct expression for the instantaneous current if instantaneous voltage is  $V_m(\sin t)$  in a resistive circuit is?
  - 1A
  - 2A**
  - 3A
  - 4A
- Calculate the resistance in the circuit if the rms voltage is 20V and the rms current is 2A.
  - 2 ohm
  - 5 ohm
  - 10 ohm**
  - 20 ohm
- The correct expression for the instantaneous current in a resistive circuit is?
  - $i = V_m(\sin t)/R$**
  - $i = V_m(\cos t)/R$
  - $i = V(\sin t)/R$
  - $i = V(\cos t)/R$
- Can ohm's law be applied in an ac circuit?
  - Yes**
  - No
  - Depends on the rms current
  - Depends on the rms voltage
- The correct expression for the instantaneous current if instantaneous voltage is  $V_m(\sin t)$  in an inductive circuit is?
  - $i = V_m(\sin t)/X_L$
  - $i = V_m(\cos t)/X_L$
  - $i = -V_m(\sin t)/X_L$
  - $i = -V_m(\cos t)/X_L$**
- Inductor does not allow sudden changes in?
  - Voltage
  - Current**
  - Resistance
  - Inductance
- Inductance is \_\_\_\_\_ to number of turns in the coil
  - directly proportional**
  - inversely proportional
  - equal
  - not related
- Choke involve use of \_\_\_\_\_
  - Resistor
  - Capacitor





- c) **Inductor** d) Transistor
12. What is the value of current in an inductive circuit when there is no applied voltage?  
a) Minimum c) Zero  
b) **Maximum** d) Cannot be determined
13. What is the current in an inductive circuit when the applied voltage is maximum?  
a) Infinity c) **Zero**  
b) Maximum d) Cannot be determined
14. In an inductive circuit, the voltage\_\_\_\_\_ the current?  
a) **Leads** c) Is greater than  
b) Lags d) Is less than
15. In an inductive circuit, the current\_\_\_\_\_ the voltage?  
a) Leads c) Is greater than  
b) **Lags** d) Is less than
16. In which device inductor cannot be used?  
a) filter circuit c) choke  
b) transformer d) **dielectric**
17. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V 50Hz sinusoidal supply. Calculate the current in the circuit.  
a) 2.2A c) 6.2A  
b) 4.2A d) **8.2A**
18. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V 50Hz sinusoidal supply. Calculate the phase difference.  
a) **-55.1** c) 6  
b) 55.1 d) -66.1
19. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V 50Hz sinusoidal supply. Calculate the voltage across the resistor.  
a) 31.8V c) 67.3V  
b) **57.4V** d) 78.2V
20. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V 50Hz sinusoidal supply. Calculate the voltage across the inductor.  
a) 52V c) 65V  
b) **82V** d) 76V
21. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a x V 50Hz sinusoidal supply. The current in the circuit is 8.2A. Calculate the value of x.  
a) 10V c) **100V**  
b) 50V d) 120
22. Which, among the following, is the correct expression for  $\phi$ .  
a)  $\phi = \tan^{-1} (XL/R)$  c)  $\phi = \tan^{-1} (XL * R)$   
b)  $\phi = \tan^{-1} (R/XL)$  d)  $\phi = \cos^{-1} (XL/R)$



23. For an RL circuit, the phase angle is always \_\_\_\_\_
- a) Positive  
b) **Negative**  
c) 0  
d) 90
24. What is  $\phi$  in terms of voltage?
- a)  $\phi = \cos^{-1} V/VR$   
b)  $\phi = \cos^{-1} V*VR$   
c)  $\phi = \cos^{-1} VR/V$   
d)  $\phi = \tan^{-1} V/VR$
25. What is  $\sin\phi$  from impedance triangle?
- a)  $X_L/R$   
b)  **$X_L/Z$**   
c)  $R/Z$   
d)  $Z/R$
26. What is the resonance frequency of ac circuit?
- a)  $1/\sqrt{LC}$   
b)  $\sqrt{L/C}$   
c)  $\sqrt{LC}$   
d)  $LC$
27. What is impedance at resonance?
- a) maximum  
b) **minimum**  
c) zero  
d) cannot be determined
28. What is the value of impedance at resonance?
- a)  $X_L$   
b)  $X_C$   
c) **R**  
d) 0
29. What is  $\phi$  in terms of voltage?
- a)  $\phi = \cos^{-1} V/V_R$   
b)  $\phi = \cos^{-1} V*V_R$   
c)  $\phi = \cos^{-1} V_R/V$   
d)  $\phi = \tan^{-1} V/V_R$
30. What is  $\tan\phi$  for RC circuit?
- a)  **$X_C/R$**   
b)  $X_L/R$   
c)  $R/Z$   
d)  $Z/R$
31. What is the resonance condition?
- a) When  $X_L > X_C$   
b) When  $X_L < X_C$   
c) **When  $X_L = X_C$**   
d) When  $X_C = \text{infinity}$
32. What is the frequency in resonance condition?
- a) Minimum  
b) **Maximum**  
c) Cannot be determined  
d) Zero
33. Can capacitor fully charge using alternating current?
- a) **Yes**  
b) No  
c) may or may not  
d) depend on value of capacitance
34. What is the resistance offered by a capacitor?
- a) Susceptance  
b) Conductance  
c) Admittance  
d) **Reactance**
35. The combination of resistance and reactance known as \_\_\_\_\_
- a) Susceptance  
b) **Impedance**



- c) Conductance  
d) Admittance
36. What is the relation between reactance, resistance and impedance?  
a)  $Z=R+Jx$   
b)  $Z=R+X$   
c)  $Z=R-X$   
d)  $Z=R-jX$
37. What is the real part of the impedance of RLC circuit?  
a) **Resistance**  
b) Conductance  
c) Admittance  
d) Reactance
38. What is imaginary part of the impedance of RLC circuit?  
a) Resistance  
b) Conductance  
c) Admittance  
d) **Reactance**
39. Which type of current can be stored in a capacitor?  
a) Alternating current  
b) Both alternating current and direct current  
c) **Direct current**  
d) Neither alternating current nor direct current
40. If in an alternating current circuit, resistance is 5 ohm, capacitive reactance is 12 ohm, what is the impedance?  
a) 5 ohm  
b) 10 ohm  
c) 12 ohm  
d) **13 ohm**
41. If in an alternating current circuit, impedance is 26 ohm, capacitive reactance is 24 ohm, what is the resistance?  
a) 25 ohm  
b) **10 ohm**  
c) 12 ohm  
d) 23 ohm
42. If in an alternating current circuit, capacitance of 30  $\mu\text{F}$  is connected to a supply of 200V, 50Hz. Find the current in the circuit.  
a) **1.38 A**  
b) 1.89 A  
c) 1.74 A  
d) 0.89 A
43. If in an alternating current circuit, capacitance C is connected to a supply of 200V, 50Hz. Current in the circuit is 1.89 A. Find the capacitance C.  
a) **30  $\mu\text{F}$**   
b) 20  $\mu\text{F}$   
c) 10  $\mu\text{F}$   
d) 15  $\mu\text{F}$
44. In ac circuit, resistance 5 ohm is connected with capacitor having capacitive reactance 12 ohm. Supply of 260 V is connected to the circuit. Calculate the current in the circuit.  
a) 40 A  
b) 10 A  
c) **20 A**  
d) 30 A
45. In ac circuit, resistance 5 ohm is connected with capacitor having capacitive reactance 12 ohm. Supply of 260 V is connected to the circuit. Calculate the voltage across resistance.  
a) 300 V  
b) 200 V



- c) 240 V  
d) **100 V**
46. In ac circuit, resistance 5 ohm is connected with a capacitor having capacitive reactance 12 ohm. Supply of 260 V is connected to the circuit. Calculate the voltage across a capacitor.
- a) 300 V  
b) 200 V  
c) **240 V**  
d) 100 V
47. Find the total voltage applied in a series RLC circuit when  $i=3\text{mA}$ ,  $V_L=30\text{V}$ ,  $V_C=18\text{V}$  and  $R=1000\text{ ohms}$ .
- a) 3.95V  
b) **51V**  
c) 32.67V  
d) 6.67V
48. In an RLC circuit, which of the following is always used as a vector reference?
- a) **Voltage**  
b) Resistance  
c) Impedance  
d) Current
49. In an RLC circuit, the power factor is always \_\_\_\_\_
- a) Positive  
b) Negative  
c) **Depends on the circuit**  
d) Zero
50. What is the correct expression for the phase angle in an RLC series circuit?
- a)  $\phi = \tan^{-1}(X_L - X_C)/R$   
b)  $\phi = \tan^{-1}(X_L + X_C)/R$   
c)  $\phi = \tan(X_L - X_C)/R$   
d)  $\phi = \tan^{-1}(X_L - X)$
51. When is  $\tan\phi$  positive?)
- a) When inductive reactance is less than capacitive reactance  
b) **When inductive reactance is greater than capacitive reactance**  
c) When inductive reactance is equal to capacitive reactance  
d) When inductive reactance is zero
52. When is  $\tan\phi$  negative?
- a) **When inductive reactance is less than capacitive reactance**  
b) When inductive reactance is greater than capacitive reactance  
c) When inductive reactance is equal to capacitive reactance  
d) When inductive reactance is zero
53. Which of the following is not ac waveform?
- a) Sinusoidal  
b) **Constant**  
c) Square  
d) triangular
54. What is not a frequency for ac current?
- a) 50 Hz  
b) 55 Hz  
c) **0Hz**  
d) 60 Hz
55. Which type of ac waveform is given in figure?
- a) **Sinusoidal**  
b) Triangular  
c) Square  
d) complex waveform



56. The correct expression for the instantaneous current if instantaneous voltage is  $V_m(\sin t)$  in an inductive circuit is?
- a)  $i = V_m(\sin t)/X_L$   
b)  $i = V_m(\cos t)/X_L$   
c)  $i = -V_m(\sin t)/X_L$   
d)  **$i = -V_m(\cos t)/X_L$**
57. Inductor does not allow sudden changes in?
- a) Voltage  
b) **Current**  
c) Resistance  
d) Inductance
58. Inductance is \_\_\_\_\_ to number of turns in the coil
- a) **directly proportional**  
b) inversely proportional  
c) equal  
d) not related
59. Choke involve use of \_\_\_\_\_
- a) Resistor  
b) Capacitor  
c) **Inductor**  
d) Transistor
60. What is the value of current in an inductive circuit when there is no applied voltage?
- a) Minimum  
b) **Maximum**  
c) Zero  
d) Cannot be determined
61. What is the current in an inductive circuit when the applied voltage is maximum?
- a) Infinity  
b) Maximum  
c) **Zero**  
d) Cannot be determined
62. In an inductive circuit, the voltage \_\_\_\_\_ the current?
- a) Lags  
b) Is greater than  
c) **lead**  
d) Is less than
63. In an RLC circuit, the power factor is always \_\_\_\_\_
- a) Positive  
b) Negative  
c) **Depends on the circuit**  
d) Zero
64. What is the correct expression for the phase angle in an RLC series circuit?
- a)  $\phi = \tan^{-1} (X_L + X_C)/R$   
b)  $\phi = \tan(X_L - X_C)/R$   
c)  $\phi = \tan^{-1} (X_L - X)$   
d)  **$\phi = \tan^{-1}(X_L - X_C)/R$**
65. When is  $\tan \phi$  positive?
- a) **When inductive reactance is greater than capacitive reactance**  
b) When inductive reactance is equal to capacitive reactance  
c) When inductive reactance is zero  
d) When inductive reactance is less than capacitive reactance
66. What is the resonance frequency of ac circuit?
- a)  $1/\sqrt{LC}$   
b)  $\sqrt{L/C}$   
c)  $\sqrt{LC}$   
d)  $LC$



# SINGLE PHASE AC PARALLEL CIRCUITS

Position in Question Paper

Total Marks-20

Q.1. c) 2-Marks.

Q.2. b) 4-Marks.


Q.3. b) 4-Marks.

Q.4. b) 4-Marks.

Q.5. a) 6-Marks.
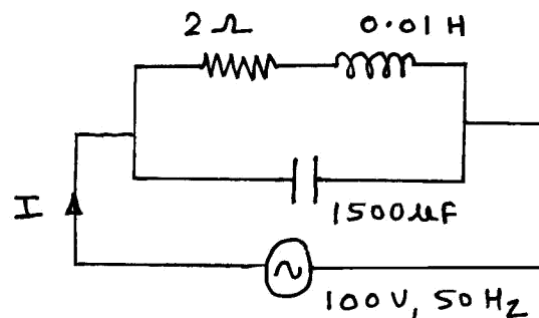
## Descriptive Question

- Two admittances  $Y_1 = 0.012 \angle 60^\circ$  and  $Y_2 = 0.015 \angle 45^\circ$  are connected in parallel across 250V, 50Hz AC. Calculate power consumed by the circuit.
- Draw an experimental set up to find current and power for parallel circuit of  $R = 50\Omega$  and  $L = 0.2H$ ,  $V = 230V$ , 50Hz, 1 $\phi$  AC.
- Write equation of resonant frequency and quality factor in terms of circuit components for a parallel circuit.
- Find current  $I$  in the circuit shown in Figure No. 1 using admittance method.




5. Fig. No. 1

- Two impedances  $(5 + j6) \Omega$  and  $(7 - j8) \Omega$  are connected in parallel across 230 V, 1 $\phi$ , 50 Hz a.c. supply. Determine current drawn by each path and total current in the circuit.
- A voltage of  $200 \angle 0^\circ$  is applied across two impedances in parallel. The values of impedance are  $(12 + j16) \Omega$  and  $(10 - j20) \Omega$ . Determine the kVA, kVAR and kW in each branch and power factor of the whole circuit.
- If  $A = 10 + j8$ ,  $B = -7 + j5$ ,  $C = 8 + j6$  Find: I.  $AB/C$  II.  $(A+B)/(B-C)$
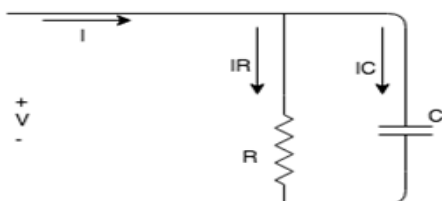
## MCQ Question

(Total number of Question=Marks\*3=20\*3=60)


- In a parallel circuit, we consider \_\_\_\_\_ instead of impedance.
  - Resistance
  - Capacitance
  - Inductance
  - Admittance**
- In a parallel circuit, we consider admittance instead of \_\_\_\_\_.
  - Resistance
  - Capacitance
  - Inductance
  - Impedance**
- Which, among the following is the correct expression for impedance?
  - $Z=Y$
  - $Z=1/Y$**
  - $Z=Y^2$
  - $Z=1/Y^2$
- Which, among the following is the correct expression for admittance?
  - $Y=Z$
  - $Y=1/Z$**
  - $Y=Z^2$
  - $Y=1/Z^2$
- What is the unit of admittance?
  - Ohm
  - Henry
  - Farad
  - $\text{ohm}^{-1}$**
- As the impedance increases, the admittance \_\_\_\_\_.
  - Increases
  - Decreases**
  - Remains the same
  - Becomes zero
- If the impedance of a system is 4 ohm, calculate its admittance.
  - $0.25 \text{ ohm}^{-1}$**
  - $4 \text{ ohm}^{-1}$
  - $25 \text{ ohm}^{-1}$
  - $0.4 \text{ ohm}^{-1}$
- In an impedance parallel network, the reactive component will either lead or lag the voltage by \_\_\_\_\_ degrees.
  - 0
  - 90**
  - 45
  - 180
- In A parallel circuit, with any number of impedances, the voltage across each impedance is?
  - Equal**
  - divided equally
  - divided proportionally
  - zero
- In a parallel circuit, current in each impedance is \_\_\_\_\_.
  - Equal
  - Different**
  - Zero
  - infinite
- From the given circuit, find the value of  $I_R$ .



- 0
- $V/I$**
- $V/R$**
- Cannot be determined




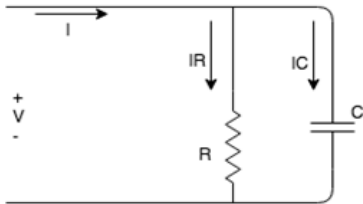12. What is the relation between  $I_R$  and  $V$  in the following circuit?




- a)  $I_R$  leads  $V$
- b)  $I_R$  lags  $V$
- c)  $I_R$  and  $V$  are in phase
- d) No relation

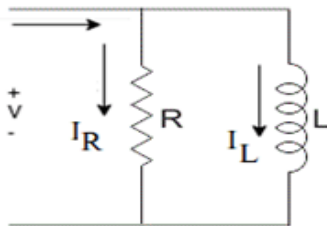13. What is the expression for the current in the inductor from the following circuit?




- a)  $V/I$
- b)  $V/X_L$
- c) 0
- d) Cannot be determined

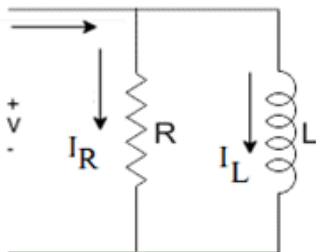14. What is the phase relation between  $I_L$  and  $V$  from the following circuit?




- a)  $I_L$  lags  $V$
- b)  $I_L$  leads  $V$
- c)  $I_L$  and  $V$  are in phase
- d) No relation

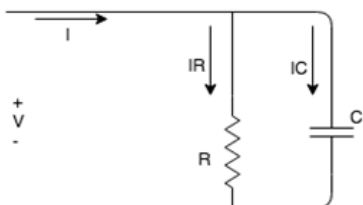15. Find the expression for the current  $I$  from the given circuit.




- a)  $I=I_C$
- b)  $I=I_R$
- c)  $I=I_C+I_R$
- d)  $I=0$

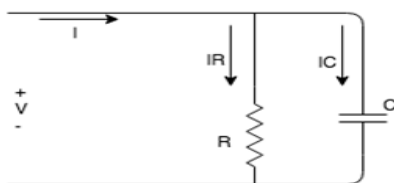16. Find the total current if  $I_C=2A$  and  $I_R=5A$ .




- a) 3A
- b) -3A
- c) 7A
- d) 10A

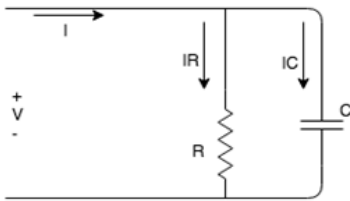17. Find the value of  $I_R$  if  $I=10A$  and  $I_C=8A$ .




- a) 5A  
 b) 18A  
 c) 12A  
 d) 2A

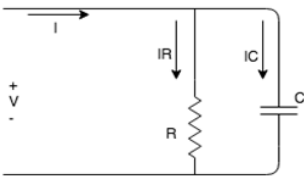18. Find the value of  $I_L$  if  $I_C=10A$  and  $I_R=6A$ .




- a) 4A  
 b) 18A  
 c) 12A  
 d) 2A

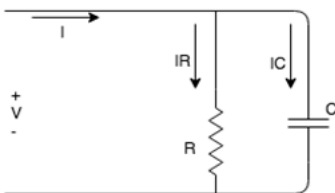19. What is the expression for the current in the capacitor from the following circuit?



- a)  $V/C$   
 b)  $V/I$   
 c) 0  
 d)  $V/X_C$

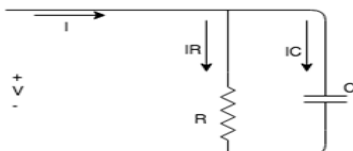20. What is the phase relation between  $I_C$  and  $V$  from the following circuit?



- a)  $I_C$  lags  $V$   
 b)  $I_C$  leads  $V$   
 c)  $I_C$  and  $V$  are in phase  
 d) No relation

21. In an impedance parallel network, the reactive component wills \_\_\_\_\_ the voltage by 90 degrees.

- a) Lead  
 b) Lag  
 c) **Either lead or lag**  
 d) Depends on the circuit

22. In an impedance parallel network, the reactive component will either lead or lag the voltage by \_\_\_\_\_ degrees.

- a) 0  
 b) 90  
 c) 45  
 d) 180

23. In an impedance parallel network, the reactive component will either lead or lag the \_\_\_\_\_ by 90 degrees.

- a) **Voltage**  
 b) Current  
 c) Either voltage or current  
 d) Cannot be determined





32. In a series RLC circuit, the phase difference between the current in the inductor and the current in the resistor is?
- a)  $0^{\circ}$  c)  $180^{\circ}$   
b)  $90^{\circ}$  d)  $360^{\circ}$
33. In a series RLC circuit, the phase difference between the current in the capacitor and the current in the inductor is?
- a)  $0^{\circ}$  c)  $180^{\circ}$   
b)  $90^{\circ}$  d)  $360^{\circ}$
34. In a series RLC circuit, the phase difference between the current in the circuit and the voltage across the resistor is?
- a)  $0^{\circ}$  c)  $180^{\circ}$   
b)  $90^{\circ}$  d)  $360^{\circ}$
35. In a series RLC circuit, the phase difference between the current in the circuit and the voltage across the capacitor is?
- a)  $0^{\circ}$  c)  $180^{\circ}$   
b)  $90^{\circ}$  d)  $360^{\circ}$
36. \_\_\_\_\_ the resonant frequency, the current in the inductor lags the voltage in a series RLC circuit.
- a) **Above** c) Equal to  
b) Below d) Depends on the circuit
37. \_\_\_\_\_ the resonant frequency, the current in the capacitor leads the voltage in a series RLC circuit.
- a) Above c) Equal to  
b) **Below** d) Depends on the circuit
38. What is imaginary part of the impedance of RLC circuit?
- a) Resistance c) Admittance  
b) Conductance d) **Reactance**
39. Which type of current can be stored in a capacitor?
- a) Alternating current  
b) Both alternating current and direct current  
c) **Direct current**  
d) Neither alternating current nor direct current
40. If in an alternating current circuit, resistance is 5 ohm, capacitive reactance is 12 ohm, what is the impedance?
- a) 5 ohm c) 12 ohm  
b) 10 ohm d) **13 ohm**
41. If in an alternating current circuit, impedance is 26 ohm, capacitive reactance is 24 ohm, what is the resistance?
- a) 25 ohm c) 12 ohm  
b) **10 ohm** d) 23 ohm





- d) When inductive reactance is zero
52. When is  $\tan\phi$  negative?
- When inductive reactance is less than capacitive reactance
  - When inductive reactance is greater than capacitive reactance
  - When inductive reactance is equal to capacitive reactance
  - When inductive reactance is zero
53. Which of the following is not ac waveform?
- Sinusoidal
  - Constant**
  - Square
  - triangular
54. What is not a frequency for ac current?
- 50 Hz
  - 55 Hz
  - 0Hz**
  - 60 Hz
55. Which type of ac waveform is given in figure?
- Sinusoidal**
  - Triangular
  - Square
  - complex waveform
56. The correct expression for the instantaneous current if instantaneous voltage is  $V_m(\sin t)$  in an inductive circuit is?
- $i = V_m(\sin t)/X_L$
  - $i = V_m(\cos t)/X_L$
  - $i = -V_m(\sin t)/X_L$
  - $i = -V_m(\cos t)/X_L$**
57. Inductor does not allow sudden changes in?
- Voltage
  - Current**
  - Resistance
  - Inductance
58. Inductance is \_\_\_\_\_ to number of turns in the coil
- directly proportional**
  - inversely proportional
  - equal
  - not related
59. Choke involve use of \_\_\_\_\_
- Resistor
  - Capacitor
  - Inductor**
  - Transistor
60. What is the value of current in an inductive circuit when there is no applied voltage?
- Minimum
  - Maximum**
  - Zero
  - Cannot be determined





# THREE PHASE CIRCUITS

Position in Question Paper

Total Marks-20

Q.1. d) 2-Marks.

Q.2. c) 4-Marks.

Q.3. c) 4-Marks.

Q.4. c) 4-Marks.

Q.6. b) 6-Marks.

## Descriptive Question

1. Draw phasor diagram for  $3\phi$  generated voltages.
2. List any two advantages of  $3\phi$  circuits over single phase circuits.
3. List any four observations from the phasor diagram of a  $3\phi$  delta connection.
4. Three impedances each of  $Z = 15 + j18\Omega$  are connected in star across a  $400V, 3\phi$ , AC. Calculate  $-V_{ph}, I_{ph}, I_L, Pf$
5. Draw the sinusoidal waveform of  $3\phi$  emf and also indicate the phase sequence.
6. State relationship between line voltage and phase voltage, line current and phase current in a balanced delta connection. Draw complete phasor diagram of voltages and current.
7. State any four advantages of poly phase circuit over single phase circuit.



## MCQ Question

(Total number of Question=Marks\*3=24\*3=72)

Note: Correct answer is marked with **bold**.

- In a balanced three-phase system-delta load, if we assume the line voltage is  $V_{RY} = V\angle 0^\circ$  as a reference phasor. Then the source voltage  $V_{YB}$  is?
  - $V\angle 0^\circ$
  - $V\angle -120^\circ$**
  - $V\angle 120^\circ$
  - $V\angle 240^\circ$
- In a balanced three-phase system-delta load, if we assume the line voltage is  $V_{RY} = V\angle 0^\circ$  as a reference phasor. Then the source voltage  $V_{BR}$  is?
  - $V\angle 120^\circ$
  - $V\angle 240^\circ$
  - $V\angle -240^\circ$**
  - $V\angle -120^\circ$
- In a delta-connected load, the relation between line voltage and the phase voltage is?
  - line voltage > phase voltage
  - line voltage < phase voltage
  - line voltage = phase voltage**
  - line voltage  $\geq$  phase voltage
- If the load impedance is  $Z\angle \theta$ , the current ( $I_R$ ) is?
  - $(V/Z)\angle -\theta$**
  - $(V/Z)\angle \theta$
  - $(V/Z)\angle 90-\theta$
  - $(V/Z)\angle -90+\theta$
- If the load impedance is  $Z\angle \theta$ , the expression obtained for current ( $I_Y$ ) is?
  - $(V/Z)\angle -120+\theta$
  - $(V/Z)\angle 120-\theta$
  - $(V/Z)\angle 120+\theta$
  - $(V/Z)\angle -120-\theta$**
- If the load impedance is  $Z\angle \theta$ , the expression obtained for current ( $I_S$ ) is?
  - $(V/Z)\angle -240+\theta$
  - $(V/Z)\angle -240-\theta$**
  - $(V/Z)\angle 240-\theta$
  - $(V/Z)\angle 240+\theta$
- A three-phase balanced delta connected load of  $(4+j8)\ \Omega$  is connected across a 400V, 3 –  $\emptyset$  balanced supply. Determine the phase current  $I_R$ . Assume the phase sequence to be  $R_{YB}$ .
  - $44.74\angle -63.4^\circ\text{A}$**
  - $44.74\angle 63.4^\circ\text{A}$
  - $45.74\angle -63.4^\circ\text{A}$
  - $45.74\angle 63.4^\circ\text{A}$
- A three-phase balanced delta connected load of  $(4+j8)\ \Omega$  is connected across a 400V, 3 –  $\emptyset$  balanced supply. Determine the phase current  $I_Y$ .
  - $44.74\angle 183.4^\circ\text{A}$
  - $45.74\angle 183.4^\circ\text{A}$
  - $44.74\angle 183.4^\circ\text{A}$**
  - $45.74\angle -183.4^\circ\text{A}$
- A three-phase balanced delta connected load of  $(4+j8)\ \Omega$  is connected across a 400V, 3 –  $\emptyset$  balanced supply. Determine the phase current  $I_B$ .
  - $44.74\angle 303.4^\circ\text{A}$
  - $44.74\angle -303.4^\circ\text{A}$**
  - $45.74\angle 303.4^\circ\text{A}$
  - $45.74\angle -303.4^\circ\text{A}$
- Determine the power (kW) drawn by the load.
  - 21
  - 22
  - 23
  - 24**
- The power generated by a machine increases \_\_\_\_\_ percent from single phase to two phase.
  - 40.4
  - 41.4**



- c) 42.4  
d) 43.4
12. The percentage of power increased from single phase to three phase is?  
a) **50**  
b) 100  
c) 150  
d) 200
13. When the power factor is \_\_\_\_\_ the power becomes zero 100 times a second in a 50Hz supply.  
a) 0  
b) **1**  
c) 2  
d) 3
14. Which motors are called self-starting motors?  
a) single phase  
b) two phase  
c) **three phase**  
d) four phase
15. In three phase system, the three voltages (currents) differ in phase by \_\_\_\_\_ electrical degrees from each other in a particular sequence.  
a) 30  
b) 60  
c) 90  
d) **120**
16. In a two phase generator, the armature has two distinct windings that are displaced \_\_\_\_\_ apart.  
a)  $45^\circ$   
b)  **$90^\circ$**   
c)  $135^\circ$   
d)  $180^\circ$
17. In three phase system at any given instant, the algebraic sum of three voltages must be?  
a) **0**  
b) 1  
c) 2  
d) 3
18. Phase sequence depends on the \_\_\_\_\_  
a) Field  
b) **rotation of the field**  
c) armature  
d) rotation of the armature
19. If  $RR'$ ,  $YY'$  and  $BB'$  constitutes three phase sequence if  $V_{RR'} = V_m \sin \omega t$  its corresponding field magnets are in clockwise direction, then  $V_{YY'} = ?$   
a)  $V_m \sin \omega t$   
b)  $V_m \sin(\omega t + 120^\circ)$   
c)  **$V_m \sin(\omega t - 120^\circ)$**   
d)  $V_m \sin(\omega t - 240^\circ)$
20. If  $RR'$ ,  $YY'$  and  $BB'$  constitutes three phase sequence if  $V_{RR'} = V_m \sin \omega t$  its corresponding field magnets are in clockwise direction, then the value of  $V_{BB'}$  is?  
a)  **$V_m \sin(\omega t - 240^\circ)$**   
b)  $V_m \sin(\omega t - 120^\circ)$   
c)  $V_m \sin(\omega t + 240^\circ)$   
d)  $V_m \sin \omega t$
21. In a three phase alternator, there are \_\_\_\_\_ independent phase windings or coils.  
a) 1  
b) 2  
c) **3**  
d) 4
22. Each coil in three phase alternator has \_\_\_\_\_ number of terminals.  
a) **2**  
b) 4  
c) 6  
d) 8



23. In wye or star connection \_\_\_\_\_ of the three phases are joined together within the alternator.
- a) **similar ends** c) one similar end, two opposite ends  
b) opposite ends d) one opposite end, two opposite ends
24. The voltage between \_\_\_\_\_ and \_\_\_\_\_ is called phase voltage.
- a) line and line c) neutral point and reference  
b) line and reference **d) line and neutral point**
25. The voltage between \_\_\_\_\_ is called line voltage.
- a) line and neutral point c) **line and line**  
b) line and reference d) neutral point and reference
26. In the Delta or Mesh connection, there will be \_\_\_\_\_ number of common terminals.
- a) 1 c) 3  
b) 2 d) **0**
27. The relation between line voltage and phase voltage in Delta or Mesh connection is?
- a)  $V_{\text{phase}} > V_{\text{line}}$  c)  **$V_{\text{phase}} = V_{\text{line}}$**   
b)  $V_{\text{phase}} < V_{\text{line}}$  d)  $V_{\text{phase}} \geq V_{\text{line}}$
28. Which of the following voltage is a phase voltage in the delta connection?
- a)  $V_{RN}$  c)  $V_{YN}$   
b)  **$V_{BR}$**  d)  $V_{BN}$
29. A balanced delta-connected load of  $(2+j3) \Omega$  per phase is connected to a balanced three-phase 440V supply. The phase current is 10A. Find the total active power.
- a) 7.26W c) **7260W**  
b) 726W d) 72.6W
30. A balanced delta-connected load of  $(2+j3) \Omega$  per phase is connected to a balanced three-phase 440V supply. The phase current is 10A. Find the apparent power.
- a) **10955.67 VAR** c) 109.5567 VAR  
b) 10.95567 VAR d) 1.095567 VAR
31. In star connected system,  $V_{RY}$  is equal to?
- a)  $V_{YR}$  c)  $2V_{YR}$   
b)  **$-V_{YR}$**  d)  $3V_{YR}$
32. In three phase system, the line voltage  $V_{RY}$  is equal to?
- a) **phasor sum of  $V_{RN}$  and  $V_{NY}$**  c) phasor sum of  $V_{RN}$  and  $V_{NY}$   
b) phasor difference of  $V_{RN}$  and  $V_{NY}$  d) algebraic sum of  $V_{RN}$  and  $V_{NY}$
33. The relation between the lengths of the phasors  $V_{RN}$  and  $-V_{YN}$  is?
- a)  $|V_{RN}| > -|V_{YN}|$  c)  **$|V_{RN}| = -|V_{YN}|$**   
b)  $|V_{RN}| < -|V_{YN}|$  d)  $|V_{RN}| \geq -|V_{YN}|$
34. In a star connected system, the phasors  $V_{RN}$ ,  $V_{YN}$  are \_\_\_\_\_ apart.
- a)  $15^\circ$  c)  $45^\circ$   
b)  $30^\circ$  d)  **$60^\circ$**
35. The relation between  $V_{RY}$ ,  $V_{ph}$  in a star connected system is?
- a)  $V_{RY} = V_{ph}$  c)  $V_{RY} = 3\sqrt{3}V_{ph}$   
b)  **$V_{RY} = \sqrt{3}V_{ph}$**  d)  $V_{RY} = 3V_{ph}$



**Maratha Vidya Prasarak Samaj's**  
**Rajarshi Shahu Maharaj Polytechnic, Nashik**

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

36. In a star connected system, the relation between  $V_{YB}$ ,  $V_{ph}$  is?  
a)  $V_{YB} = V_{ph}$   
b)  $V_{YB} = 3\sqrt{3}V_{ph}$   
c)  $V_{YB} = 3V_{ph}$   
d)  $V_{YB} = \sqrt{3}V_{ph}$
37. The voltages,  $V_{BR}$ ,  $V_{ph}$  are related in star connected system is?  
a)  $V_{BR} = 3V_{ph}$   
b)  $V_{BR} = 3\sqrt{3}V_{ph}$   
c)  $V_{BR} = \sqrt{3}V_{ph}$   
d)  $V_{BR} = V_{ph}$
38. In a delta connected system, the voltage across the terminals R and Y is  $400\angle 0^\circ$ . Calculate the line voltage  $V_{RY}$ . Assume  $R_{RY}$  phase sequence.  
a)  $400\angle 0^\circ$   
b)  $400\angle 120^\circ$   
c)  $400\angle -120^\circ$   
d)  $400\angle 240^\circ$
39. In a delta connected system, the voltage across the terminals R and Y is  $400\angle 0^\circ$ . Find the line voltage  $V_{YB}$ .  
a)  $400\angle 120^\circ$   
b)  $400\angle -120^\circ$   
c)  $400\angle 240^\circ$   
d)  $400\angle -240^\circ$
40. In a delta connected system, the voltage across the terminals R and Y is  $400\angle 0^\circ$ . Find the line voltage  $V_{BR}$ .  
a)  $400\angle 240^\circ$   
b)  $400\angle 120^\circ$   
c)  $400\angle -240^\circ$   
d)  $400\angle -120^\circ$
41. In delta-connected system, the currents  $I_R$ ,  $I_Y$ ,  $I_B$  are equal in magnitude and they are displaced by \_\_\_\_\_ from one another.  
a)  $0^\circ$   
b)  $60^\circ$   
c)  $90^\circ$   
d)  $120^\circ$
42. In a delta-connected system, the currents  $I_R = I_B = I_Y = ?$   
a)  $I_{Ph}$   
b)  $2I_{Ph}$   
c)  $3I_{Ph}$   
d)  $4I_{Ph}$
43. The relation between  $I_L$  and  $I_{Ph}$  is in a delta connected system is?  
a)  $I_L = I_{Ph}$   
b)  $I_L = \sqrt{3} I_{Ph}$   
c)  $I_L = 3 I_{Ph}$   
d)  $I_L = 3\sqrt{3}I_{Ph}$
44. The line currents are \_\_\_\_\_ behind respective phase currents in a delta connected system.  
a)  $120^\circ$   
b)  $90^\circ$   
c)  $60^\circ$   
d)  $30^\circ$
45. In a delta connected system, the expression of power (P) is?  
a)  $V_L I_L \cos\phi$  W  
b)  $\sqrt{3} V_L I_L \cos\phi$  W  
c)  $3V_L I_L \cos\phi$  W  
d)  $3\sqrt{3} V_L I_L \cos\phi$  W
46. In a balanced three-phase system-delta load, if we assume the line voltage is  $V_{RY} = V\angle 0^\circ$  as a reference phasor. Then the source voltage  $V_{YB}$  is?  
a)  $V\angle 0^\circ$   
b)  $V\angle -120^\circ$   
c)  $V\angle 120^\circ$   
d)  $V\angle 240^\circ$
47. In a balanced three-phase system-delta load, if we assume the line voltage is  $V_{RY} = V\angle 0^\circ$  as a reference phasor. Then the source voltage  $V_{BR}$  is?  
a)  $V\angle 120^\circ$   
b)  $V\angle 240^\circ$





- c)  $V\angle-240^\circ$  d)  $V\angle-120^\circ$
48. In a delta-connected load, the relation between line voltage and the phase voltage is?  
a) line voltage > phase voltage c) **line voltage = phase voltage**  
b) line voltage < phase voltage d) line voltage >= phase voltage
49. If the load impedance is  $Z\angle\theta$ , the current ( $I_R$ ) is?  
a)  $(V/Z)\angle-\theta$  c)  $(V/Z)\angle90-\theta$   
b)  $(V/Z)\angle\theta$  d)  $(V/Z)\angle-90+\theta$
50. If the load impedance is  $Z\angle\theta$ , the expression obtained for current ( $I_Y$ ) is?  
a)  $(V/Z)\angle-120+\theta$  c)  $(V/Z)\angle120+\theta$   
b)  $(V/Z)\angle120-\theta$  d)  **$(V/Z)\angle-120-\theta$**
51. If the load impedance is  $Z\angle\theta$ , the expression obtained for current ( $I_s$ ) is?  
a)  $(V/Z)\angle-240+\theta$  c)  $(V/Z)\angle240-\theta$   
b)  **$(V/Z)\angle-240-\theta$**  d)  $(V/Z)\angle240+\theta$
52. A three-phase balanced delta connected load of  $(4+j8)\ \Omega$  is connected across a 400V, 3 –  $\emptyset$  balanced supply. Determine the phase current  $I_R$ . Assume the phase sequence to be  $R_{YB}$ .  
a)  **$44.74\angle-63.4^\circ\text{A}$**  c)  $45.74\angle-63.4^\circ\text{A}$   
b)  $44.74\angle63.4^\circ\text{A}$  d)  $45.74\angle63.4^\circ\text{A}$
53. A three-phase balanced delta connected load of  $(4+j8)\ \Omega$  is connected across a 400V, 3 –  $\emptyset$  balanced supply. Determine the phase current  $I_Y$ .  
a)  $44.74\angle183.4^\circ\text{A}$  c)  **$44.74\angle183.4^\circ\text{A}$**   
b)  $45.74\angle183.4^\circ\text{A}$  d)  $45.74\angle-183.4^\circ\text{A}$
54. A three-phase balanced delta connected load of  $(4+j8)\ \Omega$  is connected across a 400V, 3 –  $\emptyset$  balanced supply. Determine the phase current  $I_B$ .  
a)  $44.74\angle303.4^\circ\text{A}$  c)  $45.74\angle303.4^\circ\text{A}$   
b)  **$44.74\angle-303.4^\circ\text{A}$**  d)  $45.74\angle-303.4^\circ\text{A}$
55. Determine the power (kW) drawn by the load.  
a) 21 c) 23  
b) 22 d) **24**
56. The wattmeter method is used to measure power in a three-phase load. The wattmeter readings are 400W and -35W. Calculate the total active power.  
a) 360 c) 370  
b) **365** d) 375
57. The wattmeter method is used to measure power in a three-phase load. The wattmeter readings are 400W and -35W. Find the power factor.  
a) **0.43** c) 0.63  
b) 0.53 d) 0.73
58. The wattmeter method is used to measure power in a three-phase load. The wattmeter readings are 400W and -35W. Find the reactive power.  
a) 751.44 c) **753.44**  
b) 752.44 d) 754.44
59. The input power to a three-phase load is 10kW at 0.8 Pf. Two watt meters are connected to measure the power. Find the reading of higher reading wattmeter.



**Maratha Vidya Prasarak Samaj's**

**Rajarshi Shahu Maharaj Polytechnic, Nashik**

**Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.**

**RSM POLY**

**Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.**

---

a) **7.165**

b) 6.165

c) 6.165

d) 4.165

60. The input power to a three-phase load is 10kW at 0.8 Pf. Two watt meters are connected to measure the power. Find the reading of lower reading wattmeter.

a) 1.835

b) **2.835**

c) 3.835

d) 4.835

# NETWORK REDUCTION AND PRINCIPLES OF CIRCUIT ANALYSIS


Position in Question Paper

Total Marks-16


- Q.1. e) 2-Marks.
- Q.2. d) 4-Marks.
- Q.3. d) 4-Marks.
- Q.5. b) 6-Marks.
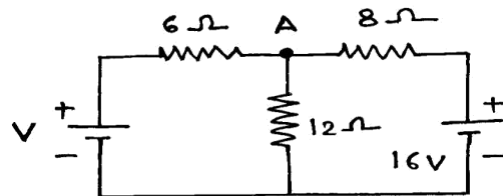
## Descriptive Question


- Three resistor each of  $23\Omega$  are connected in delta across a  $230\text{V}$ ,  $3\phi$ ,  $50\text{Hz}$  AC. Calculate the power consumed by the load.
- State only the formula for star to delta transformation.
- Find the value of  $V$  of Figure if the voltage at node A is  $12\text{V}$ .



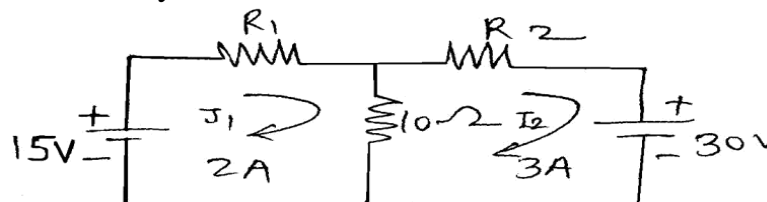- Derive the formulae for star to delta, and star to delta transformation.
- Using mesh analysis finds value of  $R_1$  and  $R_2$  shown in Figure



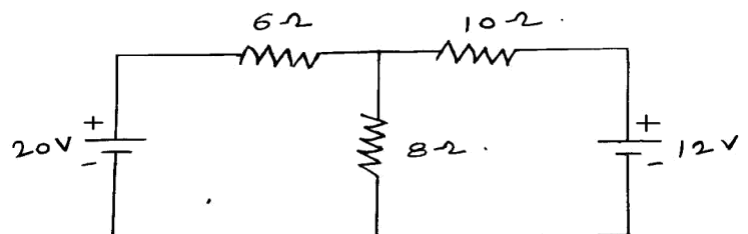- Find current through  $8\Omega$  resistance using nodal analysis in Figure






### MCQ Question


(Total number of Question=Marks\*3=16\*3=48)

Note: Correct answer is marked with **bold**.

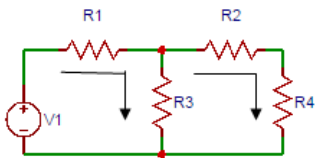
- Mesh analysis is applicable for non planar networks also.
  - True
  - false**
- A mesh is a loop which contains \_\_\_\_\_ number of loops within it.
  - 1
  - 2
  - 3
  - no loop**
- Consider the circuit shown below. The number mesh equations that can be formed are?



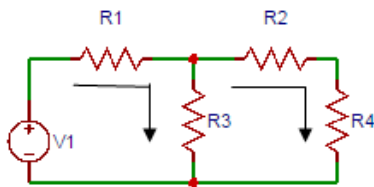- 1
  - 2**
  - 3
  - 4
4. In the figure shown below, the current through loop 1 be  $I_1$  and through the loop 2 be  $I_2$ , then the current flowing through the resistor  $R_2$  will be?




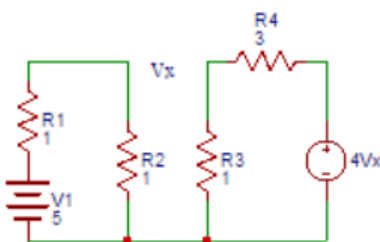- $I_1$
  - $I_2$
  - $I_1 - I_2$
  - $I_1 + I_2$
5. If there are 5 branches and 4 nodes in graph, then the number of mesh equations that can be formed are?
- 2**
  - 4
  - 6
  - 8
6. Consider the circuit shown in the figure. Find voltage  $V_x$ .




- 1
- 1.25**
- 1.5
- 1.75

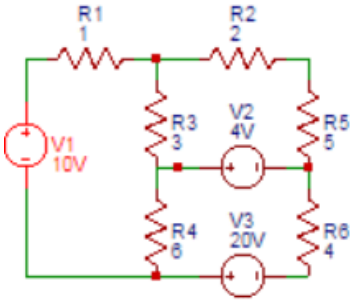7. Consider the circuit shown below. Find the current  $I_1$ .




- a) 3.3  
**b) 4.3**  
 c) 5.3  
 d) 6.3

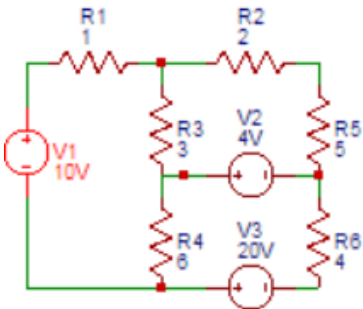8. Consider the following figure. Find the current  $I_2$  (.




- a) 1.7  
**b) 2.6**  
 c) 3.6  
 d) 4.6

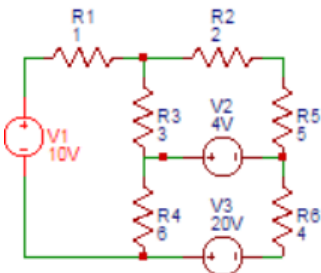9. Consider the following figure. Find the current  $I_3$  (.



- a) 4  
**b) 4.7**  
 c) 5  
 d) 5.7

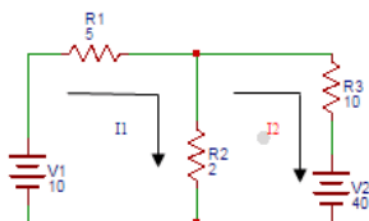10. Find current through  $R_2$  resistor.



- a) 3  
**b) 3.25**  
 c) 3.5  
**d) 3.75**

11. If there are 8 nodes in network, we can get \_\_\_\_\_ number of equations in the nodal analysis.

- a) 9
- b) 8
- c) 7
- d) 6


12. Nodal analysis can be applied for non planar networks also.

- a) True
- b) False

13. In nodal analysis how many nodes are taken as reference nodes?


- a) 1
- b) 2
- c) 3
- d) 4

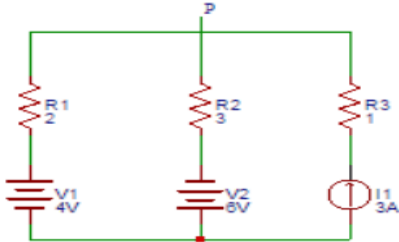14. Find the voltage at node P in the following figure.




- a) 8V
- b) 9V
- c) 10V
- d) 11V

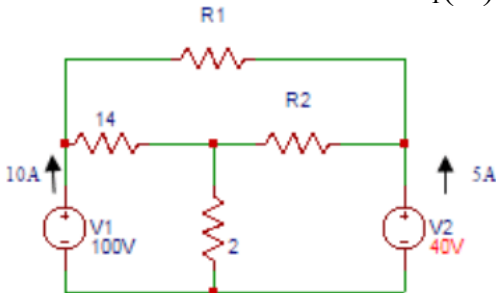15. Find the resistor value  $R_1(\Omega)$  in the figure shown below.




- a) 10
- b) 11
- c) 12
- d) 13

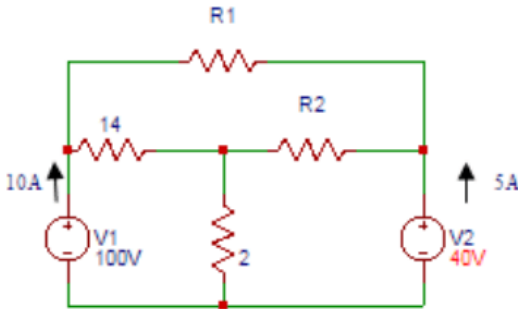16. Find the value of the resistor  $R_2 (\Omega)$  in the circuit shown below.




- a) 5
- b) 6
- c) 7
- d) 8

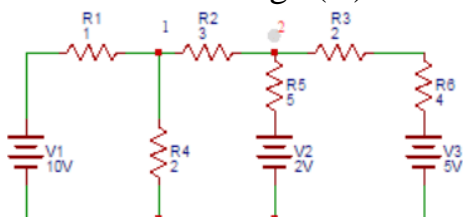17. Find the voltage (V) at node 1 in the circuit shown.




- a) 5.32  
 b) **6.32**  
 c) 7.32  
 d) 8.32

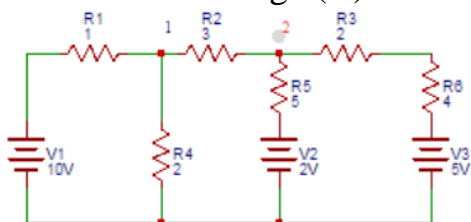18. Find the voltage (V) at node 2 in the circuit shown below.




- a) 2.7  
 b) 3.7  
 c) **4.7**  
 d) 5.7

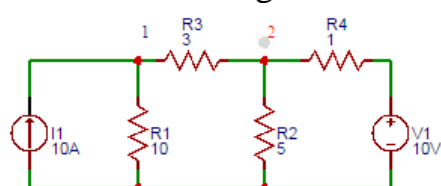19. Find the voltage at node 1 of the circuit shown below.



- a) 32.7  
 b) **33.7**  
 c) 34.7  
 d) 35.7

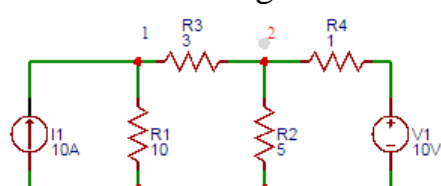20. Find the voltage at node 2 of the circuit shown below.



- a) 13  
 b) **14**  
 c) 15  
 d) 16

21. By using source transformation voltage source in series resistor is replaced by

- a) Voltage source in series with a resistor  
 b) **Current source in parallel with a resistor**  
 c) Voltage source in parallel with a resistor  
 d) Current source in series with a resistor


22. Source Transformation is \_\_\_\_\_

- a) Unilateral  
 b) Unique  
 c) **Bilateral**  
 d) Complicated

23. If there are two resistors in parallel and in series with a voltage source then


- a) **Parallel resistor has no effect**  
 b) Series resistor has no effect  
 c) Both has their respective effects  
 d) Both has no effect on the voltage source

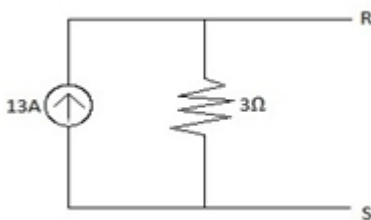24. Using source transformation, calculate the voltage.




- a) 4.33V  
 b) **39V**  
 c) 0.230V  
 d) 36V

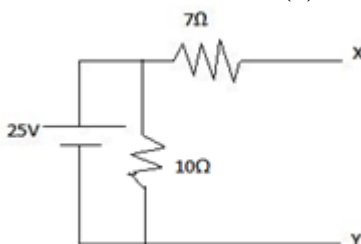25. Which element(s) has no effect in the given circuit?



- a) 7Ω  
 b) **10Ω**  
 c) Both 7Ω and 10Ω  
 d) Voltage source.

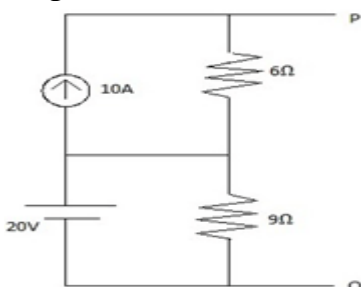26. The value of current source is \_\_\_\_\_ after replacing the given network with a single current source and a resistor.




- a) 70V  
 b) 60V  
 c) 90V  
 d) **80V**

27. If there is a 12A current source in series with 2Ω and in parallel with a 4Ω resistor, then voltage V=?


- a) 24V  
 b) **48V**  
 c) 3V  
 d) 6V

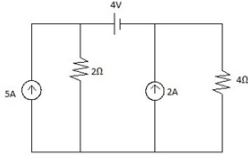28. Find the current flowing through  $4\Omega$  resistor shown in network below.



- a) 1.33A  
 b) 2.35A  
 c) **1.66A**  
 d) 2.66A

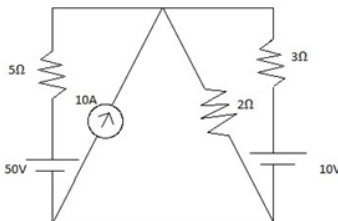29. Calculate the power delivered by the 50V source.




- a) **274W**  
 b) 276W  
 c) 285W  
 d) 291W

30. Source transformation can be used for dependent sources.


- a) **True**  
 b) False

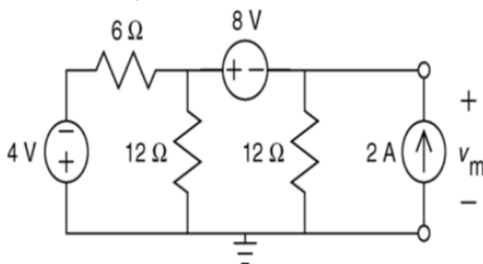31. Using source transformation, calculate  $v_m$ .



- a) 2v  
 b) **-2v**  
 c) 1v  
 d) -1v

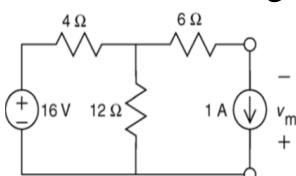32. Find the voltage value  $V_m$  in the circuit given below.




- a) **-3V**  
 b) 3V  
 c) 2.1V  
 d) -2.1V
33. Source transformation technique is mainly based on \_\_\_\_\_ law.
- a) Newton's  
 b) Kirchhoff's  
 c) **Ohm's**  
 d) Einstein's




34. In source transformation,
- Voltage sources remain same
  - Current sources remain same
  - Both voltage and current sources undergo change
  - Resistances/Impedances remain same**
35. If there are five 20V voltage sources in parallel, then in source transformation

- All are considered
- Only one is considered**
- All are ignored
- Only 2 are considered

36. Find the equivalent delta circuit.

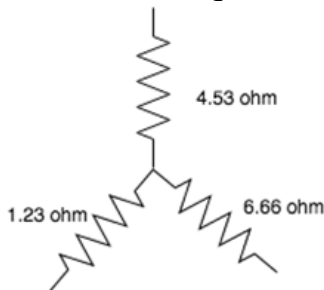

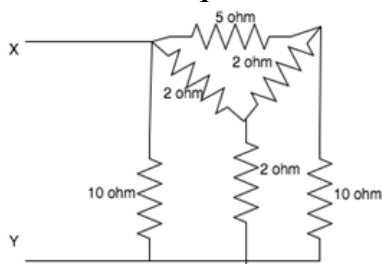- 9.69 ohm, 35.71 ohm, 6.59 ohm**
  - 10.69 ohm, 35.71 ohm, 6.59 ohm
  - 9.69 ohm, 34.71 ohm, 6.59 ohm
  - 10.69 ohm, 35.71 ohm, 7.59 ohm
37. Which, among the following is the correct expression for star-delta conversion?
- $R_1 = R_a * R_b / (R_a + R_b + R_c)$ ,  $R_2 = R_b * R_c / (R_a + R_b + R_c)$ ,  $R_3 = R_c * R_a / (R_a + R_b + R_c)$
  - $R_1 = R_a / (R_a + R_b + R_c)$ ,  $R_2 = R_b / (R_a + R_b + R_c)$ ,  $R_3 = R_c / (R_a + R_b + R_c)$
  - $R_1 = R_a + R_b + R_a * R_b / R_c$ ,  $R_2 = R_c + R_b + R_c * R_b / R_a$ ,  $R_3 = R_a + R_c + R_a * R_c / R_b$**
  - $R_1 = R_a * R_b / R_c$ ,  $R_2 = R_c * R_b / R_a$ ,  $R_3 = R_a * R_c / R_b$
38. Find the equivalent resistance between X and Y.



- 3.33 ohm
  - 4.34 ohm
  - 5.65 ohm
  - 2.38 ohm**
39. Delta connection is also known as \_\_\_\_\_
- Y-connection
  - Mesh connection**
  - Either Y-connection or mesh connection
  - Neither Y-connection nor mesh connection
40.  $R_a$  is resistance at A,  $R_b$  is resistance at B,  $R_c$  is resistance at C in star connection. After transforming to delta, what is resistance between B and C?

- a)  $R_c + R_b + R_c \cdot R_b / R_a$   
 b)  $R_c + R_b + R_a \cdot R_b / R_c$

- c)  $R_a + R_b + R_a \cdot R_c / R_b$   
 d)  $R_c + R_b + R_c \cdot R_a / R_b$

41.  $R_a$  is resistance at A,  $R_b$  is resistance at B,  $R_c$  is resistance at C in star connection. After transforming to delta, what is resistance between A and C?

- a)  $R_a + R_b + R_a \cdot R_b / R_c$   
 b)  $R_a + R_c + R_a \cdot R_c / R_b$

- c)  $R_a + R_b + R_a \cdot R_c / R_a$   
 d)  $R_a + R_c + R_a \cdot R_b / R_c$

42.  $R_a$  is resistance at A,  $R_b$  is resistance at B,  $R_c$  is resistance at C in star connection. After transforming to delta, what is resistance between A and B?

- a)  $R_c + R_b + R_a \cdot R_b / R_c$   
 b)  $R_a + R_b + R_a \cdot R_c / R_b$

- c)  $R_a + R_b + R_a \cdot R_b / R_c$   
 d)  $R_a + R_c + R_a \cdot R_c / R_b$

43. If a 1ohm 2ohm and 32/3ohm resistor is connected in star, find the equivalent delta connection.

- a) **34 ohm, 18.67 ohm, 3.19 ohm**  
 b) 33 ohm, 18.67 ohm, 3.19 ohm


- c) 33 ohm, 19.67 ohm, 3.19 ohm  
 d) 34 ohm, 19.67 ohm, 3.19 ohm

44. If an 8/9ohm, 4/3ohm and 2/3ohm resistor is connected in star, find its delta equivalent.

- a) **4ohm, 3ohm, 2ohm**  
 b) 1ohm, 3ohm, 2ohm

- c) 4ohm, 1ohm, 2ohm  
 d) 4ohm, 3ohm, 1ohm

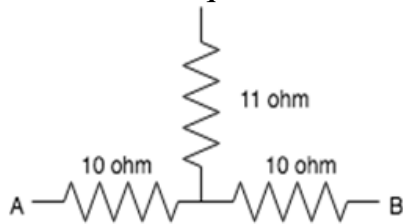45. Find the equivalent resistance between A and B.



- a) 32ohm  
 b) 31ohm

- c) 30ohm  
 d) **29ohm**

46. Source transformation technique is mainly based on \_\_\_\_\_ law.

- a) Newton's  
 b) Kirchhoff's

- c) **Ohm's**  
 d) Einstein's

47. In source transformation,

- a) Voltage sources remain same  
 b) Current sources remain same  
 c) Both voltage and current sources undergo change  
 d) **Resistances/Impedances remain same**

48. If there are two resistors in parallel and in series with a voltage source then

- a) **Parallel resistor has no effect**  
 b) Series resistor has no effect  
 c) Both has their respective effects  
 d) Both has no effect on the voltage source

# NETWORK THEOREMS

Position in Question Paper

Total Marks-24

Q.1. f) 2-Marks.

g) 2-Marks.

Q.3. e) 4-Marks.


Q.4. d) 4-Marks.

Q.5. c) 6-Marks.


Q.6. c) 6-Marks.

## Descriptive Question

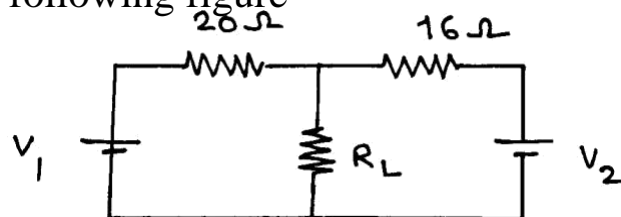
1. State 'Norton's' theorem with advantages, disadvantages, limitation, application and stepwise procedure to apply it.
2. State maximum power transfer theorem for AC circuits with advantages, disadvantages, limitation, and application and stepwise procedure to apply it.
3. State superposition theorem for AC and DC circuits with advantages, disadvantages, limitation, application and stepwise procedure to apply it.
4. State Thevenin's theorem with advantages, disadvantages, limitation, and application and stepwise procedure to apply it.
5. State Reciprocity theorem with advantages, disadvantages, limitation, and application and stepwise procedure to apply it.
6. Find  $R_{TH}$  from following figure



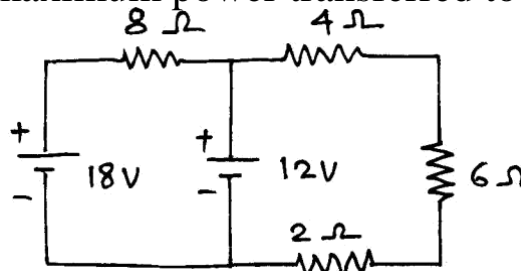7. Find the value of maximum power transferred to  $R_L = 6\Omega$  from the source of figure



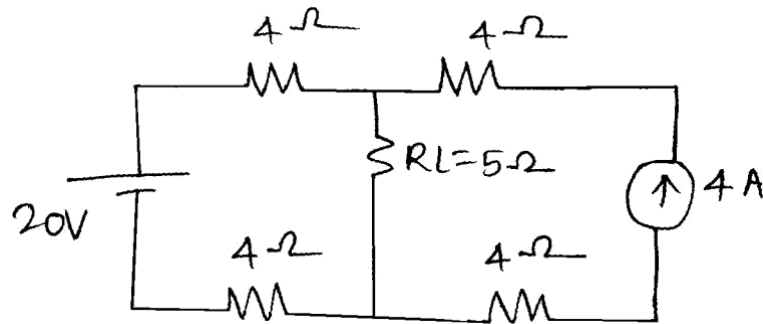8. Using Thevenin's theorem find current through  $5\Omega$  resistance. figure




## MCQ Question

(Total number of Question=Marks\*3=24\*3=72)


Note: Correct answer is marked with **bold**.

- The Norton current is the \_\_\_\_\_
  - Short circuit current**
  - Open circuit current
  - Open circuit and short circuit current
  - Neither open circuit nor short circuit current
- Norton resistance is found by?
  - Shorting all voltage sources
  - Opening all current sources
  - Shorting all voltage sources and opening all current sources**
  - Opening all voltage sources and shorting all current sources
- Norton's theorem is true for \_\_\_\_\_
  - Linear networks**
  - Non-Linear networks
  - Both linear networks and nonlinear networks
  - Neither linear networks nor non-linear networks
- In Norton's theorem  $I_{sc}$  is \_\_\_\_\_
  - Sum of two current sources
  - A single current source**
  - Infinite current sources
  - 0
- $I_{sc}$  is found across the \_\_\_\_\_ terminals of the network.
  - Input
  - Output**
  - Neither input nor output
  - Either input or output
- Can we use Norton's theorem on a circuit containing a BJT?
  - Yes
  - No**
  - Depends on the BJT
  - Insufficient data provided
- Calculate the Norton resistance for the following circuit if 5 ohm is the load resistance.

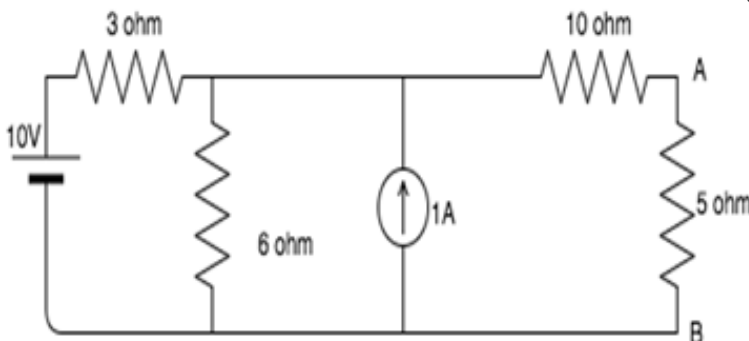


- 10 ohm
- 11 ohm
- 12 ohm**
- 13 ohm

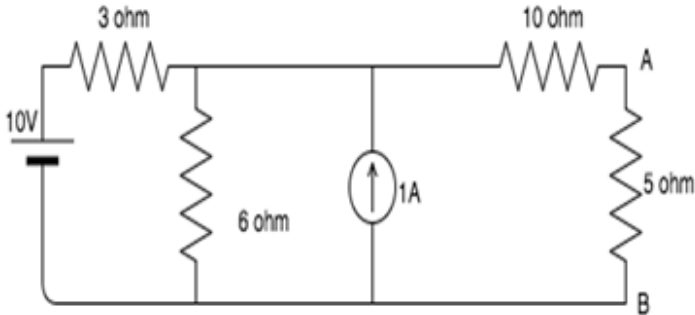8. Calculate the short circuit current is the 5 ohm resistor is the load resistance.



- a) **0.72A**
- b) 0.32A
- c) 0.83A
- d) 0.67A

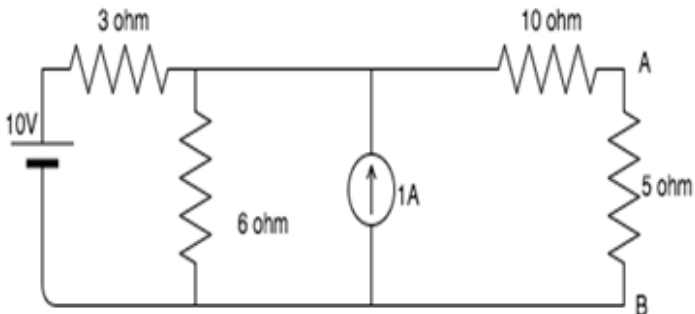9. Find the current in the 5 ohm resistance using Norton's theorem.



- a) 1A
- b) 1.5A
- c) 0.25A
- d) **0.5A**

10. Which of the following is also known as the dual of Norton's theorem?

- a) **Thevenin's theorem**
- b) Superposition theorem
- c) Maximum power transfer theorem
- d) Millman's theorem

11. In superposition theorem, when we consider the effect of one voltage source, all the other voltage sources are \_\_\_\_\_

- a) **Shorted**
- b) Opened
- c) Removed
- d) Undisturbed

12. In superposition theorem, when we consider the effect of one current source, all the other voltage sources are \_\_\_\_\_

- a) **Shorted**
- b) Opened
- c) Removed
- d) Undisturbed

13. In superposition theorem, when we consider the effect of one voltage source, all the other current sources are \_\_\_\_\_


- a) Shorted
- b) **Opened**
- c) Removed
- d) Undisturbed

14. In superposition theorem, when we consider the effect of one current source, all the other current sources are \_\_\_\_\_

- a) Shorted
- b) **Opened**
- c) Removed
- d) Undisturbed




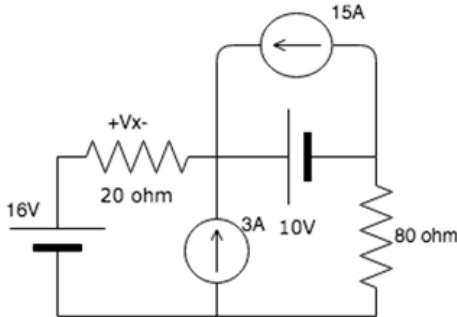15. Find the value of  $V_x$  due to the 16V source.




- a) 4.2V  
 b) **3.2V**  
 c) 2.3V  
 d) 6.3V

16. Find  $V_x$  due to the 3A source.

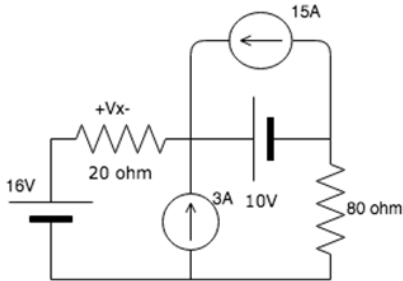


- a) 56V  
 b) 78V  
 c) 38V  
 d) **48V**

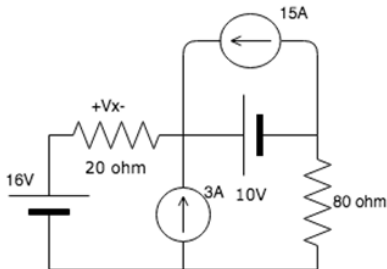17. Find the value of  $V_x$  due to the 10V source.



- a) 1V  
 b) **2V**  
 c) 3V  
 d) 4V

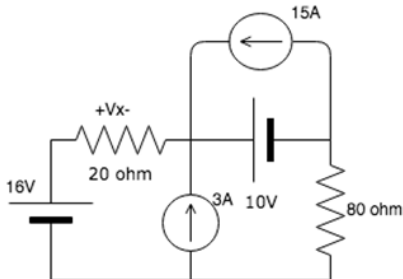18. Find the voltage due to the 15A source.




- a) **0V**  
 b) 2V  
 c) 4V  
 d) 6V


19. Superposition theorem is valid for \_\_\_\_\_

- a) **Linear systems**  
 b) Non-linear systems

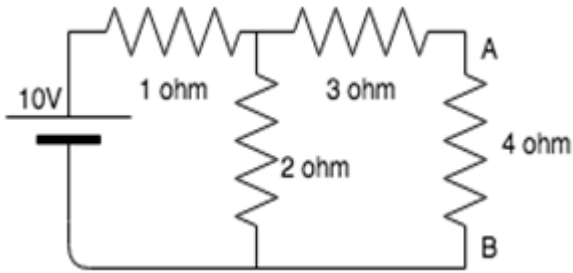
- c) Both linear and non-linear systems  
 d) Neither linear nor non-linear systems
20. Superposition theorem does not work for \_\_\_\_\_
- a) Current  
 b) Voltage  
 c) **Power**  
 d) Works for all: current, voltage and power
21. Calculate the Thevenin resistance across the terminal AB for the following circuit.



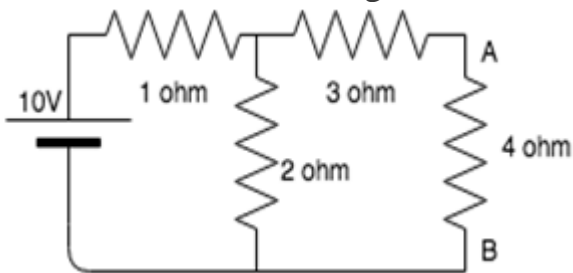- a) 4.34 ohm  
 b) **3.67 ohm**  
 c) 3.43 ohm  
 d) 2.32 ohm
22. Calculate  $V_{th}$  for the given circuit.




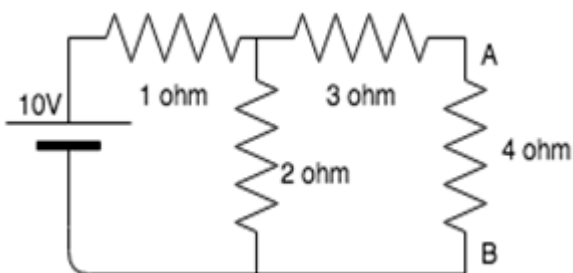- a) 5.54V  
 b) 3.33V  
 c) **6.67V**  
 d) 3.67V
23. Calculate the current across the 4 ohm resistor.




- a) **0.86A**  
 b) 1.23A  
 c) 2.22A  
 d) 0.67A
24. The Thevenin voltage is the \_\_\_\_\_
- a) **Open circuit voltage**  
 b) Short circuit voltage  
 c) Open circuit and short circuit voltage  
 d) Neither open circuit nor short circuit voltage
25. Thevenin resistance is found by \_\_\_\_\_

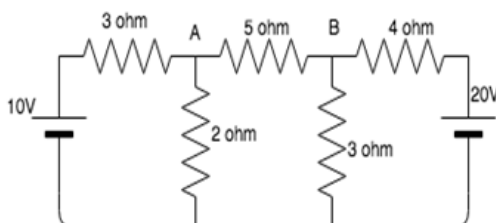- a) Shorting all voltage sources  
 b) Opening all current sources  
 c) **Shorting all voltage sources and opening all current sources**  
 d) Opening all voltage sources and shorting all current sources
26. Thevenin's theorem is true for \_\_\_\_\_  
 a) **Linear networks**  
 b) Non-Linear networks  
 c) Both linear networks and nonlinear networks  
 d) Neither linear networks nor non-linear networks
27. In Thevenin's theorem  $V_{th}$  is \_\_\_\_\_  
 a) Sum of two voltage sources  
 b) **A single voltage source**  
 c) Infinite voltage sources  
 d) 0
28.  $V_{th}$  is found across the \_\_\_\_\_ terminals of the network.  
 a) Input  
 b) **Output**  
 c) Neither input nor output  
 d) Either input or output
29. Which of the following is also known as the dual of Thevenin's theorem?  
 a) **Norton's theorem**  
 b) Superposition theorem  
 c) Maximum power transfer theorem  
 d) Millman's theorem
30. Can we use Thevenin's theorem on a circuit containing a BJT?  
 a) Yes  
 b) **No**  
 c) Depends on the BJT  
 d) Insufficient data provided
31. The maximum power drawn from source depends on \_\_\_\_\_  
 a) Value of source resistance  
 b) **Value of load resistance**  
 c) Both source and load resistance  
 d) Neither source or load resistance
32. The maximum power is delivered to a circuit when source resistance is \_\_\_\_\_ load resistance.  
 a) Greater than  
 b) **Equal to**  
 c) Less than  
 d) Greater than or equal to
33. If source impedance is a complex number  $Z$ , then load impedance is equal to \_\_\_\_\_  
 a)  **$Z'$**   
 b)  $-Z$   
 c)  $-Z'$   
 d)  $Z$
34. If  $Z_L = Z_s'$ , then  $R_L = ?$   
 a)  $-R_L$   
 b)  **$R_s$**   
 c)  $-R_s$   
 d) 0
35. Calculate the value of  $R_L$  across A and B.




- a) 3.45ohm  
 b) **2.91ohm**  
 c) 6.34ohm  
 d) 1.54ohm

36. Calculate Eth.

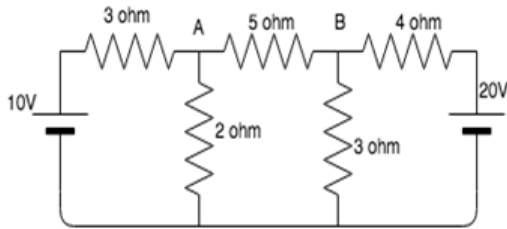

- a) 3.43V  
 b) **4.57V**  
 c) 3.23V  
 d) 5.34V

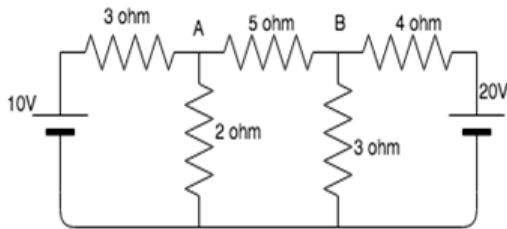37. Calculate the maximum power transferred.



- a) **1.79W**  
 b) 4.55W  
 c) 5.67W  
 d) 3.78W

38. Does maximum power transfer imply maximum efficiency?

- a) Yes  
 b) **No**  
 c) Sometimes  
 d) Cannot be determined

39. Under the condition of maximum power efficiency is?

- a) 100%  
 b) 0%  
 c) 30%  
 d) **50%**

40. Name some devices where maximum power has to be transferred to the load rather than maximum efficiency.

- a) Amplifiers  
 b) Communication circuits  
 c) **Both amplifiers and communication circuits**  
 d) Neither amplifiers nor communication

41. To check for the Reciprocity Theorem we consider \_\_\_\_\_ of response to excitation.

- a) **Ratio**  
 b) Addition  
 c) Product  
 d) subtraction


42. For the Reciprocity Theorem to satisfy the ratio of response to excitation before and after the source is replaced should be?

- a) different  
 b) **Same**  
 c) before source is replaced is greater than after the source is replaced  
 d) before source is replaced is less than after the source is replaced

43. The circuit which satisfies Reciprocity Theorem is called?


- a) Short circuit  
 b) Open circuit  
 c) **Linear circuit**  
 d) Non-linear circuit

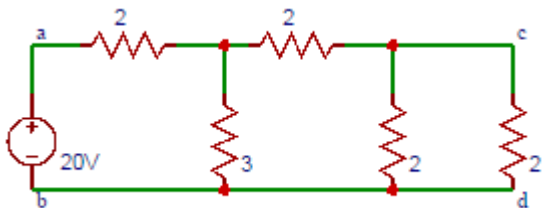44. Find the current through the  $2\Omega$  (c-resistor in the circuit shown below.




- a) 0.143
- b) 1.43**
- c) 14.3
- d) 143

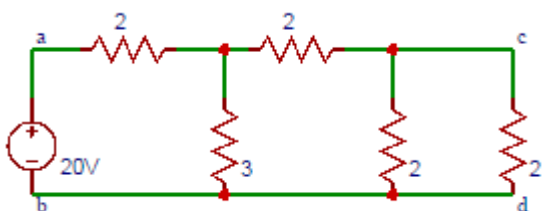45. In the following circuit, the current drawn by  $2\Omega$  resistor (a-after the source is replaced is?




- a) 143
- b) 14.3
- c) 1.43**
- d) 0.143

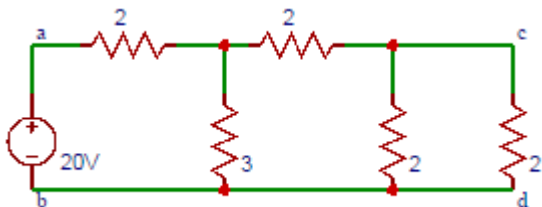46. The following circuit satisfies Reciprocity Theorem.




- a) True**
- b) False

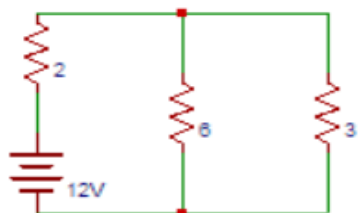47. Find the current through  $3\Omega$  resistor in the circuit shown below.




- a) 1
- b) 2**
- c) 3
- d) 4

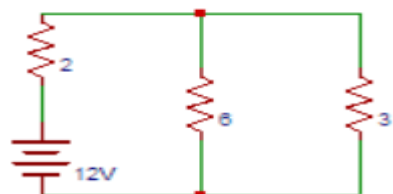48. Find the current through  $2\Omega$  resistor after source is replaced in the below circuit.



- a) 4  
 b) 3  
 c) 2  
 d) 1

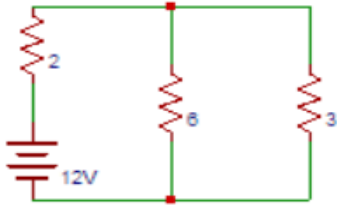49. The following circuit satisfies the reciprocity theorem.




- a) False  
 b) **True**

50. While considering Reciprocity theorem, we consider ratio of response to excitation as ratio of?


- a) voltage to voltage  
 b) current to current  
 c) **voltage to current**  
 d) none of the mentioned

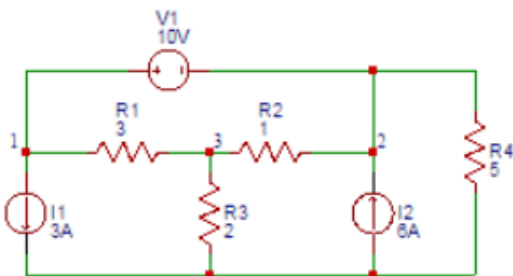51. Consider the figure shown below. Find the voltage (V) at node 1.




- a) 13  
 b) **14**  
 c) 15  
 d) 16

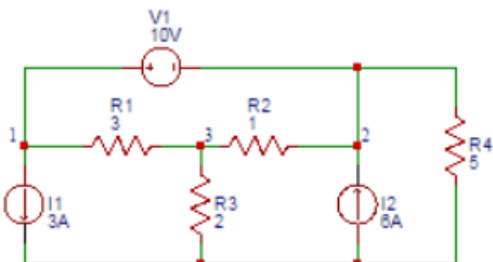52. Consider the figure shown below. Find the voltage (V) at node 2.



- a) 3  
 b) **4**  
 c) 5  
 d) 6

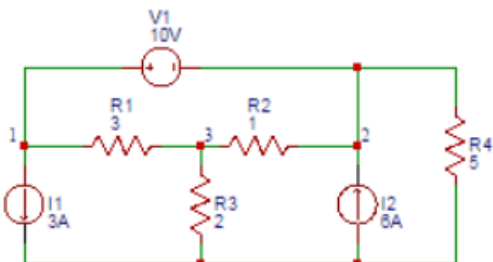
53. Consider the figure shown below. Find the voltage (V) at node 3.



- a) **4.5**  
 b) 5.5  
 c) 6.5  
 d) 7.5




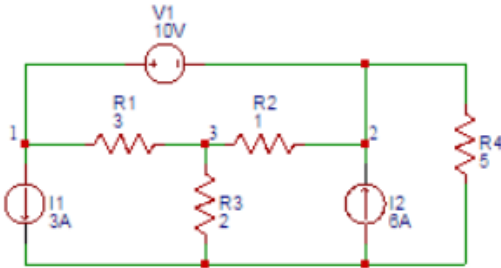54. Consider the figure shown below. Find the power (W) delivered by the source 6A.




- a) 20.3
- b) 1.3
- c) 22.3
- d) 24.3

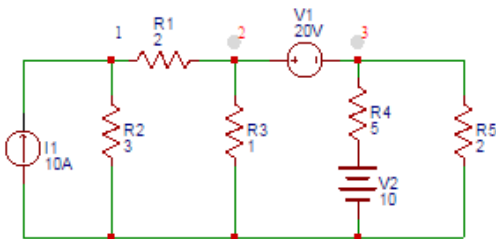55. Find the voltage (V) at node 1 in the circuit shown below.




- a) 18
- b) 19
- c) 20
- d) 21

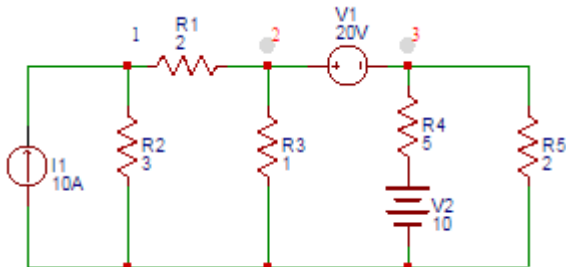56. Consider the figure shown below. Find the voltage (V) at node 2.




- a) 11.5
- b) 12
- c) 12.5
- d) 13

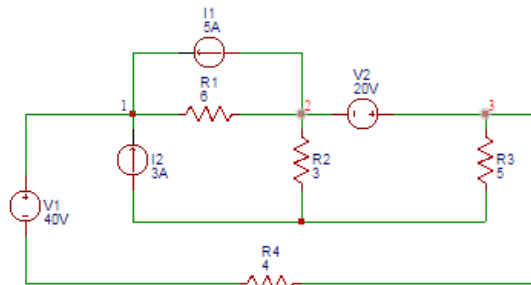57. Find the voltage (V) at node 3 in the figure shown below.




- a) 18
- b) 20
- c) 22
- d) 24

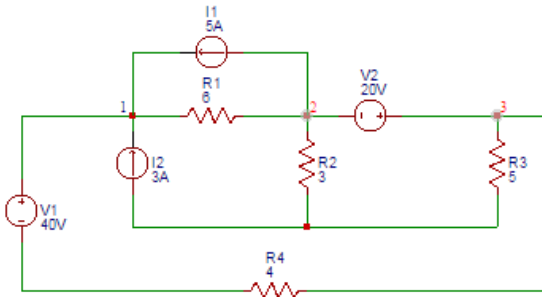58. Find the power absorbed by  $5\Omega$  resistor in the following figure.




- a) 60  
**b) 65.5**  
 c) 70.6  
 d) 75

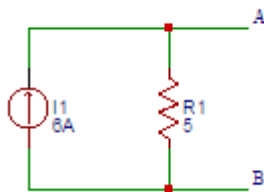59. Find the value of the voltage (V) in the equivalent voltage source of the current source shown below.




- a) 20  
 b) 25  
**c) 30**  
 d) 35

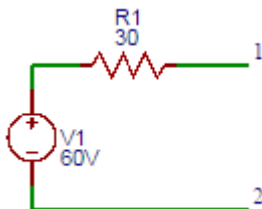60. Find the value of the current ( in the equivalent current source of the voltage source shown below.



- a) 1  
**b) 2**  
 c) 3  
 d) 4

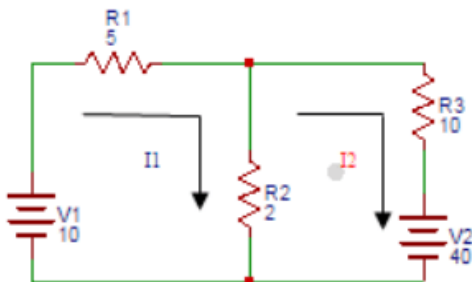61. Find current through  $R_2$  resistor.



- a) 3  
**b) 3.25**  
 c) 3.5  
**d) 3.75**

62. If there are 8 nodes in network, we can get \_\_\_\_\_ number of equations in the nodal analysis.

- a) 9
- b) 8
- c) 7
- d) 6


63. Nodal analysis can be applied for non planar networks also.

- a) True
- c) False

64. In nodal analysis how many nodes are taken as reference nodes?


- a) 1
- b) 2
- c) 3
- d) 4

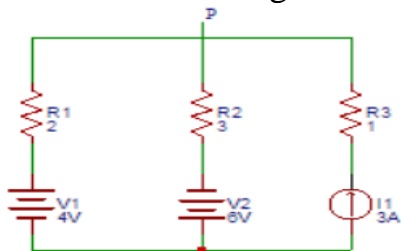65. Find the voltage at node P in the following figure.




- a) 8V
- b) 9V
- c) 10V
- d) 11V

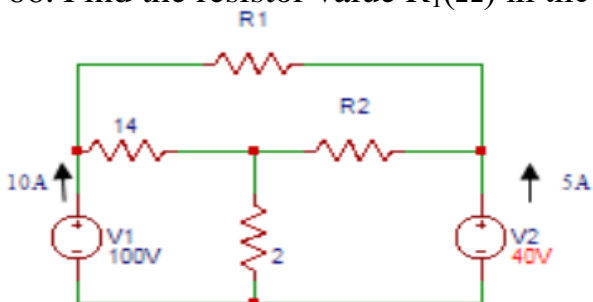66. Find the resistor value  $R_1(\Omega)$  in the figure shown below.




- a) 10
- b) 11
- c) 12
- d) 13

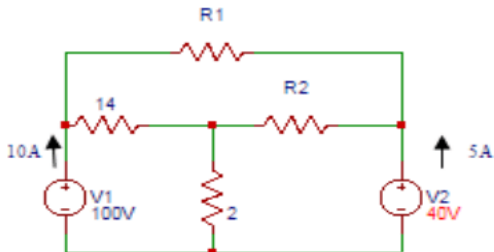67. Find the value of the resistor  $R_2(\Omega)$  in the circuit shown below.




- a) 5
- b) 6
- c) 7
- d) 8

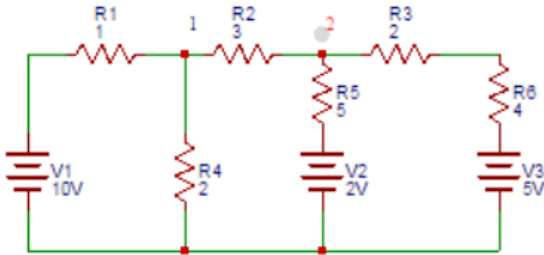68. Find the voltage (V) at node 1 in the circuit shown.




- a) 5.32
- b) 6.32**
- c) 7.32
- d) 8.32

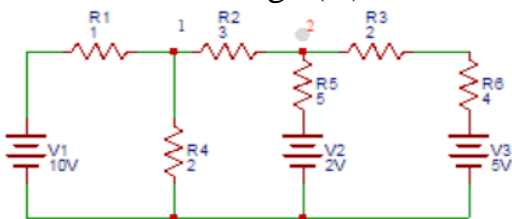69. Find the voltage (V) at node 2 in the circuit shown below.




- a) 2.7
- b) 3.7
- c) 4.7**
- d) 5.7

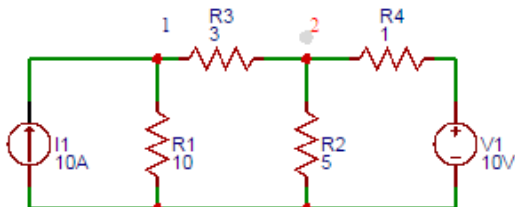70. Find the voltage at node 1 of the circuit shown below.



- a) 32.7
- b) 33.7**
- c) 34.7
- d) 35.7

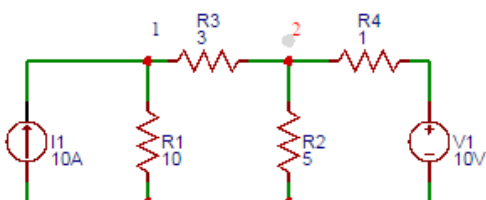71. Find the voltage at node 2 of the circuit shown below.



- a) 13
- b) 14**
- c) 15
- d) 16

72. In nodal analysis how many nodes are taken as reference nodes?

- a) 1**
- b) 2
- c) 3
- d) 4