



Maratha Vidya Prasarak Samaj's

Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

Subject:- Basic Electronics (22216)



SYLLABUS

Chapter No.	Name of Unit	Marks With Option
1	Semiconductor diodes	20
2	Applications of diode	24
3	Bipolar Junction Transistor	26
4	Field effect Transistor	18
5	Regulators and Power Supply	14
Total Marks :-		102



BOARD THEORY

PAPER PATTERN

FOR BEL (22216)

Q.1		Attempt any FIVE	5*2=10
	a)	Semiconductor diodes	
	b)	Field effect Transistor	
	c)	Bipolar Junction Transistor	
	d)	Field effect Transistor	
	e)	Bipolar Junction Transistor	
	f)	Regulators and Power Supply	
	g)	Semiconductor diodes	
Q.2		Attempt any THREE	3*4=12
	a)	Semiconductor diodes	
	b)	Bipolar Junction Transistor	
	c)	Regulators and Power Supply	
	d)	Bipolar Junction Transistor	
Q.3		Attempt any THREE	3*4=12
	a)	Applications of diode	



Maratha Vidya Prasarak Samaj's
Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

	b)	Applications of diode
	c)	Field effect Transistor
	d)	Regulators and Power Supply
Q.4		Attempt any FOUR 3*4=12
	a)	Applications of diode
	b)	Bipolar Junction Transistor
	c)	Bipolar Junction Transistor
	d)	Field effect Transistor
	e)	Regulators and Power Supply
Q.5		Attempt any TWO 2*6=12
	a)	Field effect Transistor
	b)	Applications of diode
	c)	Semiconductor diodes
Q.6		Attempt any TWO 2*6=12
	a)	Semiconductor diodes
	b)	Applications of diode
	c)	Bipolar Junction Transistor



CLASS TEST - I

PAPER PATTERN

COURSE: - Basic Electronics (22216)

PROGRAMME: - E&TC Engineering

Syllabus :-

Unit No.	Name of the Unit	Course Outcome (CO)
1	Semiconductor diodes	CO-216.1
2	Applications of diode	CO-216.2
3	Bipolar Junction Transistor	CO-216.3

Q.1	Attempt any FOUR 4*2=8Marks	Course Outcome (CO)
a)	Semiconductor diodes	CO-216.1
b)	Applications of diode	CO-216.2
c)	Applications of diode	CO-216.2
d)	Bipolar Junction Transistor	CO-320.3
e)	Bipolar Junction Transistor	CO-216.3
f)	Semiconductor diodes	CO-216.1
Q.2	Attempt any THREE 3*4=12 Marks	
a)	Semiconductor diodes	CO-216.1
b)	Applications of diode	CO-216.2
c)	Bipolar Junction Transistor	CO-216.3
d)	Applications of diode	CO-216.2
e)	Applications of diode	CO-216.2
f)	Bipolar Junction Transistor	CO-216.3



CLASS TEST - II

PAPER PATTERN

COURSE: - Basic Electronics (22216)

PROGRAMME: - E&TC Engineering

Syllabus :-

Unit	Name of the Unit	Course Outcome(CO)
3	Bipolar Junction Transistor	CO-216.3
4	Field effect Transistor	CO-216.4
5	Regulators and Power Supply	CO-216.5

Q.1	Attempt any FOUR	4*2=8Marks	Course Outcome (CO)
a)	Bipolar Junction Transistor		CO-216.3
b)	Field effect Transistor		CO-216.4
c)	Bipolar Junction Transistor		CO-216.3
d)	Field effect Transistor		CO-216.4
e)	Regulators and Power Supply		CO-216.5
f)	Regulators and Power Supply		CO-216.5
Q.2	Attempt any THREE	3*4=12 Marks	
a)	Bipolar Junction Transistor		CO-216.3
b)	Field effect Transistor		CO-216.4
c)	Field effect Transistor		CO-216.4
d)	Regulators and Power Supply		CO-216.5
e)	Bipolar Junction Transistor		CO-216.3
f)	Bipolar Junction Transistor		CO-216.3



COURSE OUTCOME

(CO)

COURSE: - Basic Electronics (22216)

PROGRAMME: - E&TC Engineering

CO.NO	Course Outcome
CO-216.1	Use relevant diode in different electronics circuits.
CO-216.2	Maintain rectifiers comprising of diodes.
CO-216.3	Use BJT in electronics circuits.
CO-216.4	Use FET in electronics circuits.
CO-216.5	Maintain DC regulated power supply.



1. Semiconductor diode

Position in Question Paper

Total Marks-20

Q.1. a) 2-Marks.

Q.1. g) 2-Marks.

Q.2. a) 4-Marks.

Q.5. c) 6-Marks.

Q.6. a) 6-Marks.

Descriptive Question

1. Explain the forward and reverse bias characteristics of PN junction diode?
2. Write the diode equation and discuss the effect of temperature on diode current?
3. The current flowing in a silicon PN diode at room temperature is $10 \mu\text{A}$, when the large reverse bias is applied. Calculate the current flowing when 0.2V forward bias is applied?
4. Calculate the factor by which the current will increase in silicon diode operating at 5M a forward voltage of 0.4V when the temperature is raised from 25°C to 150°C ?
5. Describe the principle of operation of and V-I characteristics of
 - a) Photo diode
 - b) LED
6. Describe the V-I characteristics of P-N Junction diode?
7. Differentiate between tunnel diode and normal PN junction diode?
8. Derive the expression for dynamic resistance of PN diode?
9. With simple circuit explains how the zener diode acts as a voltage regulator



- 10.** Write short notes on LED Sketch and explain the volt-ampere characteristics of a Zener diode.
- 11.** Draw band diagram of PN junction under open circuit conditions and explain?
- 12.** What are the general specifications of PN junction diode?
- 13.** With neat sketch explain principle and operation of Zener diode?
- 14.** What are the basic applications of conventional diode and zener diode?



MCQ Questions:-

(Total number of Question=Marks*3=14*3=42)

Note: Correct answer is marked with **bold**.

- Why is there a sudden increase in current in Zener diode?
a) Due to the rupture of ionic bonds c) Due to viscosity
b) Due to covalent bonds d) Due to potential difference
- What is the semiconductor diode used as?
a) Oscillator **c) Rectifier**
b) Amplifier d) Modulator
- What is a Zener diode used as?
a) Oscillator c) Rectifier
b) Regulator d) Filter
- When a junction diode is reverse biased, what causes current across the junction?
a) Diffusion of charges **c) Drift of charges**
b) Nature of material d) Both drift and diffusion of charges
- What can a p-n junction diode be used as?
a) Condenser c) Amplifier
b) Regulator **d) Rectifier**
- Current carrier in conductors is_
a) Electron c) Neutron
b) Proton d) Positron
- Which group among the following is insulator?
a) Silver, copper, gold c) The human body, wood, iron
b) Paper, glass, cotton d) Glass, copper, paper
- The band gap bet the valence band and conduction band is the measure of _
a) The conductivity of material c) Charge density
b) The resistivity of material d) Ease of ionization
- The rubber used in the wheels of aero-plane is _____
a) Perfect insulator c) Can be an insulator or conducting
b) Slightly conducting d) Semiconductor



10. Insulation breakdown may occur at _____
- a) **High temperature**
 - b) Low temperature
 - c) At any temperature
 - d) Depends on pressure
11. Superconductors have _____
- a) **Almost zero resistivity**
 - b) Very high resistivity
 - c) Temperature-dependent resistivity
 - d) Moderate value of resistivity
12. An intrinsic semiconductor, at the absolute zero temperature, behaves like which one of the following?
- a) **Insulator**
 - b) Superconductor
 - c) n-type semiconductor
 - d) p-type semiconductor
13. Increases exponentially with the increasing bandgap
- a) Is independent of the temperature and the bandgap
 - b) **Decreases exponentially with the increasing bandgap**
 - c) Decreases with increasing temperature
 - d) None
14. Which of the following statements is not true?
- a) The resistance of intrinsic semiconductor decreases with the increase of temp.
 - b) Doping pure Si with trivalent impurities gives p-type semiconductors
 - c) **The majority carriers in n-type semiconductors are holes**
 - d) A p-n junction can act as a semiconductor diode
15. Holes are charge carriers in which one of the following?
- a) **Intrinsic semiconductors**
 - b) Ionic solids
 - c) n-type semiconductors
 - d) Metals
16. In semiconductors at a room temperature correspond to which among the follo?
- a) **The valence band is partially empty and the conduction band is partially filled**
 - b) The valence band is filled and the conduction band is partially filled
 - c) The valence band is filled
 - d) The conduction band is empty
17. At absolute zero, Si acts as which of the following?
- a) Non-metal
 - b) Metal
 - c) **Insulator**
 - d) Capacitor



19. Choose the false statement from the following.

- a) In conductors the valence and conduction band overlap
- b) Substances with an energy gap of the order of 10 eV are insulators
- c) The resistivity of a semiconductor increases with increase in temperature**
- d) The conductivity of a semiconductor increases with increase in temperature

20. At which temperature, a pure semiconductor behaves slightly as a conductor?

- a) Low temperature
- c) High temperature**
- b) Room temperature
- d) Vacuum

21. In a pure semiconductor crystal, if current flows due to breakage of crystal bonds, then what is the semiconductor called?

- a) Acceptor
- c) Intrinsic semiconductor**
- b) Donor
- d) Extrinsic semiconductor

22. How many junction/s do a diode consist?

- a) 0
- b) 1**
- c) 2
- d) 3

23. If the positive terminal of the battery is connected to the anode of the diode, then it is known as

- a) Forward biased**
- b) Reverse biased
- c) Equilibrium
- d) Schottky barrier

24. During reverse bias, a small current develops known as

- a) Forward current
- c) Reverse saturation current**
- b) Reverse current
- d) Active current

25. If the voltage of the potential barrier is V_0 . A voltage V is applied to the input, at what moment will the barrier disappear?

- a) $V < V_0$
- b) $V = V_0$**
- c) $V > V_0$
- d) $V \ll V_0$

26. What is the maximum electric field when $V_{bi}=2V$, $V_R=5V$ and width of the semiconductor is 7cm?

- a) -100V/m
- b) -200V/m**
- c) 100V/m
- d) 200V/m

27. When the diode is reverse biased with a voltage of 6V and $V_{bi}=0.63V$. potential?

- a) 6V
- b) 6.63V**
- c) 5.27V
- d) 0.63V



28. Zener diodes are also known as
- a) **Voltage regulators**
 - b) Forward bias diode
 - c) Breakdown diode
 - d) None of the mentioned
29. Which of the following is true about the resistance of a Zener diode?
- a) It has an incremental resistance
 - b) It has dynamic resistance
 - c) The value of the resistance is the inverse of the i-v char of the Zener diode
 - d) **All of the mentioned**
30. Which of the following is true about the temp coef of the Zener diode?
- a) For Zener voltage less than 5V, TC is negative
 - b) For Zener voltage around 5V, TC can be made zero
 - c) For higher values of Zener voltage, TC is positive
 - d) **All of the mentioned**
31. Which of the following can be used in series with a Zener diode so that comb. has almost zero temperature coefficient?
- a) **Diode**
 - b) Resistor
 - c) Transistor
 - d) MOSFET
32. In Zener diode, for currents greater than the knee current, the v-i curve is almost
- a) Almost a straight line parallel to y-axis
 - b) **Almost a straight line parallel to x-axis**
 - c) Equally inclined to both the axes with a positive slope
 - d) Equally inclined to both the axes with a negative slope
33. Zener diodes can be effectively used in voltage regulator. However, they are these days being replaced by more efficient
- a) Operational Amplifier
 - b) MOSFET
 - c) **Integrated Circuits**
 - d) None of the mentioned
34. What is the forbidden gap voltage for silicon material?
- a) 1.46 V
 - b) 1.56 V
 - c) 10 V
 - d) **1.21 V**
35. Which of the following parameters of P-N junction diode increases with temp.
- a) Cut in voltage
 - b) **Reverse saturation current.**
 - c) Ideality factor
 - d) Resistance



36. Which of these P-N junction characteristics are not dependent on temperature.
- a) **Junction resistance**
 - b) Reverse saturation current
 - c) Bias current
 - d) Barrier voltage
37. As the temperature to the P-N junction increases the current increases due to?
- a) Leakage in bias region
 - b) **Electron-hole pair**
 - c) Leakage in P region
 - d) Leakage in N region
38. By what percentage the reverse saturation current increases with 10 C rise in the temp.
- a) 25%
 - b) 12.5%
 - c) 50%
 - d) **7%**
39. What will be the decrease of barrier voltage with the rise in 10C in temperature?
- a) 10V
 - b) 1mV
 - c) 10mV
 - d) **2mV**
40. What will be the reverse saturation current in the junction when the voltage across the junction is 0?
- a) 0.3A
 - b) 0.7A
 - c) **0A**
 - d) 1.24A
41. The breakdown voltage of the P-N junction diode decreases due to the increase in.
- a) Reverse saturation current
 - b) **Reverse leakage current**
 - c) Bias voltage
 - d) Barrier voltage
42. A diode is__
- a) Is the simplest of the semiconductor devices
 - b) Has a characteristic that closely follows that of a switch
 - c) Is two terminal device
 - d) **All of the mentioned**



2. Applications of diodes

Position in Question Paper

Total Marks-24

Q.3. a) 4-Marks.

Q.3. b) 4-Marks.

Q.4. a) 4-Marks.

Q.5. b) 6-Marks.

Q.6. b) 6-Marks.

Descriptive Question

1. Describe the operation of Half Wave Rectifier with and with out filters?
2. Derive efficiency and Ripple Factor of half wave rectifier?
3. With neat diagram explain Capacitor input filter and derive its ripple factor.
4. Discuss working of Bridge rectifier & derive its Ripple factor and efficiency?
5. Explain the operation of CLC filter and derive its ripple factor?
6. Explain the operation of inductor input filter with Fullwave Rectifier?
7. Describe the operation of center tapped full wave rectifier along with i/o w/f?
8. Compare Half Wave Rectifier, Full Wave Rectifier and Bridge rectifier?
9. Explain working of π Section filter and derive the expression for ripple factor?
10. Describe about Multiple π -section filters?
11. Explain Multiple L-section filter with neat sketch and derive its ripple factor?
12. Draw the circuit diagram of FWR with inductor filter and explain its operation
13. Compare various filter circuits in terms of its ripple factors.
14. Define ripple factor. What is meant by Peak Inverse Voltage?



MCQ Question

(Total number of Question=Marks*3=16*3=48)

Note: Correct answer is marked with **bold**.

- Which of the following isn't a type of rectifier?
 - Precision Half-wave Rectifier
 - Bridge Rectifier
 - Peak Rectifier
 - None of the mentioned**
- For a half wave or full wave rectifier the Peak Inverse Voltage of the rectifier is always
 - Greater than the input voltage
 - Smaller than the input voltage**
 - Equal to the input voltage
 - Greater than the input voltage for full wave rectifier and smaller for the half wave rectifier
- Bridge rectifier is an alternative for
 - Full wave rectifier**
 - Peak rectifier
 - Half wave rectifier
 - None of the mentioned
- Find V_o when V_i is -1V.
 - 0V**
 - 0.7V
 - 1V
 - 1.7V
- Find V_o when V_i is 2V.
 - 0V**
 - 0.7V
 - 1V
 - 1.7V
- DC average current of a half wave rectifier output is _____
(Where I_m is the maximum peak current of input)
 - $2I_m/\pi$
 - I_m/π**
 - $I_m/2\pi$
 - $1.414I_m/\pi$
- DC power output of half wave rectifier is equal to _____
(I_m is the peak current and R_L is the load resistance)
 - $(2I_m^2/\pi^2)R_L$
 - $(I_m^2/2\pi^2)R_L$
 - $(I_m^2/\pi^2)R_L$**
 - $(4I_m^2/\pi^2)R_L$
- Ripple factor of half wave rectifier is _____
 - 1.414
 - 1.21**
 - 1.3
 - 0.48



37. The value of inductance at which the current in a choke filter does not fall to zero is__
- a) peak inductance
b) cut-in inductance
c) **critical inductance**
d) damping inductance
38. The condition for the regulation curve in a choke filter is ____
- a) **$LC \geq RL/3\omega$**
b) $LC \leq RL/3\omega$
c) $L \geq RL/3\omega$
d) $LC \geq RL3\omega$
39. The ripple factor for an L section filter is_____
- a) **$Y = 1/6\sqrt{2\omega 2LC}$**
b) $Y = 6\sqrt{2\omega 2LC}$
c) $Y = 6\sqrt{3\omega 2LC}$
d) $Y = 1/6\sqrt{3\omega 2LC}$
40. The output dc voltage of an LC filter is_____
- a) $V_{DC} = 2V_m/\pi + ID_{CR}$
b) $V_{DC} = V_m/\pi - ID_{CR}$
c) $V_{DC} = 2V_m/\pi - 2ID_{CR}$
d) **$V_{DC} = 2V_m/\pi - ID_{CR}$**
41. The rms value of ripple current for an L section filter is_____
- a) **$IRMS = \sqrt{2/3} * X_L * V_{DC}$**
b) $IRMS = \sqrt{2/3} * X_L * V_{DC}$
c) $IRMS = \sqrt{2/3} * X_L * V_{DC}$
d) $IRMS = \sqrt{2/3} * X_L * V_{DC}$
42. What makes the load in a choke filter to bypass harmonic components?
- a) **capacitor**
b) inductor
c) resistor
d) diodes
43. The ripple to heavy loads by a capacitor is_____
- a) high
b) depends on temperature
c) **low**
d) no ripple at all
44. In a choke L section filter_____
- a) the inductor and capacitor are connected across the load
b) **the inductor is connected in series and capacitor is connected across the load**
c) the inductor is connected across and capacitor is connected in series to the load
d) the inductor and capacitor are connected in series
45. What is the number of capacitors and inductors used in a CLC filter?
- a) 1, 2 respectively
b) **2, 1 respectively**
c) 1, 1 respectively
d) 2, 2 respectively
46. Major part of the filtering is done by the first capacitor in a CLC filter because
- a) **The capacitor offers a very low reactance to the ripple frequency**
b) The capacitor offers a very high reactance to the ripple frequency
c) The inductor offers a very low reactance to the ripple frequency
d) The inductor offers a very high reactance to the ripple frequency



3. Bipolar Junction Transistors

Position in Question Paper

Total Marks-26

Q.1. c) 2-Marks.

Q.1. e) 2-Marks.

Q.2. b) 4-Marks.

Q.2. d) 4-Marks.

Q.4. b) 4-Marks.

Q.4. c) 4-Marks

Q.6. c) 6-Marks

Descriptive Question

1. With reference to a BJT, explain the following terms in detail?

- Emitter Efficiency 4M
- Base Transportation Factor 3M
- Large signal current gain. 3M

2. Write the current components of PNP transistor and explain.

3. For a transistor the leakage current is $0.1\mu\text{A}$ in CB configuration, while it is 19mA when it is connected in CE configuration. Calculate α & β of the same transistor?

4. What is early effect? How does it modify the VI characteristics of a BJT? 5M

5. Describe the operation of a PNP BJT in common collector configuration? 5M

6. Draw the common collector transistor characteristics? 5M

7. With a neat diagram explain how a transistor acts as an amplifier? 5M

8. Explain the characteristics of CE configuration?

9. Compare CB, CE and CC configurations of BJT

10. Why transistor is considered as current controlled device?

11. Define thermal instability, what are the factors affecting the stability factor?



12. How self-bias circuit will eliminate the drawbacks in fixed bias circuit ?
13. Discuss the criteria of fixed operating point?
14. What is thermal runaway? What is the condition for thermal stability in CE configuration?
15. Derive the stability factor S in fixed bias circuit? What are the drawbacks of transistor fixed bias circuit?
16. Differentiate the bias stabilization and compensation techniques?
17. Mention the merits and demerits of collector to base feedback bias.
18. Differentiate between thermistor and sensistor compensation techniques?
19. What do you understand by DC & AC load line?
20. Define operating point Q of transistor.
21. Define stability factor S , S' , S'' .
22. What are the compensation techniques used for bias stability?
23. What is thermal runaway and thermal stability?



MCQ Questions:-

(Total number of Question=Marks*3= 18*3=54)

Note: Correct answer is marked with **bold**.

- Which of the following is not a part of a BJT?
 - Base
 - Collector
 - Emitter
 - None of the mentioned**
- The number of pn junctions in a BJT is/are
 - 1
 - 2**
 - 3
 - 4
- In which of the following modes can a BJT be used?
 - Cut-off mode
 - Active mode
 - Saturation mode
 - All of the mentioned**
- If a BJT is to be used as an amplifier, then it must operate in_____
 - Cut-off mode
 - Active mode**
 - Saturation mode
 - All of the mentioned
- If a BJT is to be used as a switch, it must operate in_____
 - Cut-off mode or active mode
 - Active Mode or saturation mode
 - Cut-off mode or saturation mode**
 - Cut-off mode or saturation mode or active mode
- In cut off mode
 - The base-emitter junction is F.B and emitter-collector junction is R.B
 - The base-emitter junction is F.B and emitter-collector junction is F.B
 - The base-emitter junction is R.B and emitter-collector junction is R.B**
 - The base-emitter junction R.B and emitter-collector junction is F.B
- On which of the following does the scale current not depends upon?
 - Effective width of the base
 - Charge of an electron
 - Electron diffusivity
 - Volume of the base-emitter junction**
- On which of the following does the collector current not depends upon?
 - Saturation current
 - Thermal voltage
 - Voltage difference between the base and emitter
 - None of the mentioned**



19. For the BJT to operate in active mode Collector-Base junction must be
- Heavily doped
 - Must reversed bias**
 - Must be forward bias
 - Lightly doped
20. Collector current (I_c) reaches zero when
- $V_{ce} = V_t \ln (I_{sc}/I)$**
 - $V_t = V_{ce} \ln (I_{sc}/I)$
 - $V_{ce} = V_t \ln (I/I_{sc})$
 - $V_{ce} = V_t \ln (I_{sc} + I/I)$
21. Which of the following condition is true for cut-off mode?
- The collector current I_s is zero**
 - The collector current is proportional to the base current
 - The base current is non zero
 - All of the mentioned
22. The potential difference between the base and the collector V_{cb} in a pnp transistor in saturation region is _____
- 0.2 V
 - 0.5V**
 - 0.2 V
 - 0.5 V
23. For a pnp transistor in the active region the value of V_{ce} is
- Less than 0.3V**
 - Less than 3V
 - Greater than 0.3V
 - Greater than 3V
24. Which of the following is true for a pnp transistor in active region?
- CB junction is reversed bias and the EB junction is forward bias**
 - CB junction is forward bias and the EB junction is forward bias
 - CB junction is forward bias and the EB junction is reverse bias
 - CB junction is reversed bias and the EB junction is reverse bias
25. Which of the following is true for a pnp transistor in saturation region?
- CB junction is reversed bias and the EB junction is forward bias
 - CB junction is forward bias and the EB junction is forward bias**
 - CB junction is forward bias and the EB junction is reverse bias
 - CB junction is reversed bias and the EB junction is reverse bias
26. Find the value of $R(E)$ to establish a dc emitter current of about 0.5 mA.
- 28.57 k Ω**
 - 57.04 k Ω
 - 114.08 k Ω
 - 228.16 k Ω
27. Find $R(C)$ to establish a dc collector voltage of about +5V.
- 5 k Ω
 - 10 k Ω
 - 15 k Ω
 - 20 k Ω**



28. For $R(L) = 10\text{ k}\Omega$ and transistor $R_o = 200\text{ k}\Omega$, determine the overall voltage gain.
- a) -21 V/V
b) -42 V/V
c) **-86 V/V**
d) -123 V/V
29. The advantages over the vacuum triode for a junction transistor is _____
- a) high power consumption
b) **high efficiency**
c) large size
d) less doping
30. What is the left hand section of a junction transistor called?
- a) base
b) collector
c) **emitter**
d) depletion region
31. In an NPN transistor, the arrow is pointed towards _____
- a) the collector
b) the base
c) depends on the configuration
d) **the emitter**
32. Which of the following is true in construction of a transistor?
- a) the collector dissipates lesser power
b) the emitter supplies minority carriers
c) **the collector is made physically larger than the emitter region**
d) the collector collects minority charge carriers
33. In the operation of an NPN transistor, the electrons cross which region?
- a) emitter region
b) the region where high depletion
c) the region where there is low depletion
d) **P type base region**
34. Which of the following are true for a PNP transistor?
- a) the emitter current is less than the collector current
b) **the collector current is less than the emitter current**
c) the electrons are majority charge carriers
d) the holes are the minority charge carriers
35. In the saturated region, the transistor acts like a _____
- a) poor transistor
b) amplifier
c) open switch
d) **closed switch**
36. When does the transistor act like an open switch?
- a) **cut off region**
b) inverted region
c) saturated region
d) active region



4. Field effect Transistors.

Position in Question Paper

Total Marks-18

- Q.1. b) 2-Marks.
- Q.1. d) 2-Marks.
- Q.3. c) 4-Marks.
- Q.4. d) 4-Marks.
- Q.5. a) 6-Marks

Descriptive Questions

1. Detail the construction of an n-channel MOSFET of depletion type. Draw and explain its Characteristics?
2. Explain the construction and principle of operation of n-channel JFET.
3. Define the JFET Volt-Ampere Characteristics.
4. Draw and explain construction and operation of Enhancement mode MOSFET with its Characteristics?
5. Draw and explain construction and operation of Enhancement mode MOSFET with its Characteristics?
6. Draw the basic circuit and small signal model of Common drain FET amplifier.
7. Derive the expression for input and output impedance of common drain amplifier using FET?
8. Explain the small signal equivalent circuit of Common Gate amplifier.
9. Explain the construction of n channel JFET
10. Give classification of FET. Draw the symbol of each type.



MCQ Questions:-

(Total number of Question=Marks*3= 12*3=36)

Note: Correct answer is marked with **bold**.

- Ideal maximum voltage for common drain amplifier is _____
a) 0
b) 1
c) 0.5
d) 2
- If a certain drain JFET has a transconductance of 4ms. And has external drain resistance of 1.5 ohm than ideal voltage gain will be _____
a) 4
c) 6
b) 5
d) 8
- Input resistance of common gate of the amplifier is _____
a) zero
c) extremely low
b) infinity
d) extremely high
- A FET circuit has a transconductance of 2500 μ seconds and drain resistance equals to 10Kohms than voltage gain will be _____
a) 20
b) 25
c) 30
d) 35
- Voltage gain of common drain amplifier is always slightly less than _____
a) 0.5
b) 1
c) 1.5
d) 2
- A common gate amplifier has _____
a) low input impedance
b) high input impedance
c) infinite input impedance
d) no impedance
- D-MOSFET in case of common source amplifier can operate with gate to source voltage zero at _____
a) Peak positive point
c) Q point
b) Peak negative point
d) Origin
- A common source amplifier has _____
a) no source resistance
b) no drain resistance
c) no gate resistance
d) low input impedance
- The drain of FET is analogous to BJT
a) collector
b) emitter
c) base
d) drain



10. Input signal of common drain amplifier is applied to the gate through _____
- a) input resistor
 - b) coupling capacitor**
 - c) output capacitor
 - d) transformer
11. For NMOS transistor which of the following is not true?
- a) The substrate is of p-type semiconductor
 - b) Inversion layer or induced channel is of n type
 - c) Threshold voltage is negative**
 - d) None of the mentioned
12. Process transconductance parameter is directly proportional to
- a) Electron mobility only
 - b) (Electron mobility)⁻¹ only
 - c) Oxide capacitance only
 - d) Product of capacitance, electron mobility**
13. The SI Units of the Process transconductance Parameter (k') is
- a) V²/A
 - b) A/V²**
 - c) V/A
 - d) A/V
14. Aspect ratio of the MOSFET has the units of
- a) No units**
 - b) m
 - c) m²
 - d) m⁻¹
15. The MOSFET transconductance parameter is the product of
- a) Process transconductance and inverse of aspect ratio
 - b) Inverse of Process transconductance and aspect ratio
 - c) Inverse of Process transconductance and inverse of aspect ratio
 - d) Process transconductance and aspect ratio**
16. If a MOSFET is to be used in the making of an amplifier then it work_
- a) Cut-off region
 - b) Triode region
 - c) Saturation region**
 - d) Both cut-off and triode region
17. For MOSFET is to be used as a switch then it must operate in
- a) Cut-off region
 - b) Triode region
 - c) Saturation region
 - d) Both cut-off and triode region**
18. In the saturation region of the MOSFET the saturation current is
- a) Independent of the voltage difference between the source and the drain**
 - b) Depends directly on the voltage difference between the source and the drain
 - c) Depends directly on the overdriving voltage
 - d) Depends directly on the voltage supplied to the gate terminal



5. Regulators and Power Supply.

Position in Question Paper

Total Marks-14

Q.1. f) 2-Marks.

Q.2. c) 4-Marks.

Q.3. d) 4-Marks.

Q.4. e) 4-Marks.

Descriptive Questions

1. Explain with a neat diagram, shunt voltage regulator.
2. Explain with a neat diagram, series voltage regulator.
3. Distinguish between unregulated & regulated power supply.
4. Draw the block diagram of regulated power supply, explain each block in short.
5. Explain in brief-Load & Line regulation.
6. Write a short note on – Three terminal voltage regulator
7. List basic elements of a power supply. Distinguish between regulated & unregulated power
8. Calculate percentage load regulation for a voltage regulator giving 10.2V & 10V outputs at no load & full load conditions respectively
9. Explain with the help of a block diagram three terminal IC voltage regulator.



Maratha Vidya Prasarak Samaj's
Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

-
- 10.** Draw the functional block diagram of three terminal voltage regulator & explain brief.
 - 11.** Explain with neat circuit diagram dual power supply using IC7815 and IC7915.
 - 12.** Define line regulation & load regulation. Elaborate the difference between series shunt type voltage regulation.
 - 13.** Explain the working of shunt regulator. What are advantages over a series regulator?



MCQ Questions:-

(Total number of Question=Marks*3= 10*3=30)

Note: Correct answer is marked with **bold**.

1. What is IC 723?
 - a) **A voltage regulator**
 - b) A full-wave rectifier
 - c) A half-wave rectifier
 - d) A clipper
2. What is line regulation?
 - a) The process of keeping Zener diode voltage constant inspite of changes in AC s/p
 - b) The process of keeping load voltage constant irrespective of the fluctuation in AC supply or the line voltage**
 - c) The process of keeping load voltage constant irrespective of fluctuation in IL
 - d) The process of keeping Zener current constant irrespective of fluctuation in AC supply
3. Given that V_1 varies from 20V to 50V, the diode breakdown voltage is 5V, the knee current is 1mA and the current is 9 mA across R_1 , find the maximum value of R_2 .
 - a) 4500 Ω
 - b) 1500 Ω**
 - c) 2000 Ω
 - d) 5000 Ω
4. Which of these is a not drawback of Zener diode shunt regulator?
 - a) The output voltage is fixed
 - b) The output voltage can vary with temperature
 - c) Variation in load current needs to be minimal
 - d) It is difficult to design**
5. In a power supply, the output voltage can vary due to multiple reasons. Which of these is not true if it is found that the output voltage is constant?
 - a) The voltage stability factor is very high**
 - b) The output resistance is zero
 - c) The temperature coefficient is zero
 - d) The voltage stability factor is very small
6. The breakdown voltage of the Zener is 5V. β for the transistor is 100. $R_1=10k\Omega$ $R_2=90k\Omega$, $R_3=30k\Omega$, $R_4=50k\Omega$. Calculate the total output voltage.
 - a) 20V**
 - b) 30V
 - c) 5V
 - d) 50V



7. Given that the Zener diode breakdown voltage is 5V, the source voltage is 15V, the output voltage is 10V, $R_4 = 2k\Omega$, $\beta=99$, $R_1=2k\Omega$. Find I_L
- a) 5.05 mA
 - b) 4.95 mA**
 - c) 3.33 mA
 - d) 0
8. What is not related to a transistorized series regulator?
- a) The output can be varied by using a variable resistor
 - b) The output is independent of temperature
 - c) The overload and short circuit protection is not required**
 - d) The circuit has negative feedback responsible for regulation
9. What is the output of the IC 7924?
- a) 12V
 - b) -12V
 - c) 24V
 - d) -24V**
10. In the IC 7805, what is the minimum input voltage for proper functioning?
- a) 5V**
 - b) 6V
 - c) 7V
 - d) 8V
11. Which is not considered as a linear voltage regulator?
- a) Fixed output voltage regulator
 - b) Adjustable output volt regulator
 - c) **Switching regulator**
 - d) Special regulator
12. What is the dropout voltage in a three terminal IC regulator?
- a) $|V_{in}| \geq |V_o| + 2v$**
 - b) $|V_{in}| < |V_o| - 2v$
 - c) $|V_{in}| = |V_o|$
 - d) $|V_{in}| \leq |V_o|$
13. To get a maximum output current, IC regulation are provided with
- a) Radiation source
 - b) Heat sink**
 - c) Peak detector
 - d) None of the mentioned
14. Which type of regulator is considered more efficient?
- a) All of the mentioned
 - b) Special regulator
 - c) Fixed output regulator
 - d) Switching regulator**
15. State the reason for thermal shutdown of IC regulator?
- a) Spikes in temperature
 - b) Decrease in temperature
 - c) Fluctuation in temperature
 - d) Increase in temperature**
16. The change in output voltage for the corresponding change in load current in a 7805 IC regulator is defined
- a) All of the mentioned
 - b) Line regulation
 - c) **Load regulation**
 - d) Input regulation



17. How the avg temp coef of output voltage expre in fixed voltage regulator?
- a) **miilivolts/oC**
 - b) miilivoltsoC
 - c) None of the mentioned
 - d) oC/ miilivolts
18. Compute the input voltage of 7805c voltage regulator with a current Source that will deliver a 0.725A current to 65Ω , 10w load
- a) $V_{in} = 84v$
 - b) $V_{in} = 34v$
 - c) **$V_{in} = 54v$**
 - d) $V_{in} = 64v$
19. Which of the following is not a characteristic of adjustable voltage regulators?
- a) **Non-versatile**
 - b) Better performance
 - c) Increased reliability
 - d) None of the mentioned
20. In an unregulated power supply, if load current increases, the output voltage
- a) **Remains the same**
 - b) Decreases
 - c) Increases
 - d) None of the above
21. Voltage regulators require
- a) Only line regulation
 - b) Only load regulation
 - c) A constant load
 - d) **Load and line regulation**
22. What type of regulators offer inherent short-circuit protection?
- a) **Shunt regulators**
 - b) Series regulators
 - c) Three-terminal regulators
 - d) Switching regulators
23. Voltage regulators keep a constantoutput voltage when the input or load varies within limits
- a) **DC**
 - b) AC
 - c) ripple
 - d) None
24. The V_o of a regulated power supply is affected by which of the following factors
- a) Input voltage
 - b) Load current
 - c) Temperature
 - d) **All the above**
25. Series pass transistor always operates in the_ region in a linear IC voltage regulator
- a) **Active**
 - b) Saturation
 - c) Cut-off
 - d) All of theses
26. Find the difference between output current having a load of 100Ω and 120Ω 7805 IC regulator. Consider the following specification: $V_L = 5v$; $V_R = 350mA$
- a) **8.4mA**
 - b) 7mA
 - c) 9mA
 - d) 3.4mA



Maratha Vidya Prasarak Samaj's
Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

RSM POLY Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

27. The 7912 regulator IC provides _____ .
- a) 5 V
 - b) -5 V
 - c) 12 V
 - d) **-12 V**
28. _____ Acts as a regulator
- a) **Zener diode**
 - b) Photodiode
 - c) Tunnel diode
 - d) None
29. A power supply which has voltage regulation of ... is unregulated p/s
- a) 0 %
 - b) 5 %
 - c). **10 %**
 - d) 8%
30. Commercial power supplies have voltage regulation ...
- a) of 10%
 - b) of 15%
 - c) of 25%
 - d) **within 1%**