



Maratha Vidya Prasarak Samaj's

Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

Subject:- Linear Integrated Circuits.
(22423)



SYLLABUS

Chapter No.	Name of Unit	Marks With Option
1	Fundamental of Operational Amplifiers	12
2	Applications of Operational Amplifiers	18
3	Linear Applications of Op-Amp.	26
4	Filters and Oscillators.	26
5	Specialized IC Applications.	20
Total Marks :-		102



BOARD THEORY

PAPER PATTERN

FOR LIC (22423)

Q.1		Attempt any FIVE	5*2=10
	a)	Fundamental of Operational Amplifiers	
	b)	Applications of Operational Amplifiers	
	c)	Filters and Oscillators	
	d)	Fundamental of Operational Amplifiers	
	e)	Specialized IC Applications.	
	f)	Filters and Oscillators	
	g)	Filters and Oscillators	
Q.2		Attempt any THREE	3*4=12
	a)	Fundamental of Operational Amplifiers	
	b)	Filters and Oscillators	
	c)	Specialized IC Applications	
	d)	Applications of Operational Amplifiers	
Q.3		Attempt any THREE	3*4=12
	a)	Fundamental of Operational Amplifiers	



Maratha Vidya Prasarak Samaj's
Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

	b)	Linear Applications of Op-Amp
	c)	Filters and Oscillators
	d)	Specialized IC Applications
Q.4		Attempt any FOUR 3*4=12
	a)	Linear Applications of Op-Amp
	b)	Fundamental of Operational Amplifiers
	c)	Applications of Operational Amplifiers
	d)	Fundamental of Operational Amplifiers
	e)	Specialized IC Applications
Q.5		Attempt any TWO 2*6=12
	a)	Linear Applications of Op-Amp
	b)	Filters and Oscillators
	c)	Linear Applications of Op-Amp
Q.6		Attempt any TWO 2*6=12
	a)	Applications of Operational Amplifiers
	b)	Linear Applications of Op-Amp
	c)	Filters and Oscillators



CLASS TEST - I

PAPER PATTERN

COURSE: - Linear Integrated Circuits (22423)

PROGRAMME: - E&TC Engineering

Syllabus :-

Unit No.	Name of the Unit	Course Outcome (CO)
1	Fundamental of Operational Amplifiers	CO-423.1
2	Applications of Operational Amplifiers	CO-423.2
3	Linear Applications of Op-Amp	CO-423.3

Q.1	Attempt any FOUR 4*2=8Marks	Course Outcome (CO)
a)	Fundamental of Operational Amplifiers	CO-423.1
b)	Fundamental of Operational Amplifiers	CO-423.1
c)	Linear Applications of Op-Amp	CO-423.3
d)	Applications of Operational Amplifiers	CO-423.2
e)	Applications of Operational Amplifiers	CO-423.2
f)	Linear Applications of Op-Amp	CO-423.3
Q.2	Attempt any THREE 3*4=12 Marks	
a)	Linear Applications of Op-Amp	CO-423.3
b)	Linear Applications of Op-Amp	CO-423.3
c)	Fundamental of Operational Amplifiers	CO-423.1
d)	Fundamental of Operational Amplifiers	CO-423.1
e)	Applications of Operational Amplifiers	CO-423.2
f)	Applications of Operational Amplifiers	CO-423.2



CLASS TEST - II

PAPER PATTERN

COURSE: - Linear Integrated Circuits (22423)

PROGRAMME: - E&TC Engineering

Syllabus :-

Unit	Name of the Unit	Course Outcome(CO)
3	Linear Applications of Op-Amp.	CO-423.3
4	Filters and Oscillators.	CO-423.4
5	Specialized IC Applications.	CO-423.5

Q.1	Attempt any FOUR	4*2=8Marks	Course Outcome (CO)
a)	Linear Applications of Op-Amp.		CO-423.3
b)	Filters and Oscillators		CO-423.4
c)	Filters and Oscillators		CO-423.4
d)	Specialized IC Applications.		CO-423.5
e)	Specialized IC Applications.		CO-423.5
f)	Linear Applications of Op-Amp.		CO-423.3
Q.2	Attempt any THREE	3*4=12 Marks	
a)	Linear Applications of Op-Amp.		CO-423.3
b)	Linear Applications of Op-Amp.		CO-423.3
c)	Specialized IC Applications.		CO-423.5
d)	Specialized IC Applications.		CO-423.5
e)	Filters and Oscillators		CO-423.4
f)	Filters and Oscillators		CO-423.4



COURSE OUTCOME

(CO)

COURSE: - Linear Integrated Circuits (22423)

PROGRAMME: - E&TC Engineering

CO.NO	Course Outcome
CO-423.1	Use OP-Amp in linear electronic circuits.
CO-423.2	Use Various configurations of OP-Amp for different applications.
CO-423.3	Troubleshoot various linear applications of op-amp for given specifications.
CO-423.4	Maintain Filters and Oscillators used in various electronic circuits.
CO-423.5	Troubleshoot specified applications using various linear ICs.



1. Applications of OP-Amp

Position in Question Paper

Total Marks-12

Q.1. a) 2-Marks.

Q.1. d) 2-Marks

Q.2. a) 4-Marks.

Q.3. a) 4-Marks.

Descriptive Question

1. What is Op-Amp? State Advantages of OP-Amp.
2. Draw Pin diagram and equivalent Ckt.
3. Define 1. I/P offset Voltage 2. CMRR
4. Define 1. O/P offset voltage 2. SVRR
5. Draw and explain the block diagram of OP-Amp.
6. Draw the ideal and Practical transfer characteristics of Op-amp.
7. State the function of Level shifter block of op-amp.
8. Compare the characteristics values of op-amp IC741 and ideal op-amp.
9. Draw Ideal and Practical Characteristics of Op-amp.
10. Draw and explain the block diagram of op-amp.
11. What is the use of level shifter stage? Draw its circuit diagram.



MCQ Questions:-

(Total number of Question=Marks*3=8*3=24)

Note: Correct answer is marked with **bold**.

1. A differential amplifier
 - a) is a part of an Op-amp
 - b) has one input and one output
 - c) has two outputs
 - d) answers (1) and (2)**
2. When a differential amplifier is operated single-ended,
 - a) the output is grounded
 - b) one input is grounded and signal is applied to the other**
 - c) both inputs are connected together
 - d) the output is not inverted
3. In differential-mode,
 - a) opposite polarity signals are applied to the inputs
 - b) the gain is one**
 - c) the outputs are of different amplitudes
 - d) only one supply voltage is used
4. In the common mode,
 - a) both inputs are grounded**
 - b) the outputs are connected together
 - c) an identical signal appears on both the inputs
 - d) the output signal are in-phase
5. The common-mode gain is.....
 - a) very high
 - b) very low**
 - c) always unity
 - d) unpredictable
6. The differential gain is
 - a) very high**
 - b) very low
 - c) dependent on input voltage
 - d) about 100
7. If $A_{DM} = 3500$ and $A_{CM} = 0.35$, the CMRR is
 - a) 1225
 - b) 10,000
 - c) 80 dB
 - d) answers (1) and (3)**



8. With zero volts on both inputs, an OP-amp ideally should have an output..
- a) equal to the positive supply voltage
 - b) equal to the negative supply voltage
 - c) equal to zero**
 - d) equal to CMRR
9. Of the values listed, the most realistic value for open-loop voltage gain of an OP-amp is
- a) 1
 - b) 2000
 - c) 80 dB
 - d) 100,000**
10. A certain OP-amp has bias currents of 50 μA . The input offset current is
- a) 700 nA**
 - b) 99.3 μA
 - c) 49.7 μA
 - d) none of these
11. The output of a particular Op-amp increases 8V in 12 μs . The slew rate is
- a) 90 V/ μs
 - b) 0.67 V/ μs**
 - c) 1.5 V/ μs
 - d) none of th
12. For an Op-amp with negative feedback, the output is
- a) equal to the input
 - b) increased
 - c) feed back to the inverting input**
 - d) feed back to the noninverting input
13. The use of negative feedback
- a) reduces the voltage gain of an Op-amp
 - b) makes the Op-amp oscillate
 - c) makes linear operation possible
 - d) answers (1) and (2)**
14. A certain noninverting amplifier has R_i of 1 k Ω and R_f of 100 k Ω . The closed-loop voltage gain is
- a) 100,000
 - b) 1000
 - c) 101**
 - d) 100
15. If the feedback resistor is open, the voltage gain
- a) increases**
 - b) decreases
 - c) is not affected
 - d) depends on R_i



16. The Op-amp can amplify

- a) a.c. signals only
- b) d.c. signals only
- c) **both a.c. and d.c. signals**
- d) neither d.c. nor a.c. signals

17. The input offset current equals the

- a) **difference between two base currents**
- b) average of two base currents
- c) collector current divided by current gain
- d) none of these

18. The node voltage at the top of the tail resistor is close to

- a) collector supply voltage
- b) **zero**
- c) emitter supply voltage
- d) tail current times base

19. The differential voltage gain of a differential amplifier is equal to R_C divided by

- a) r'_e
- b) $r'_e/2$
- c) **$2r'_e$**
- d) R_E

20. A common-mode signal is applied to

- a) the noninverting input
- b) the inverting input
- c) **both inputs**
- d) top of the tail resistor

21. The common-mode voltage gain is

- a) **smaller than differential voltage gain**
- b) equal to differential voltage gain
- c) greater than differential voltage gain
- d) none of the above

22. The input stage of an Op-amp is usually a

- a) **differential amplifier**
- b) class B push-pull amplifier
- c) CE amplifier
- d) ampified amplifier

23. Current cannot flow to ground through

- a) a mechanical ground
- b) an a.c. ground
- c) **a virtual ground**
- d) an ordinary ground



Maratha Vidya Prasarak Samaj's
Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

RSM POLY Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

24. The tail current in a differential amplifier equals

- a) difference between two emitter currents
- b) sum of two emitter currents**
- c) collector current divided by current gain
- d) collector voltage divided by collector resistance



2. Applications of OP-Amp

Position in Question Paper

Total Marks-18

Q.1. b) 2-Marks.

Q.2. c) 4-Marks.

Q.3. b) 4-Marks.

Q.3. d) 4-Marks.

Q.4. d) 4-Marks.

Descriptive Question

1. Explain Virtual short Concept.
2. Draw and derive the o/p expression for Inverting Adder.
3. Draw and derive the o/p expression for Non-inverting Adder
4. State the need of closed loop configuration for an op-amp.
5. Explain virtual ground concept of op-amp
6. Draw circuit diagram of basic differentiator.
7. Draw the ckt. Diagram of Inverter
8. Draw the ckt. Diagram of unity gain amplifier.
9. Draw the ckt. Diagram of Inverting amplifier, and derive its o/p expression.
10. Draw the ckt. Diagram of Non- Inverting amplifier, and derive its o/p expression.
11. Draw the ckt diagram of basic differentiator and derive its o/p expression
12. Draw the ckt diagram of basic Integrator and Derive e its o/p expression



MCQ Question

(Total number of Question=Marks*3=12*3=36)

Note: Correct answer is marked with **bold**.

- The opamp in the Inverting circuit is in _____
 - Linear region**
 - Saturation
 - Cut-off region
 - Non-linear region
- In an Inv Amplifier circuit, the output voltage v_o is expressed as a function of ____
 - Input current
 - Output current
 - Source voltage**
 - Source current
- The other name for Gain is _____
 - Scaling factor**
 - Output
 - Amplifying factor
 - Scaling level
- If $V_{CC} = 12V$ and $v_s = 1mV$, then R_f/R_s is _____
 - >12000
 - <12000**
 - 12000
 - 1
- In the expression $v_o = -A_{vnl} v_i$, A is called _____
 - Closed loop gain
 - Closed loop fault
 - Open loop fault
 - Open loop gain**
- The circuits of an inv and Non-Inv amplifying comprises of _ & _ resistors.
 - 3, 2
 - 2, 3**
 - 2, 2
 - 3, 3
- The condition for a Non-inv ampl ckt to operate in linear region _
 - $(R_s + R_f)/R_s < |V_{CC}/v_g|$**
 - $(R_s + R_f)/R_s \neq |V_{CC}/v_g|$
 - $(R_s + R_f)/R_s > |V_{CC}/v_g|$
 - $(R_s + R_f)/R_s = |V_{CC}/v_g|$
- If $R_s = 3\Omega$, $R_f = 6\Omega$ then the relation bet v_o and v_g in case of a Non-Inv ckt.
 - $v_o = 9v_g$
 - $v_o = 6v_g$
 - $v_o = 3v_g$**
 - $v_o = v_g$



28. Find out the gain value by which each input of averaging amplifier is amplified ?

- a) 0.5
- b) **0.25**
- c) 1
- d) 2

29. 3v, 5v and 7v are the 3 input voltage applied to the inv i/p of avg amplifier, V_o ?

- a) **-5v**
- b) -10v
- c) -15v
- d) -20v

30. Which of the following electrical chara is not exhibited by an ideal op-amp?

- a) Infinite voltage gain
- b) Infinite bandwidth
- c) **Infinite output resistance**
- d) Infinite slew rate

31. An ideal op-amp requires infinite bandwidth because

- a) **Signals can be amplified without attenuation**
- b) Output common-mode noise voltage is zero
- c) Output voltage occurs simultaneously with input voltage changes
- d) Output can drive infinite number of device

32. Ideal op-amp has infinite voltage gain because

- a) To control the output voltage
- b) **To obtain finite o/p voltage**
- c) To receive zero noise output voltage
- d) None of the mentioned

33. Find the output voltage of an ideal op-amp. If V_1 and V_2 are the two input

- a) $V_O = V_1 - V_2$
- b) **$V_O = A \times (V_1 - V_2)$**
- c) $V_O = A \times (V_1 + V_2)$
- d) $V_O = V_1 \times V_2$

34. How will be the output voltage obtained for an ideal op-amp?

- a) **Amplifies the difference between the two input voltages**
- b) Amplifies individual voltages input voltages
- c) Amplifies products of two input voltage
- d) None of the mentioned

35. Which is not the ideal characteristic of an op-amp?

- a) **Input Resistance $\rightarrow 0$**
- b) Output impedance $\rightarrow 0$
- c) Bandwidth $\rightarrow \infty$
- d) Open loop voltage gain $\rightarrow \infty$

36. Find the I/P vtg of an ideal op-amp. It's I/P and o/p are 2v & 12v. ($A_v = 3$)

- a) 8v
- b) 4v
- c) -4v
- d) **-2v**



3. Linear Applications of op-Amp

Position in Question Paper

Total Marks-26

Q.1. c) 2-Marks.

Q.1. d) 2-Marks.

Q.2. d) 4-Marks.

Q.2 e) 4 Marks

Q.3. a) 4-Marks.

Q.5. b) 6-Marks.

Q.4. e) 4-Marks

Descriptive Question

1. State the need of signal conditioning.
2. Draw and explain temperature compensated logarithmic amplifier using op-amp.
3. Draw the circuit diagram of I. A. using three op – amp and write its output equation.
4. Explain current to voltage converter. Write its applications. 24) Draw and explain Window detector.
5. Compare between Schmitt Trigger and Comparator.
6. Define UTP, LTP, Hysteresis with respect to Schmitt trigger
7. Draw the circuit of a V-I converter and derive an expression for the output current in terms of input voltage.
8. Draw the diagram of log amplifier using op-amp. Derive the expression for its output voltage.
9. Draw the sample and hold circuit using op-amp. Explain its working and show input and output waveform.



Maratha Vidya Prasarak Samaj's
Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

-
10. Draw the neat diagram of analog multiplier using log-antilog amplifiers and explain its operation.
 11. Draw and explain zero crossing detector with i/p and o/p waveform.
 12. Draw and explain Inverting Schmitt Trigger using IC 741. 33) With suitable circuit diagram explain Active peak detector
 13. Draw I-V Converter using Op-amp .Derive the expression for its output voltage.



MCQ Questions:-

(Total number of Question=Marks*3= 20*3=60)

Note: Correct answer is marked with **bold**.

1. What are the features of instrumentation amplifier?
 - a) Low noise
 - b) High gain accuracy
 - c) Low thermal and time drift
 - d) All of the mentioned**
2. What instrument is used to amplify output signal of transducer?
 - a) Peaking amplifier
 - b) Instrumentation amplifier**
 - c) Differential amplifier
 - d) Bridge amplifier
3. General purpose op-amps are used in applications as
 - a) Instrumentation amplifier
 - b) Differential instrumentation amplifier**
 - c) Inverting instrumentation amplifier
 - d) Non-inverting instrumentation amplifier
4. Voltage to current converter is also called as
 - a) Current series positive feedback amplifier
 - b) Voltage series negative feedback amplifier
 - c) Current series negative feedback amplifier**
 - d) Voltage series positive feedback amplifier
5. Which of the following application uses voltage to current converter?
 - a) Low voltage dc and ac voltmeter
 - b) Diode match finding
 - c) Light emitting diode
 - d) All of the mentioned**
6. The op-amp in low voltage DC voltmeter cannot be nullified due to
 - a) D'Arsonval meter movement**
 - b) Offset voltage compensating
 - c) Selection of switch
 - d) Gain of amplifier
7. How to modify a low voltage DC voltmeter to low voltage ac voltmeter
 - a) Add a full wave rectifier in the feedback loop**
 - b) Add a half wave rectifier in the feedback loop
 - c) Add a square wave rectifier in the feedback loop
 - d) Add a sine wave rectifier in the feedback loop
8. What is the alternate method to measure the values of non-sinusoidal waveform other than ac voltmeter?
 - a) Clipper
 - b) Clamper
 - c) Peak detector**
 - d) Comparator



9. State the condition satisfied by peak detector for proper operation of circuit.
- a) $CRd \leq T/10$ and $CRL \geq 10T$ c) $CRd \geq T/10$ and $CRL \leq 10T$
b) $CRd \leq 10T$ and $CRL \geq T/10$ d) $CRd \geq 10T$ and $CRL \leq T/10$
10. The resistor in the peak detector are used to
- a) To maintain proper operation c) To get shaped non-sinusoidal waveform
b) **Protect op-amp from damage** d) None of the mentioned
11. How the recovery time of the op-amp is reduced?
- a) **Diode is connected at the output of amplifier**
b) Load resistor
c) Forward biased diode resistor
d) Discharge capacitor
12. In the S/H Ckt, the period during which the voltage across capacitor $= i/p \text{ vtg}$
- a) **Sample period** c) Delay period
b) Hold period d) Charging period
13. During which period the op-amps output of sample and hold circuits is processed?
- a) Delay period c) Sample period
b) Sample and hold period **d) Hold period**
14. Which IC is mostly preferred for sample and hold circuit?
- a) $\mu 771$ **c) LF398**
b) IC741 d) $\mu 351$
15. Sample and hold circuit are used in__
- a) Analog to Digital modulation c) Pulse position modulation
b) Digital to analog modulation **d) All of the mentioned**
16. The value of input and reference voltage a comparator can be named as
- a) Voltage follower c) Schmitt trigger
b) Digital to analog converter **d) Voltage level detector**
17. Why clamp diodes are used in comparator?
- a) To reduce output offset voltage c) To reduce input offset current
b) To increase gain of op-amp **d) To protect op-amp from damage**
18. How the op-amp comparator should be chosen to get higher speed of operation?
- a) Large gain **c) Wider bandwidth**
b) High slew rate d) None of the mentioned



19. How to obtain high rate of accuracy in comparator?
- a) Input offset
 - b) High voltage gain
 - c) High CMRR
 - d) All of the mentioned**
20. Output voltage swing of the op-amp comparator within specific limits?
- a) External resistors or diodes
 - b) **External zeners or diodes**
 - c) External capacitors or diodes are used
 - d) External inductors or diodes are used
21. Zero crossing detectors is also called as
- a) Square to sine wave generator
 - b) **Sine to square wave generator**
 - c) Sine to triangular wave generator
 - d) All of the mentioned
22. What is the drawback in zero crossing detectors?
- a) Low frequency signal and noise at output terminal
 - b) High frequency signal and noise at input terminal
 - c) Low frequency signal and noise at input terminal**
 - d) High frequency signal and noise at output terminal
23. State a method to overcome the drawback of zero crossing detectors?
- a) Increasing input voltage
 - b) **Use of positive feedback**
 - c) Connect a compensating network
 - d) None of the mentioned
24. Name the comparator that helps to find unknown input.
- a) Time marker generator
 - b) Zero crossing detectors
 - c) Phase meter
 - d) Window detector**
25. Following is used to increase phase angle between different voltages?
- a) Phase detector**
 - b) Window detector
 - c) Zero crossing detector
 - d) None of the mentioned
26. Which circuit converts irregularly shaped waveform to regular shaped waveforms?
- a) Schmitt trigger**
 - b) Voltage limiter
 - c) Comparator
 - d) None of the mentioned
27. If the threshold voltages are made longer than the noise voltages in Schmitt trigger?
- a) All the mentioned
 - b) Enhance the output signal
 - c) Reduce the transition
 - d) Eliminate false output transition**
28. To a Schmitt trigger in non-inverting confi. triangular wave of 1Vp is applied. What will be the output waveform, if the upper and lower threshold voltages are 0.25V?
- a) Square waveform**
 - b) Pulse waveform
 - c) Sawtooth waveform
 - d) Cannot be determined



29. In which configuration a dead band condition occurs in schmitt trigger__
- a) Differential amplifier with positive feedback
 - b) Voltage follower with positive feedback
 - c) Comparator with positive feedback**
 - d) None of the mentioned
30. Which of the following functions does the antilog computation required to perform continuously with log-amps?
- a) $\ln(x)$
 - b) $\log(x)$
 - c) $\sinh(x)$
 - d) All of the mentioned**
31. How to provide saturation current and temperature compensation in log-amp?
- a) Applying reference voltage alone to two different log-amps
 - b) Applying input and reference voltage to same log-amps
 - c) Applying input and reference voltage to separate log-amps**
 - d) None of the mentioned
32. The input voltage, 6v and reference voltage, 4 v are applied to a log-amp with saturation current and temperature compensation. Find the output voltage of the log-amp?
- a) $6.314(kT/q)v$
 - b) $0.597(kT/q)v$
 - c) $0.405(kT/q)v$**
 - d) $1.214(kT/q)v$
33. An antilog amplifier has a _____ in series with the input.
- a) BJT
 - b) diode
 - c) diode or BJT**
 - d) resistor
34. A log amplifier may use the _____ junction of a BJT in the feedback loop.
- a) base-collector
 - b) base-emitter
 - c) emitter-collector**
 - d) emitter-ground
34. Instrumentation amplifiers are normally used to measure
- a) small differential signal voltages.
 - b) signals superimposed on a common-mode voltage often much larger than the
 - c) both of the above**
 - d) none of the above
35. The log of a number is the
- a) base to which the power must be raised to get that number.
 - b) power to which the base must be raised to get that number.**
 - c) base of that number.
 - d) power of that number.



36. What is a key characteristic of an instrumentation amplifier?
- a) **high CMRR**
 - b) high output offset
 - c) high output impedance
 - d) none of the above
37. A basic _____ amplifier is formed by three op-amps and seven resistors.
- a) **instrumentation**
 - b) isolation
 - c) log
 - d) antilog
38. The voltage gain of a basic instrumentation amplifier is set by a(n)
- a) diode.
 - b) capacitor.
 - c) **resistor.**
 - d) inductor.
39. A log amplifier has _____ in the feedback loop.
- a) a diode
 - b) a BJT
 - c) a resistor
 - d) **either a diode or a BJT**
40. The process known as signal compression is used with a(n) _____ amplifier.
- a) **log**
 - b) antilog
 - c) instrumentation
 - d) isolation
40. Zero crossing detector circuit plays a crucial role in conversion of input sine wave into a perfect _____ at its output.
- a) triangular wave
 - b) **square wave**
 - c) saw-tooth wave
 - d) pulse wave
41. For reducing the effects of input offset in comparator, what would be the possible value of input offset voltage?
- a. **Low**
 - b. Moderate
 - c. High
 - d. None of the above
42. Zero crossing detector circuit plays a crucial role in conversion of input sine wave into a perfect _____ at its output.
- a) triangular wave
 - b) **square wave**
 - c) saw-tooth wave
 - d) pulse wave
43. For an ideal comparator, what should be the value of the response time?
- a) **Zero**
 - b) Unity
 - c) Infinite
 - d) Unpredictable
44. Which parameter/s is/are used to indicate the speed of a comparator?
- a) Response Time
 - b) Propagation Delay
 - c) **Both a and b**
 - d) None of the above



45. For a temperature controller circuit comprising instrumentation amplifier?
which among the following is adopted as a temperature?
a) **Thermistor** c) Thyristor
b) Sensistor d) Thermocouple
46. Which among the following is/are the requirement/s of an instrumentation amplifier?
a) High slew rate c) High CMRR
b) High input resistance d) **All of the above**
47. Which among the following is a nonlinear application of op-amp?
a) V to I converter c) **Precision rectifier**
b) Comparator d) Instrumentation amplifier
48. In a nonlinear op-amp circuit, the
a) Op amp never saturates c) Output shape is the same
b) **Feedback never opened** d) Op amp may saturate
49. To detect when the input is greater than a particular value, use a
a) **Comparator** c) Limiter
b) Clamper d) Relaxation oscillator
50. The voltage out of a Schmitt trigger is
a) A low voltage c) **Either a low or a high voltage**
b) A high voltage d) A sine wave
51. If the input is a rectangular pulse, the output of an integrator is a
a) Sine wave c) **Ramp**
b) Square wave d) Rectangular pulse
52. When a large sine wave drives a Schmitt trigger, the output is a
a) **Rectangular wave** c) Rectified sine wave
b) Triangular wave d) Series of ramps
53. If pulse width decreases and the period stays the same, the duty cycle
a) **Decreases** c) Increases
b) Stays the same d) Is zero
54. The output of a relaxation oscillator is a
a) Sine wave c) Ramp
b) **Square wave** d) Spike



4. Filters and Oscillators.

Position in Question Paper

Total Marks-26

Q.1. e) 2-Marks.

Q.1. f) 2-Marks.

Q.1. g) 2-Marks.

Q.3. c) 4-Marks.

Q.4. a) 4-Marks.

Q.5. b) 6-Marks

Q.6. c) 6-Marks

Descriptive Questions

1. Give the classification of filters.
2. Define Roll of Rate and order of filter.
3. Define Bandwidth and cut off frequency
4. Define Pass band and stop band.
5. Draw ideal frequency response of filters.
6. Draw frequency response of High pass Filter.
7. State the key characteristics of Butterworth response.
8. Explain the term Quality Factor.
9. Write the formula for notch frequency.
10. Classify Oscillators
11. Explain the principle of oscillator with block diagram.
12. Differentiate between first order and second order Filter.
13. State the advantages of active filter over passive filter.
14. Draw and explain first order high pass filter.



Maratha Vidya Prasarak Samaj's
Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

RSM POLY Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

15. Draw and explain the ckt. of Wide band pass filter.
16. Draw the circuit and frequency response of notch filter. give expression for notch.
17. Design a band reject filter to reject band of 10kHz to 20kHz.



MCQ Questions:-

(Total number of Question=Marks*3= 18*3=54)

Note: Correct answer is marked with **bold**.

- Which filter type is called a flat-flat filter?
a) Causer filter
b) Butterworth filter
c) Chebyshev filter
d) Band-reject filter
- Which filter performs exactly the opposite to the band-pass filter?
a) Band-reject filter
b) Band-stop filter
c) Band-elimination filter
d) All of the mentioned
- Given the lower and higher cut-off frequency of a band-pass filter are 2.5kHz and 10kHz. Determine its bandwidth.
a) 750 Hz
b) 7500 Hz
c) 75000 Hz
d) None of the mentioned
- In which filter the o/p and i/p volt are equal in amplitude for all freq?
a) All-pass filter
b) High pass filter
c) Low pass filter
d) All of the mentioned
- The gain of the first order low pass filter
a) Increases at the rate 20dB/dec
b) Increases at the rate 40dB/dec
c) **Decreases at the rate 20dB/dec**
d) Decreases at the rate 40dB/dec
- Which among the following has the best stop band response?
a) Butterworth filter
b) Chebyshev filter
c) **Cauer filter**
d) All of the mentioned
- Determine the order of filter used, when the gain increases at the rate of 60dB/decade on the stop band.
a) Second-order low pass filter
b) Third-order High pass filter
c) First-order low pass filter
d) None of the mentioned
- Name the filter that has two stop bands?
a) Band-pass filter
b) Low pass filter
c) High pass filter
d) Band-reject filter
- An electrical filter is a
a) Phase-selective circuit
b) Frequency-selective circuit
c) Filter-selective circuit
d) None of the mentioned



10. Filters are classified as

- a) Analog or digital
- b) Passive or active
- c) Audio or radio frequency
- d) All of the mentioned**

11. Why inductors are not preferred for audio frequency?

- a) Large and heavy**
- b) High power dissipation
- c) High input impedance
- d) None of the mentioned

12. The problem of passive filters is overcome by using

- a) Analog filter
- b) Active filter**
- c) LC filter
- d) combination of analog, digital filters

13. What happens if inductors are used in low frequency applications?

- a) Enhance inductor usage
- b) No losses occurs
- c) Degrades inductor performance**
- d) Low power dissipation

14. Find out the incorrect statement about active and passive filters.

- a) Gain is not attenuated in active filter
- b) Passive filters are less expensive**
- c) Active filter does not cause loading of source
- d) Passive filters are difficult to tune or adjust

15. What are the most commonly used active filters?

- a) All of the mentioned**
- b) Low pass and High pass filters
- c) Band pass and Band reject filters
- d) All-pass filters

16. Choose the op-amp that improves the filter performance.

- a) $\mu A741$
- b) LM318**
- c) LM101A
- d) MC34001

17. Ideal response of filter takes place in

- a) Pass band, stop band freq
- b) Stop band frequency
- c) Pass band frequency**
- d) None of the mentioned

18. Which filter attenuates any frequency outside the pass band?

- a) Band-pass filter**
- b) Band-reject filter
- c) Band-stop filter
- d) All of the mentioned

19. Narrow band-pass filters are defined as

- a) $Q < 10$
- b) $Q = 10$
- c) $Q > 10$**
- d) None of the mentioned



37. How can a first order low pass filter can be converted into second order LPF

- a) By adding LC network c) By adding RC || LC network
b) **By adding RC network** d) None of the mentioned

38. Where pass band gain of the filter is 5, frequency and the high cut-off frequency of the filter are 3000Hz and 1kHz. Find the gain and phase angle of the second order low pass filter?

- a) None of the mentioned c) **Gain mag = -5.19dB , $\phi = 71.56^\circ$**
b) Gain mag = -1.03dB , $\phi = 63.32^\circ$ d) Gain mag = -4.94dB , $\phi = 90^\circ$

39. A second order LPF is given an input frequency of 30kHz and produce .. a output having phase angle of 79° . Determine the pass band gain of the filter?

- a) 11 dB c) **46.78 dB**
b) 89.11 dB d) None of the mentioned

40. The pass band voltage gain of a second order low pass butterworth filter is

- a) **1.586** c) 0.586
b) 8.32 d) 0.707

41. Frequency scaling is done using

- a) **Standard capacitor** c) Standard resistance
b) Varying capacitor d) None of the mentioned

42. How is the higher order filters formed?

- a) By increasing resistors and capacitors in low pass filter
b) By decreasing resistors and capacitors in low pass filter
c) **By inter changing resistors and capacitors in low pass filter**
d) All of the mentioned

43. In a first order high pass filter, frequencies higher than low cut-off frequencies are called

- a) Stop band frequency c) Centre band frequency
b) **Pass band frequency** d) None of the mentioned

44. Determine the expression for output voltage of first order high pass filter?

- a) **$V_O = [1 + (R_F / R_1)] \times [(j2\pi fRC) / (1 + j2\pi fRC)] \times V_{in}$**
b) $V_O = [-(R_F / R_1)] \times [(j2\pi fRC) / (1 + j2\pi fRC)] \times V_{in}$
c) $V_O = \{ [1 + (R_F / R_1)] \times [1 / (1 + j2\pi fRC)] \} \times V_{in}$
d) None of the mentioned



5. Specialized IC Applications

Position in Question Paper

Total Marks-20

Q.2. c) 4-Marks.

Q.4. c) 4-Marks.

Q.5. c) 6-Marks.

Q.6. b) 6-Marks.

Descriptive Questions

1. Give the classification of filters.
2. Define Roll of Rate and order of filter.
3. Define Bandwidth and cut off frequency
4. Define Pass band and stop band.
5. Draw ideal frequency response of filters.
6. Draw frequency response of High pass Filter.
7. State the key characteristics of Butterworth response.
8. Explain the term Quality Factor.
9. Write the formula for notch frequency.
10. Classify Oscillators
11. Explain the principle of oscillator with block diagram. 04Marks Questions:
12. Differentiate between first order and second order Filter.
13. State the advantages of active filter over passive filter.
14. Draw and explain first order high pass filter.
15. Draw and explain the ckt. of Wide band pass filter.
16. Draw the circuit and frequency response of notch filter. give expression



for notch frequency.

17. Design a band reject filter to reject band of 10kHz to 20kHz.

18. Design a wide band pass filter with lower cutoff frequency $f_L=5\text{kHz}$ and higher cutoff frequency $f_H=15\text{kHz}$ and pass band gain =2. Assume $C=0.05\mu\text{F}$, $C'=0.01\mu\text{F}$. Draw full ckt. diagram for the filter.

19. Draw and explain the working of phase shift Oscillator using IC741. 9) Design a high pass filter at a cut off frequency of 2 kHz with a pass band gain of 2. 10) Design and draw Op-Amp based Wien bridge oscillator for frequency 1kHz.



MCQ Questions:-

(Total number of Question=Marks*3= 12*3=36)

Note: Correct answer is marked with **bold**.

- Free running multivibrator is also called as___
 - Stable multivibrator
 - Voltage control oscillator**
 - Square wave oscillator
 - Pulse stretcher
- The output voltage of phase detector is
 - Phase voltage
 - Free running voltage
 - Error voltage**
 - None of the mentioned
- At which state the phase-locked loop tracks any change in input frequency?
 - Free running state
 - Capture state
 - Phase locked state**
 - All of the mentioned
- What is the function of low pass filter in phase-locked loop?
 - Improves low frequency noise
 - Removes high freq noise**
 - Tracks the voltage changes
 - Changes the input frequency
- What is the need to generate corrective control voltage?
 - To maintain the lock
 - To track the freq change
 - To shift the VCO frequency
 - All of the mentioned**
- At what range the PLL can maintain the lock in the circuit?
 - Lock in range**
 - Input range
 - Feedback loop range
 - None of the mentioned
- The pull-in time depends on
 - Initial phase and frequency difference between two sign
 - Overall loop gain
 - Loop filter characteristics
 - All of the mentioned**
- Analog phase detector is often referred as
 - Full wave detector
 - Half wave detector**
 - Rectifier wave detector
 - None of the mentioned
- What happens when VCO output is 90o out of phase with respect to input signal?
 - Perfect lock**
 - Attenuation
 - Shift in phase of comparator
 - Error signal is removed



10. The maximum dc output voltage in digital phase detector occurs
- a) When the phase diff is $\pi/2$
 - b) When the phase diff is π**
 - c) When the phase difference is $3\pi/4$
 - d) When the phase difference is 2π
11. Which among the following has better capture tracking & locking characteristics?
- a) XOR phase detector
 - b) Edge trig phase detector**
 - c) Analog phase detector
 - d) All of the mentioned
1. Determine the time period of a monostable 555 multivibrator.
- a) $T = 0.33RC$
 - b) $T = 1.1RC$**
 - c) $T = 3RC$
 - d) $T = RC$
12. Overcome mistriggering on the positive pulse edges in the monostable circuit?
- a) Connect a RC network at the input
 - b) Connect an integrator at the input
 - c) Connect a differentiator at the input**
 - d) Connect a diode at the input
13. A monostable multivibrator has $R = 120k\Omega$ and the time delay $T = 1000ms$ calculate the value of C?
- a) $0.9\mu F$
 - b) $1.32\mu F$
 - c) $7.5\mu F$**
 - d) $2.49\mu F$
14. Which among the following can be used to detect the missing heart beat?
- a) Monostable multivibrator**
 - b) Astable multivibrator
 - c) Schmitt trigger
 - d) None of the mentioned
15. A 555 timer in monostable application mode can be used for
- a) Pulse position modulation
 - b) Frequency shift keying
 - c) Speed control and measurement**
 - d) Digital phase detector
16. Free running frequency of Astable multivibrator?
- a) $f = 1.45 / (RA + 2RB)C$**
 - b) $f = 1.45(RA + 2RB)C$
 - c) $f = 1.45C / (RA + 2RB)$
 - d) $f = 1.45 RA / (RA + RB)$
17. Astable multivibrator operating at 150Hz has a discharge time of 2.5m. Find the duty cycle of the circuit.
- a) 50%
 - b) 75%
 - c) 95.99%
 - d) 37.5%**
18. How to obtain symmetrical waveform in Astable multivibrator?
- a) Use clocked RS flip-flop
 - b) Use clocked JK flip-flop**
 - c) Use clocked D-flip-flop
 - d) Use clocked T-flip-flop



19. How does a monostable multivibrator used as frequency divider?
- a) **Using square wave gen.** c) Using sawtooth wave generator
b) Using triangular wave gen. d) Using sine wave generator
20. Which device is used for diagnostic purposes and for recording?
- a) Low pass filter c) **Voltage Controlled Oscillator**
b) Monolithic PLL d) None of the mentioned
21. Write the equation for time period of VCO?
- a) $(2 \times V_{cc} \times C_T) / i$ c) $(V_{cc} \times C_T \times i) / 2$
b) **$(V_{cc} C_T) / (2 \times i)$** d) $(2 \times V_{cc}) / (i \times C_T)$
22. Determine the value of current flow in VCO, when the NE566 VCO external timing resistor $R_T = 250 \Omega$ and the modulating input voltage $V_c = 3.25V$, $V_{cc} = +5V$.
- a) 3mA c) **7mA**
b) 12mA d) 10mA
23. External tuning resistor c) Modulating input voltage
b) External tuning capacitor d) **All of the mentioned**
24. Calculate the value of external timing capacitor, if no modulating input signal is applied to VCO. Consider $f_o = 25 \text{ kHz}$ and $R_T = 5 \text{ k}\Omega$.
- a) 6nF c) **2nF**
b) 100 μ F d) 10nF
25. What is the advantage of using filter?
- a) **High noise immunity** c) Provides dynamic range of frequencies
b) Reduce the b.W of PLL d) None of the mentioned
26. Choose the VCO for attaining higher output frequency.
- a) NE566 c) **MC4024**
b) SE566 d) All of the mentioned
27. Voltage to frequency conversion factor for VCO is
- a) $K_v = \Delta V_c / \Delta f_o$ c) $K_v = \Delta f_o \times \Delta V_c$
b) **$K_v = \Delta f_o / \Delta V_c$** d) $K_v = 1 / (\Delta f_o \times \Delta V_c)$
28. Calculate the voltage to frequency conversion factor, where $f_o = 155 \text{ Hz}$ and $V_{cc} = 10V$.
- a) 130 c) 134
b) **124** d) 116
29. Find the equation for change in frequency of VCO?
- a) **$\Delta f_o = (2 \times \Delta V_c) / (R_T \times C_T \times V)$** c) $\Delta f_o = \Delta V_c / (2 \times R_T \times C_T \times V_{cc})$
b) $\Delta f_o = \Delta V_c / (4 \times R_T \times C_T \times V)$ d) $\Delta f_o = (4 \times \Delta V_c) / (R_T \times C_T \times V_{cc})$



30. How to obtain a desired amount of multiplication in frequency multiplier?
a) decreasing the multi factor **c) By selecting proper divide by N-network**
b) increasing the input frequency d) None of the mentioned
31. The frequency corresponding to logic 1 state in FSK is called
a) Space frequency c) Both mark and space frequency
b) Mark frequency d) None of the mentioned
32. Find the frequency shift in FSK generator?
a) 230 Hz c) 180 Hz
b) 250 Hz **d) 200 Hz**
33. Which filter to remove the carrier component in the frequency shift keying?
a) Three stage filter c) Single stage filter
b) Two stage filter d) All of the mentioned
34. What kind of input signal, the freq divider can be avoided frequency multiplier?
a) Triangular waveform c) Saw tooth waveform
b) Square waveform d) Sine waveform
35. What must the typical value of n for a frequency multiplication / division?
a) $n \leq 12$ c) $n < 10$
b) $n > 11$ **d) $n = 7$**
36. Determine the offset frequency of frequency translation,
when the output and input frequency are given as 75kHz and 1000Hz.
a) 35 kHz c) 29 kHz
b) 20 kHz d) 14 kHz