



Maratha Vidya Prasarak Samaj's

Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

*Subject: -Elements of Electrical
Engineering (22215)*



Maratha Vidya Prasarak Samaj's

Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

SYLLABUS

Chapter No.	Name of chapter	Marks With Option
1	Magnetic Circuits	14
2	AC Fundamentals	16
3	Poly phase AC circuit	12
4	Transformer and DC Motor	22
5	Fractional horse Power motors	20
6	devices and switchgear	18
Total Marks: -		104



BOARD THEORY PAPER PATTERN FOR EEC (22215)

Q.1		Attempt any FIVE	5*2=10
	a)	Magnetic Circuits	
	b)	AC Fundamentals	
	c)	Poly phase AC circuits	
	d)	Transformer and DC Motor	
	e)	Transformer and DC Motor	
	f)	Fractional horse Power motors	
	g)	Protective devise and switchgear	
Q.2		Attempt any THREE	3*4=12
	a)	Magnetic Circuits	
	b)	AC Fundamentals	
	c)	Poly phase AC circuits	
	d)	Transformer and DC Motor	
Q.3		Attempt any THREE	3*4=12
	a)	Magnetic Circuits	



Maratha Vidya Prasarak Samaj's
Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.
Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

	b)	Transformer and DC Motor
	c)	Fractional horse Power motors
	d)	Protective devise and switchgear
Q.4		Attempt any Three 3*4=12
	a)	Magnetic Circuits
	b)	Transformer and DC Motor
	c)	Fractional horse Power motors
	d)	Fractional horse Power motors
	e)	AC Fundamentals
Q.5		Attempt any TWO 2*6=12
	a)	AC Fundamentals
	b)	Poly phase AC circuits
	c)	Transformer and DC Motor
Q.6		Attempt any TWO 2*6=12
	a)	Fractional horse Power motors
	b)	Protective devise and switchgear
	c)	Protective devise and switchgear



CLASS TEST - I

PAPER PATTERN

COURSE: -Elements of Electrical Engineering (22215)

PROGRAMME: -Electrical Engineering

Syllabus: -

Unit No.	Name of the Unit	Course Outcome (CO)
1	Magnetic Circuits	CO-215.01
2	AC Fundamentals	CO-215.02
3	Poly phase AC circuits	CO-215.03

Q.1	Attempt any FOUR$4*2=8$Marks	Course Outcome (CO)
a)	Magnetic Circuits	CO.215.1
b)	AC Fundamentals	CO.215.2
c)	Poly phase AC circuits	CO.215.3
d)	Magnetic Circuits	CO.215.1
e)	AC Fundamentals	CO.215.2
f)	Poly phase AC circuits	CO.215.3
Q.2	Attempt any THREE$3*4=12$ Marks	
a)	Magnetic Circuits	CO.215.1
b)	AC Fundamentals	CO.215.2
c)	Poly phase AC circuits	CO.215.3
d)	AC Fundamentals	CO.215.2



CLASS TEST - II

PAPER PATTERN

COURSE: - Elements of Electrical Engineering (22215)

PROGRAMME: -Electrical Engineering

Syllabus: -

Unit No.	Name of the Unit	Course Outcome (CO)
4	Transformer and DC Motor	CO-215.04
5	Fractional horse Power motors	CO-215.05
6	Protective devise and switchgear	CO-215.06

Q.1	Attempt any FOUR	4*2=8Marks	Course Outcome (CO)
a)	Transformer and DC Motor		CO.215.4
b)	Fractional horse Power motors		CO.215.5
c)	Protective devise and switchgear		CO.215.6
d)	Transformer and DC Motor		CO.215.4
e)	Fractional horse Power motors		CO.215.5
f)	Protective devise and switchgear		CO.215.6
Q.2	Attempt any THREE	3*4=12 Marks	
a)	Transformer and DC Motor		CO.215.4
b)	Fractional horse Power motors		CO.215.5
c)	Protective devise and switchgear		CO.215.6
d)	Transformer and DC Motor		CO.215.4



Maratha Vidya Prasarak Samaj's

Rajarshi Shahu Maharaj Polytechnic, Nashik

Udoji Maratha Boarding Campus, Near Pumping Station, Gangapur Road, Nashik-13.

Affiliated to MSBTE Mumbai, Approved by AICTE New Delhi, DTE Mumbai & Govt. of Maharashtra, Mumbai.

COURSE OUTCOME

(CO)

COURSE: - Elements of Electrical Engineering (22215)

PROGRAMME: -Electrical Engineering

CO.NO.	Course Outcome
CO-215.01	Use principles of magnetic circuits
CO-215.02	Use single phase AC supply for electrical and electronics equipment
CO-215.03	Use three phase AC supply for industrial equipment and machines
CO-215.04	Connect transformer and DC motors for specific requirements
CO-215.05	Use FHP motors for diversified applications.
CO-215.06	Use relevant protective devices/switchgear for different requirements.



1. Magnetic Circuits

Position in Question Paper

Total Marks-10

Q.1. a) 2-Marks.

Q.3. a) 4-Marks.

Q.4. a) 4-Marks.

Descriptive Question

1. Define Reluctance. What are its units?
2. Explain self-induced emf and mutually induced emf with neat sketch
3. Compare magnetic circuit and electric circuit on any four points.
4. Explain B-H curve and draw with all parameters.
5. Explain with neat diagram series and parallel magnetic circuits.
6. State Fleming's right hand rule
7. Define Faraday's first law of electromagnetic induction.
8. Compare electric and magnetic circuit on any four points.
9. Define Electromagnetism, Magnetic Flux, and MMF with their units.
10. Explain the terms 1. Statically induced EMF 2. Dynamically induced EMF
11. State and Explain Lenz Law.

MCQ Question

(Total number of Question=Marks*3=10*3=30)

Note: Correct answer is marked with **bold**.

1. An air gap is usually inserted in a magnetic circuits to
 - a) Increase m.m.f.
 - b) Increase the flux
 - c) **Prevent saturation**
 - d) None of the above
2. Permeability in a magnetic circuit corresponds toin an electric circuit
 - a) Resistance
 - b) Resistivity
 - c) **Conductivity**
 - d) Conductance
3. Those magnetic materials are best suited for making armature and transform cores which havepermeability andhysteresis loss
 - a) High, high
 - b) **Low, high**



- a) Low co-ercivity
b) Low retentivity
16. Conductivity is analogous to
a) Retentivity
b) Resistivity
17. Conductance is analogous to
a) Permeance
b) Reluctance
18. Material for good magnetic memory should have
a) Low hysteresis loss
b) High permeability
c) **Low hysteresis loss**
d) High co-ercivity
19. Hard steel is suitable for making permanent magnets because
a) **It has good residual magnetism**
b) Its hysteresis loop has large area
c) Its mechanical strength is high
d) Its mechanical strength is low
20. Permanent magnets are normally made of
a) **Alnico alloys**
b) Aluminium
c) Cast iron
d) Wrought iron
21. How is mutual inductance between two coils decreased?
a) By using a common core
b) By moving the coils closer
c) By moving the coils apart
d) By increasing the number of turns of either coil
22. A magnetic field is
a) The current flow through space around a permanent magnet
b) **The force set up when current flows through a conductor**
c) The force that drives current through a resistor
d) The force between the plates of a charged capacitor
23. Ohm's law can be used only to a _____ circuit or component.
a) Unilateral
b) Exponential
c) Trivalent
d) **Linear**
24. The current flows, the magnetic field conductor is in what direction?
a) The same as the current direction
b) Opposite the current direction
c) Omnidirectional
d) In the direction determined by the left hand rule
25. The magnetic field around the conductor is determined by the
a) Size of the conductor
b) Amount of current
c) Current divided by the resistance



- d) Resistance divided by the current
26. Back emf refers to the
- a) Current equal to the applied emf
 - b) Opposing emf
 - c) Current opposing the applied emf
 - d) Voltage opposing the applied emf**
27. The magnetic flux through a coil changes. This results to the induced emf acting in a direction as to
- a) Oppose the change**
 - b) Aid the change
 - c) Either oppose or aid the change
 - d) Neither oppose nor aid the change
28. A magnetic flux of 2.5×10^4 Wb through an area of 5×10^4 square meters results
- a) Wb
 - b) Tesla of flux density
 - c) 5×10^{-5} Wb of flux**
 - d) 5000 Tesla of flux density
29. If a 20 V potential is applied across a relay coil with 50 turns having 1Ω of resistance, the total magnetomotive producing magnetic flux in the circuit is
- a) 10 Wb
 - b) 50 T
 - c) 1000 A t/m
 - d) 1000 A.t**
30. What is the reluctance of a magnetic path having a length of 2×10^{-3} m and cross-sectional area of $2.5 \times 10^{-3} \text{ m}^2$?
- a) 6366 A.t/Wb**
 - b) 6000 A.t/Wb
 - c) 8×10^{-3} A.t/Wb
 - d) 0.8 A.t/Wb



2. AC Fundamental

Position in Question Paper

Total Marks-10

Q.1. b) 2-Marks.

Q.2. b) 4-Marks.

Q.4. a) 4-Marks.

Descriptive Question

1. Define - frequency. State its relation with time period.
2. If maximum value of a sine wave is 25A. Calculate its average value.
3. Draw a power triangle and state the relation between its sides.
4. State the range of phase angle and hence pf for a series RC circuit.
5. In a series RL circuit $V_R = 100V$ and $V_L = 150V$. Find equivalent voltage across the circuit.
6. An alternating current is given by $i = 20 \sin (314t)$. Find –Current at $t = 0.0025$ sec at first instant. Time required to reach at 12A for first time.
7. A series circuit has a leading pf. Express it with circuit, waveform and phasor diagram.
8. In RLC series circuit $R = 8W$, $L = 0.42 H$ with an unknown capacitor. If the circuit is connected across 230V, 50 Hz, 1ϕ AC. Calculate value of capacitor so that circuit resonates at supply frequency. Also calculate current and pf at this instant.
9. Define peak factor and form factor. State value of each for a pure sine wave.
10. Define - frequency. State its relation with time period.
11. If maximum value of a sine wave is 25A. Calculate its average value.
12. Draw a power triangle and state the relation between its sides.
13. State the range of phase angle and hence pf for a series RC circuit.
14. In a series RL circuit $V_R = 100V$ and $V_L = 150V$. Find equivalent voltage across the circuit.
15. An alternating current is given by $i = 20 \sin (314t)$. Find –
 - 1) Current at $t = 0.0025$ sec at first instant.
 - 2) Time required to reach at 12A for first time.
16. A series circuit has a leading pf. Express it with circuit, waveform and phasor diagram.



17. In RLC series circuit $R = 8\Omega$, $L = 0.42\text{ H}$ with an unknown capacitor. If the circuit is connected across 230V , 50 Hz , 1ϕ AC. Calculate value of capacitor so that circuit resonates at supply frequency. Also calculate current and pf at this instant.
18. Define peak factor and form factor. State value of each for a pure sine wave.
19. A series RLC circuit consists of $R = 20\Omega$, $L = 1\text{H}$ and $C = 2500\ \mu\text{f}$. If it is connected across 230V , 1ϕ AC. Calculate Q factor and resonant frequency.
20. Derive the condition for resonance in an RLC series circuit. Also derive the equation for Q factor.
21. State nature of pf for any two conditions in RLC series circuit. Draw phasor diagram for each.
22. Write any two advantages of AC over DC
23. Explain the concept of lagging and leading phase angle by waveform.
24. Define: (i) Form factor (ii) Peak factor
25. State value of power factor for purely resistive and purely capacitive circuit.
26. Explain the generation of single phase AC supply by an elementary alternator with neat sketch.
27. An alternating current given by equation $i = 142.14 \sin 628 t$. find –
(i) Maximum value (ii) Time period (iii) RMS value (iv) Average value (v) Form factor (vi) Peak factor

MCO Question

(Total number of Question=Marks*3=10*3=30)

Note: Correct answer is marked with **bold**

1. Instantaneous voltage is the product of resistance and _____ current in a **resistive circuit**.
a) **Instantaneous** c) RMS
b) Average d) Peak
2. Find the value of the instantaneous voltage if the resistance is $2\ \Omega$ and the instantaneous current in the circuit is 5A .
a) **5V** c) 10V
b) 2V d) 2.5
3. The power for a purely resistive circuit is zero when?



- a) Current is zero
b) Voltage is zero
c) Both current and voltage are zero
d) Either current or voltage is zero
4. The correct expression for the instantaneous current if instantaneous voltage is $V_m(\sin t)$ in a resistive circuit is?
a) 1A
b) 2A
c) 3A
d) 4A
5. Calculate the resistance in the circuit if the rms voltage is 20V and the rms current is 2A.
a) 2 ohm
b) 5 ohm
c) 10 ohm
d) 20 ohm
- 6 The correct expression for the instantaneous current in a resistive circuit is?
a) $i = V_m(\sin t)/R$
b) $i = V_m(\cos t)/R$
c) $i = V(\sin t)/R$
d) $i = V(\cos t)/R$
- 7 Can ohm's law be applied in an ac circuit?
a) Yes
b) No
c) Depends on the rms current
d) Depends on the rms voltage
- 8 The correct expression for the instantaneous current if instantaneous voltage is $V_m(\sin t)$ in an inductive circuit is?
a) $i = V_m(\sin t)/X_L$
b) $i = V_m(\cos t)/X_L$
c) $i = -V_m(\sin t)/X_L$
d) $i = -V_m(\cos t)/X_L$
- 9 Inductor does not allow sudden changes in?
a) Voltage
b) Current
c) Resistance
d) Inductance
- 10 Inductance is _____ to number of turns in the coil
a) **directly proportional**
b) inversely proportional
c) equal
d) not related
11. Choke involve use of _____
a) Resistor
b) Capacitor
c) Inductor
d) Transistor
12. What is the value of current in an inductive circuit when there is no applied voltage?
a) Minimum
b) Maximum
c) Zero
d) Cannot be determined
13. What is the current in an inductive circuit when the applied voltage is maximum?
a) Infinity
b) Maximum
c) Zero
d) Cannot be determined
14. In an inductive circuit, the voltage _____ the current?
a) Leads
b) Lags



- c) Is greater than
15. In an inductive circuit, the current _____ the voltage?
a) Leads
b) **Lags**
16. In which device inductor cannot be used?
a) filter circuit
b) transformer
c) choke
d) **dielectric**
- d) Is less than
c) Is greater than
d) Is less than
17. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V 50Hz sinusoidal supply. Calculate the current in the circuit.
a) 2.2A
b) 4.2A
c) 6.2A
d) **8.2**
18. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V 50Hz sinusoidal supply. Calculate the phase difference.
a) **-55.1**
b) 55.1
c) 6
d) -66.1
19. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V 50Hz sinusoidal supply. Calculate the voltage across the resistor.
a) 31.8V
b) **57.4V**
c) 67.3V
d) 78.2
20. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a 100V 50Hz sinusoidal supply. Calculate the voltage across the inductor.
a) 52V
b) **82V**
c) 65V
d) 76V
21. A resistance of 7 ohm is connected in series with an inductance of 31.8mH. The circuit is connected to a x V 50Hz sinusoidal supply. The current in the circuit is 8.2A. Calculate the value of x.
a) 10V
b) 50V
c) **100V**
d) 120
22. Which, among the following, is the correct expression for ϕ .
a) $\phi = \tan^{-1} (XL/R)$
b) $\phi = \tan^{-1} (R/XL)$
c) $\phi = \tan^{-1} (XL * R)$
d) $\phi = \cos^{-1} (XL/R)$
23. For an RL circuit, the phase angle is always _____
Positive
a) **Negative**
b) 0
c) 90



24. What is ϕ in terms of voltage?
a) $\phi = \cos^{-1} V/V_R$
b) $\phi = \cos^{-1} V * V_R$
c) $\phi = \cos^{-1} V_R/V$
d) $\phi = \tan^{-1} V/V_R$
25. What is $\sin\phi$ from impedance triangle?
a) X_L/R
b) X_L/Z
c) R/Z
d) Z/R
26. What is the resonance frequency of ac circuit?
a) $1/\sqrt{LC}$
b) $\sqrt{L/C}$
c) \sqrt{LC}
d) LC
27. What is impedance at resonance?
a) maximum
b) **minimum**
c) zero
d) cannot be determined
28. What is the value of impedance at resonance?
a) X_L
b) X_C
c) **R**
d) 0
29. What is ϕ in terms of voltage?
a) $\phi = \cos^{-1} V/V_R$
b) $\phi = \cos^{-1} V * V_R$
c) $\phi = \cos^{-1} V_R/V$
d) $\phi = \tan^{-1} V/V_R$
30. What is $\tan\phi$ for RC circuit?
a) X_C/R
b) X_L/R
c) R/Z
d) Z/R



3. Poly phase AC Circuits

Position in Question Paper

Total Marks-10

Q.1. c) 2-Marks.

Q.2. c) 4-Marks.

Q.4. b) 4-Marks.

Descriptive Question

1. Draw phasor diagram for 3ϕ generated voltages.
2. List any two advantages of 3ϕ circuits over single phase circuits.
3. List any four observations from the phasor diagram of a 3ϕ delta connection.
4. Three impedances each of $Z = 15 + j18\Omega$ are connected in star across a 400V, 3ϕ , AC.
Calculate $-V_{ph}$, I_{ph} , I_L , Pf
5. Draw the sinusoidal waveform of 3ph emf and also indicate the phase sequence.
6. State relationship between line voltage and phase voltage, line current and phase current in a balanced delta connection. Draw complete phasor diagram of voltages and current.
7. State any four advantages of poly phase circuit over single phase circuit.
8. Draw the waveform representation of a three phase AC supply with neat labels.
9. State four advantages of poly-phase circuit over single phase circuit.
10. Draw delta connected load. State relation between: Line voltage and phase voltage, Line current and phase current
11. Draw 3-phase voltage waveform of a.c. supply with respect to time.
12. Write any four advantages of 3f system over 1f system.
13. Write meaning of the term "balanced load" in case of 3f system.
14. Draw phasor diagram for 3ϕ generated voltages.
15. List any two advantages of 3ϕ circuits over single phase circuits.
16. List any four observations from the phasor diagram of a 3ϕ delta connection.
17. Three impedances each of $Z = 15 + j18\Omega$ are connected in star across a 400V, 3ϕ , AC.
Calculate $-V_{ph}$, I_{ph} , I_L , Pf
18. Draw the sinusoidal waveform of 3ph emf and also indicate the phase sequence.



11. The power generated by a machine increases _____ percent from single phase to two phase.
- a) 40.4
b) 41.4
c) 42.4
d) 43.4
12. The percentage of power increased from single phase to three phase is?
- a) **50**
b) 100
c) 150
d) 200
13. When the power factor is _____ the power becomes zero 100 times a second in a 50Hz supply.
- a) 0
b) 1
c) 2
d) 3
14. Which motors are called self-starting motors?
- a) single phase
b) two phase
c) three phase
d) four phase
15. In three phase system, the three voltages (currents) differ in phase by _____ electrical degrees from each other in a particular sequence.
- a) 30
b) 60
c) 90
d) 120
16. In a two phase generator, the armature has two distinct windings that are displaced _____ apart.
- a) 45°
b) 90°
c) 135°
d) 180°
17. In three phase system at any given instant, the algebraic sum of three voltages must be?
- a) **0**
b) 1
c) 2
d) 3
18. Phase sequence depends on the _____
- a) Field
b) rotation of the field
c) armature
d) rotation of the armature
19. If RR' , YY' and BB' constitutes three phase sequence if $V'_{RR} = V_m \sin \omega t$ its corresponding field magnets are in clockwise direction, then $V'_{YY} = ?$
- a) $V_m \sin \omega t$
b) $V_m \sin(\omega t + 120^\circ)$
c) $V_m \sin(\omega t - 120^\circ)$
d) $V_m \sin(\omega t - 240^\circ)$
20. If RR' , YY' and BB' constitutes three phase sequence if $V'_{RR} = V_m \sin \omega t$ its corresponding field magnets are in clockwise direction, then the value of V'_{BB} is?
- a) **$V_m \sin(\omega t - 240^\circ)$**
b) $V_m \sin(\omega t - 120^\circ)$
c) $V_m \sin(\omega t + 240^\circ)$
d) $V_m \sin \omega t$



21. In a three phase alternator, there are _____ independent phase windings or coils.
- a) 1
b) 2
c) **3**
d) 4
22. Each coil in three phase alternator has _____ number of terminals.
- a) **2**
b) 4
c) 6
d) 8
23. In wye or star connection _____ of the three phases are joined together within the alternator.
- a) **similar ends**
b) opposite ends
c) one similar end, two opposite ends
d) one opposite end, two opposite ends
24. The voltage between _____ and _____ is called phase voltage.
- a) line and line
b) line and reference
c) neutral point and reference
d) **line and neutral point**
25. The voltage between _____ is called line voltage.
- a) line and neutral point
b) line and reference
c) **line and line**
d) neutral point and reference
26. In the Delta or Mesh connection, there will be _____ number of common terminals.
- a) 1
b) 2
c) 3
d) **0**
27. The relation between line voltage and phase voltage in Delta or Mesh connection is?
- a) $V_{\text{phase}} > V_{\text{line}}$
b) $V_{\text{phase}} < V_{\text{line}}$
c) **$V_{\text{phase}} = V_{\text{line}}$**
d) $V_{\text{phase}} \geq V_{\text{line}}$
28. Which of the following voltage is a phase voltage in the delta connection?
- a) V_{RN}
b) **V_{BR}**
c) V_{YN}
d) V_{BN}
29. A balanced delta-connected load of $(2+j3) \Omega$ per phase is connected to a balanced three-phase 440V supply. The phase current is 10A. Find the total active power.
- a) 7.26W
b) 726W
c) **7260W**
d) 72.6W
30. A balanced delta-connected load of $(2+j3) \Omega$ per phase is connected to a balanced three-phase 440V supply. The phase current is 10A. Find the apparent power.
- a) **10955.67 VAR**
b) 10.95567 VAR
c) 109.5567 VAR
d) 1.095567 VAR



4. Transformer and DC Motor

Position in Question Paper

Total Marks-14

Q.1. c) 2-Marks.

Q.2. d) 4-Marks.

Q.3. b) 4-Marks.

Q.4. b) 4-Marks.

Descriptive Question

1. Define the transformation ratio of a transformer
2. State working principle of transformer.
3. Draw a practical set up to find voltage and current ratio on a 230/115 V, 1KVA, 1φ 50Hz transformer. Also write reading of each meter.
4. Compare auto transformer and two winding transformer on any four points
5. Write two applications of D.C. series motor.
6. State function of poles and brushes in DC motors. State material for each.
7. Write principle of operation for a DC motor
8. Draw neat constructional sketch of auto transformer. State its advantages and applications.
9. Draw neat constructional sketch of shell type transformer.
10. A 2000/200 V, single phase, 50 Hz transformer has the maximum flux of 30 mwb. Find out the no. of turns on primary and secondary windings if the cross sectional area of the core is 1.1 cm²
11. Compare two winding transformer and auto transformer. (Any four points)
12. Draw schematic representation of - DC shunt motor
13. Draw schematic representation of DC series motor
14. Draw schematic representation of DC compound motor

MCQ Question

(Total number of Question=Marks*3=14*3=42)

Note: Correct answer is marked with **bold**

1. The main purpose of using core in transformer is to
 - a) **Decrease reluctance of the common magnetic circuit**
 - b) Decrease iron losses



- c) Prevent hysteresis loss
- d) Prevent eddy current losses
2. Transformer works on the principle of
 - a) **Self induction**
 - b) Mutual induction
 - c) Faraday's law of electromagnetic induction
 - d) Self and mutual induction both
3. If dc voltage is applied to the primary of a transformer it may
 - a) Work
 - b) **Burn the winding**
 - c) Not work
 - d) Give lower voltage on the secondary side
4. Which of the following will improve the mutual coupling between primary and secondary of a transformer ?
 - a) Transformer oil of high breakdown voltage
 - b) Winding material of high resistivity
 - c) High reluctance magnetic core
 - d) **Low reluctance magnetic core**
5. Which type of core is used for a high-frequency transformer
 - a) Open iron core
 - b) **Air core**
 - c) Closed iron core
 - d) None of these
6. Transformer oil used in transformer provides
 - a) **Insulation and cooling**
 - b) Cooling and lubrication
 - c) Lubrication and insulation
 - d) Insulation, cooling and lubrication
7. Enamel layer is coated over the lamination of a transformer core to
 - a) Attain adhesion between the lamination
 - b) Prevent corrosion of laminations
 - c) Decrease the hum
 - d) **Insulate the lamination from each other**
8. In a transformer, the magnetic coupling between the primary and secondary circuit can be increased by
 - a) increasing the number of turns
 - b) using soft material for winding
 - c) **using magnetic core of low reluctance**
 - d) using transformer oil better quality



9. If the density in the core of a transformer is increased
- the frequency the secondary winding voltage increases**
 - wave shape of the secondary winding voltage gets distorted
 - size of the transformer can be reduced
 - eddy current losses increase
10. The power factor in a transformer
- is always unit
 - is always leading
 - is always lagging
 - depends on the power factor of load**
11. Which of the following transformer will be largest in size?
- 1 kVA, 50 Hz
 - 1 KVA, 60 Hz
 - 1KVA, 100Hz
 - 1KVA, 500 Hz**
12. A transformer transforms
- Current
 - Voltage
 - Frequency
 - Both voltage and current**
13. A transformer does not change the following
- Waveform
 - Frequency
 - Voltage
 - Both frequency and waveform**
14. A transformer provides a path for magnetic flux of
- High reluctance
 - High conductivity
 - Low reluctance**
 - Low conductivity
15. An ordinary transformer works on
- A.C**
 - D.C
 - Both a.c. and d.c.
 - Pulsating d.c.
16. An ideal transformer is one which has
- A common core for its primary and secondary winding
 - Core of stainless steel and winding of pure copper wire
 - No losses and magnetic leakage**
 - Interleaved primary and secondary windings
17. The primary and secondary induced emfs E_1 and E_2 in two-winding transformer are always
- Antiphase with each other
 - In phase with each other**
 - Equal in magnitude
 - Determined by load on transformer secondary



18. An step-up transformer increases
- a) Current
 - b) Frequency
 - c) **Voltage**
 - d) Power
19. Eddy current losses in a transformer core may be reduced by
- a) Reducing the air gap in the magnetic circuit
 - b) **Reducing the thickness of lami-nations**
 - c) Increasing the thickness of lami-nations
 - d) Increasing the gap in the magnetic circuit
20. The transformer core is generally made of
- a) Alumimium
 - b) **Silicon steel**
 - c) Copper
 - d) Wood
- 21.22. Which of the following is minimized by laminating the core of a transformer?
- a) Hysteresis loss
 - b) Eddy current loss
 - c) Heat loss
 - d) **All of these**
- 22.23. Thickness of laminations of trans-former core is usually of the order of
- a) 0.35 mm to 0.5 mm
 - b) 3.5 mm to 5 mm
 - c) 35 mm to 50 mm
 - d) **5mm to 10 mm**
23. The size of transformer core depends on
- a) Area of the core
 - b) Flux density of core material
 - c) Frequency
 - d) **Both (b) and (c)**
24. In power transformers, breather is used to
- a) Provide insulation to the windings
 - b) Provide cooling to the windings
 - c) **Take insulating oil from the con-servator**
 - d) Extract moisture from the air
25. In a transformer, conservator con-sists of
- a) Drum placed at the bottom of the tank
 - b) **An air tight metal drum fixed at the top of the tank**
 - c) Overload protection circuit
 - d) None of these
26. In a transformer, the resistance between its primary and secondary should be
- a) **Infinite**
 - b) Zero
 - c) About 1 M Ω
 - d) About 100 M Ω
27. For large power transformer, best utilization of available core space can be made by using
- a) Square core section
 - b) **Stepped core section**
 - c) Rectangular core section
 - d) None of these



28. Five limb core construction of transformer has advantage over three limb core construction that
- Hysteresis loss is less
 - Permeability is higher
 - Magnetic reluctance of the three phases can be balanced**
 - Eddy current loss is less
29. A shunt motor is fitted with a field regulator for speed control. For constant torque load, the speed will be minimum when the resistance of the regulator is
- 0Ω**
 - Infinite
 - About 10Ω
 - About 100Ω
30. Transformer windings are tapped in the middle because
- It eliminates axial forces on the windings**
 - It eliminates radial forces on the windings
 - It reduces insulation requirement
 - None of these
31. Which of the following materials is used to absorb moisture from air entering the transformer ?
- Silica sand
 - Silical gel**
 - Felt pad
 - Sodium chloride
32. Which of the following acts as a protection against high voltage surges due to lightning and switching?
- Horn gaps**
 - Thermal overload relays
 - Conservator
 - Breather
33. A tap changer is used on a trans-former for
- Adjustment in power factor
 - Adjustment in secondary voltage**
 - Adjustment in primary voltage
 - Adjustments in both primary and secondary voltage
34. Overcurrents in a transformer affect
- Insulation life
 - Temperature rise
 - Mechanical stress
 - All of these**
35. Highest rating transformers are likely to find application in
- Generation
 - Transmission
 - Distribution**
 - Substation
36. Transformer ratings are usually expressed in terms of
- Voltage
 - KVA
 - KWh**
 - KW



37. The noise in transformer due to vibration of laminations set by magnetic forces, is called
- a) Flicker noise
 - b) Transit-time noise
 - c) Agitation noise
 - d) **Humming noise**
38. The maximum load that a power transformer can carry is limited by its
- a) **Voltage ratio**
 - b) Copper loss
 - c) Temperature noise
 - d) Dielectric strength of oil
39. In a three-phase transformer, the phase difference between the primary voltage and the induced secondary winding voltage is
- a) 90°
 - b) 120°
 - c) **180°**
 - d) None of the above
40. In dc motor, the rotor is
- a) Welded to the shaft
 - b) **Keyed to the shaft**
 - c) Soldered to the shaft
 - d) Both to the shaft
41. In a dc motor, pole shoes are fixed to the magnet core by
- a) **Set of screws**
 - b) Key
 - c) Soldering
 - d) Welding
42. Carbon brushes are used in electric motors to
- a) Prevent sparking during commutation
 - b) **Provide a path for flow of current**
 - c) Brush off carbon deposits on the commutator
 - d) None Of these



5. Fractional Horse Power Motor

Position in Question Paper

Total Marks-14

Q.1. f) 2-Marks.

Q.3. c) 4-Marks.

Q.4. c) 4-Marks.

Q.4. d) 4-Marks.

Descriptive Question

1. State the types of single phase induction motors.
2. Draw schematic representation of capacitor. Start capacitor run induction motor. Also state its applications.
3. Draw a neat schematic of shaded pole 1φ Induction motor. List any two applications of it.
4. Explain principle of operation of universal motor with neat diagram
5. Write any two applications of following motors - Universal motor (ii) Stepper motor
6. Explain the working principle of stepper motor and explain any one type with neat sketch.
7. Suggest suitable motor for following applications- (i) Food Mixer (ii) Electric Fan
8. List different types of stepper motor. State one application of stepper motor.
9. List any four applications of stepper motor
10. Draw a neat schematic of universal motor. State its principle of operations. Write the method for reversal of direction.
11. Draw a neat sketch of permanent capacitor 1φ induction motor. Explain its working

MCQ Question

(Total number of Question=Marks*3=14*3=42)

Note: Correct answer is marked with **bold**

1. At zero in an induction motor
 - a) Motor runs as a generator
 - b) **Motor does not run**
 - c) The motor runs an at synchronous speed
 - d) Slip produced is zero
2. In an induction motor, rotor slots are usually not quite parallel to the shaft but are given a slight skew



- a) To reduce the magnetic hum
 - b) To reduce the locking tendency of the rotor
 - c) **Both (a) and (b) above**
 - d) To increase the speed of the motor
3. The field of an induction motor rotor rotates relative to the stator at
- a) Rotor speed
 - b) **Synchronous speed**
 - c) Slip speed
 - d) Very low speed
4. In an induction motor, rotor runs at a speed
- a) Equal to the speed of stator field
 - b) **Lower than the speed of stator field**
 - c) Higher than the speed of stator field
 - d) Having no relation with the speed of stator field
5. Starters are used in induction motor because
- a) Its starting torque is high
 - b) It is run against heavy load
 - c) It can not run in reverse direction
 - d) **Its starting current is five times or more than its rated current**
6. When an induction motor runs at rated load and speed, the iron losses are
- a) Negligible
 - b) Very heavy
 - c) **Independent of supply frequency**
 - d) Independent of supply voltage
7. By synchronous wattage of an induction motor is meant
- a) Stator input in watts
 - b) Rotor output in watts
 - c) **Rotor input in watts**
 - d) Shaft output in watts
8. The emf induced in the rotor of an induction motor is proportional to
- a) Voltage applied to stator
 - b) Relative velocity between flux and rotor conductors
 - c) **Both (a) and (b) above**
 - d) Slip
9. The synchronous speed of an induction motor is defined as
- a) **Natural speed at which a magnetic field rotates**
 - b) The speed of a synchronous motor
 - c) The speed of an induction motor at no load
 - d) None of these
10. The starting torque of an indication motor is maximum when
- a) **Rotor resistance equals rotor reactance**



- b) Rotor resistance is twice the rotor reactance
c) Rotor resistance is half the rotor reactance
d) Rotor resistance is R_2 times the rotor reactance
11. In a shaded pole motor, the locked rotor current is
a) 10 times the full load current
b) 4 to 5 times the full load current
c) **slightly more than the full load current**
d) less than the full load current.
12. A capacitor motor of 1/4 HP needs a condenser of $8 \mu\text{F}$. A similar motor of 3/4 HP will need a condenser of
a) **$20 \mu\text{F}$** c) $2 \mu\text{F}$.
b) $8 \mu\text{F}$ d) $3 \mu\text{F}$
13. The rotor of which motor does not have winding on it ?
a) Universal motor c) Reluctance motor
b) **Hysteresis motor** d) Repulsion motor.
14. Which motor has unsymmetrical rotor ?
a) Universal motor c) Split-phase motor
b) Shaded pole motor d) **Reluctance motor.**
15. If a single phase motor runs slow, the probable case may be
a) overload c) low voltage
b) low frequency d) **any of the above.**
16. A single phase capacitor start motor will take starting current nearly
a) same as full load current
b) **twice the full load current**
c) three times the full load current
d) four to six times the full load current.
17. Which motor will make least noise ?
a) Capacitor motor c) Shaded pole motor
b) Universal motor d) **Hysteresis motor.**
18. Shaded pole motors are not provided with
a) capacitor c) commutator
b) centrifugal switch d) **all of the above.**
19. In a universal motor, normally the ratio of width of brush to the width of commutator segments is
a) 1 : 1 c) **2 : 1**
b) 1 : 2 d) 4 : 1.
20. For a given output and speed, a universal motor as compared to 220 V, 50 Hz supply will require
a) **less voltage at low frequency** c) high voltage at high frequency
b) less voltage at high frequency d) high voltage at low frequency.
21. The short coming of repulsion motor is



- a) variation of speed with load
b) low power factor
c) tendency to spark at brushes
d) **all of the above.**
- 22..The disadvantage of shaded pole motor is
a) low starting torque'
b) low efficiency
c) very little over load capacity
d) **all of the above.**
- 23.. The efficiency of shaded pole motor is in the range
a) 80 to 95 percent
b) 70 to 80 percent
c) 50 to 70 percent
d) **5 to 35 percent.**
- 24.For domestic sewing machine the size of the motor required will be
a) 10-15 watts
b) 15-25 watts
c) **100-150 watts**
d) 250 to 750 watts.
25. A ceiling fan of 1400 mm sweep will have motor rating of
a) to 15 watts
b) 50 to 70 watts
c) **120 to 180 watts**
d) 250 to 500 watts.
26. Which of the following applications would need the smallest size of motor
a) Domestic motor
b) **Electric clock**
c) Table fan
d) Sewing machine.
- 27.All single phase ac motors are designed to operate usually on
a) 220 V only
b) 220V + 10V
c) 220 ± 0 V
d) **220 ± 10% volts.**
28. All single phase ac motors are designed usually to operate on the frequency
a) 50 Hz
b) 50 ± 0.5 Hz
c) 50 ± 1 Hz
d) **50. ± 5 Hz.**
29. When a dc series motor is connected to ac supply, it will
a) spark excessively
b) give poor efficiency
c) run on poor power factor
d) **all of the above.**
- 30.The torque-speed characteristic of a repulsion motor resembles that of which of the following dc motor ?
a) separately excited motor
b) shunt motor
c) series is motor
d) **compound motor.**
31. In a single phase capacitor motor the direction of rotation will be in the opposite direction to the original when
a) electrolytic capacitor is replaced by paper capacitor
b) two capacitors of equal value are used
c) capacitor is replaced by a resistance
d) **capacitor is replaced by an inductor.**
- 32.In a hysteresis motor, the position of shaded pole with respect to main pole determines
a) speed of motor
b) **direction of rotation**
c) hysteresis loss
d) no load rpm
33. In a shaded pole motor, the direction of rotation is from
a) **main pole to shaded pole**
b) shaded pole to main pole
c) depends on supply line polarity.

- d) None of the above
34. Which motor is generally used in tape recorders ?
- a) Universal motor
b) Reluctance motor
c) Split phase motor
d) **Hysteresis motor.**
35. In a shaded pole motor, shading coils are used to
- a) reduce windage losses
b) reduce friction losses
c) **produce rotating magnetic field**
d) to protect against sparking.
36. The type of starting relay used on single phase hermetic motor is
- a) hot wire relay
b) timing relay
c) **current coil relay**
d) voltage coil relay
37. Reluctance motors are
- a) doubly excited
b) **singly excited**
c) either doubly excited or singly excited
d) none of the above.
38. Electric motors are generally designed to have maximum efficiency at
- a) full load
b) **near full load**
c) half load
d) near half load.
39. Which of the following is non-reversible motor ?
- a) Universal motor
b) Capacitor start split phase motor
c) **Resistance start split phase motor**
d) Permanent split capacitor motor.
40. Which motor is generally used for electric shavers ?
- a) Shaded pole motor
b) Hysteresis motor
c) Reluctance motor
d) **Universal motor.**
41. The motor useful for signaling and timing device is
- a) **Reluctance motor**
b) Shaded pole motor
c) Hysteresis motor
d) Two value capacitor motor
42. A motor generally used in toys is
- a) Hysteresis motor
b) **Shaded pole motor**
c) Two value capacitor motor
d) Reluctance motor.

6. Protective Devices and Switchgear

Position in Question Paper

Total Marks-12

Q.1. g) 2-Marks.

Q.3. d) 4-Marks.

Q.6. c) 6-Marks.

Descriptive Question

1. List the types of Fuses.
2. Explain pipe earthing with a neat labeled diagram.
3. State the function of the fuse and material used for fuse.
4. Explain the need of earthing in electrical systems.
5. State the types of earthing and any two advantages of earthing.
6. Explain with neat diagram, operation of ELCB and two applications.
7. State function of ELCB.
8. List any two factors that affect earthing.
9. Write any four major points related to rewirable fuse
10. With neat sketch explain principle of operation of ELCB. Write any two applications of it.
11. State any three methods of reducing earthing resistance
12. Write any three major points related to IE rules relevant to earthing.
13. State any four abnormal conditions which can develop in power system and state its effect on power system

MCQ Question

(Total number of Question=Marks*3=12*3=36)

Note: Correct answer is marked with **bold**

1. The main function of a fuse is to
 - a) protect the line
 - b) open the circuit
 - c) protect the appliance
 - d) prevent excessive currents**
2. On which of the following routine tests are conducted?
 - a) Oil circuit breakers
 - b) Air blast circuit breakers
 - c) Minimum oil circuit breakers
 - d) All of the above**
3. SF₆ gas
 - a) is yellow in colour
 - b) is lighter than air
 - c) is nontoxic**
 - d) has pungent smell

4. The arcing contacts in a circuit breaker are made of
- a) **copper tungsten alloy**
 - b) porcelain
 - c) electrolytic copper
 - d) aluminium alloy
5. Which of the following medium is employed for extinction of arc in air circuit breaker?
- a) Water
 - b) Oil
 - c) **Air**
 - d) SF
6. With which of the following, a circuit breaker must be equipped for remote operation?
- (a) Inverse time trip
 - (b) Time-delay trip
 - (c) **Shunt trip**
 - (d) None of the above
7. Fault diverters are basically
- a) fuses
 - b) relays
 - c) **fast switches**
 - d) circuit breakers
8. A thermal protection switch can protect against
- a) short-circuit
 - b) temperature
 - c) **overload**
 - d) over voltage
9. Arc in a circuit behaves as
- a) a capacitive reactance
 - b) an inductive reactance
 - c) a resistance increasing with voltage rise across the arc
 - d) **a resistance decreasing with voltage rise across the arc**
10. Thermal circuit breaker has
- a) **delayed trip action**
 - b) instantaneous trip action
 - c) both of the above
 - d) none of the above
11. Overload relays are of type.
- a) induction
 - b) solid state
 - c) thermal
 - d) **all above**
12. Thermal overload relays are used to protect the motor against overcurrent due to
- a) short-circuits
 - b) **heavy loads**
 - c) grounds
 - d) all of the
13. Magnetic circuit breaker has trip action.



- a) delayed
b) instantaneous
14. D.C. shunt relays are made of
a) few turns of thin wire
b) few turns of thick wire
c) both of the above
d) **none of the**
15. many turns of thick wire The relay operating speed depends upon
a) the spring tension
b) the rate of flux built up
c) armature core air gap
d) **all of the above**
16. In order that current should flow without causing excessive heating or voltage drop, the relay contacts should
a) have low contact resistance
b) be clean and smooth
c) be of sufficient size and proper shape
d) **have all above properties**
17. Circuit breakers usually operate under
a) transient state of short-circuit current
b) sub-transient state of short-circuit current
c) **steady state of short-circuit current**
d) after D.C. component has ceased
18. Circuit breakers are essentially
a) current carrying contacts called electrodes
b) **arc extinguishers**
c) circuits to break the system
d) transformers to isolate the two systems
19. The current zero interruption, in oil and air blast circuit breakers, is achieved by
a) lengthening of the gap
b) cooling and blast effect
c) **both (a) and (b)**
d) demonizing the oil with forced air
20. To prevent overload and overheating of wires
a) fuses are used
b) circuit breakers are used
c) **fuses and circuit breakers are used**
d) fuses and resistor are used
21. The magnetic field of the coil and the permanent magnet
a) attract each other
b) **repel each other**
c) combine with each other
d) stay with each other
22. ELCB is an abbreviation of
a) electrolytic circuit breaker
b) earth locking circuit breaker
c) **earth leakage circuit breaker**
d) electric leakage circuit breaker
23. Electricity is required to
a) **light up homes**
b) clean your car
c) flush the toilet
d) change weather



24. A block of impure copper is used as
- a) cathode
 - b) **anode**
 - c) posit rode
 - d) nematode
25. Miniature circuit breaker is a small
- a) **fuse**
 - b) magnetic switch
 - c) electromagnetic switch
 - d) two way switch
26. Which of the following circuit breaker can be installed on 400 kV line
- a) **Tank type oil circuit breaker**
 - b) Miniature circuit breaker
 - c) Vacuum circuit breaker
 - d) Air blast circuit breaker.
27. Out of the following circuit breakers, which one has the lowest voltage range ?
- a) **Air-break circuit breaker**
 - b) Tank type oil circuit breaker
 - c) Air-blast circuit breaker
 - d) SF₆ circuit breaker.
28. In a vacuum circuit breaker, the vacuum is of the order of
- a) 10mm Hg
 - b) 10⁻²mmHg
 - c) 10⁻⁶ mmHg
 - d) **10⁻⁹mmHg.**
29. In modem EHV circuit breakers, the operating time between instant of receiving trip signal and final contact separation is, of the order of
- a) 0.001 sec
 - b) 0.015 sec
 - c) 0.003 sec
 - d) **0.03 sec.**
30. In a HRC fuse the time between cut-off and final current zero, is known as



- a) total operating time
b) arcing time
- c) **pre-arcing time**
d) any of the above
- 31 . Low voltage circuit breakers have rated voltage of less than
a) 220 V
b) 400V
c) **1000 V**
d) 10,000 V.
- 32 .The fault clearing time of a circuit breaker is usually
a) few minutes
b) few seconds
c) one second
d) **few cycles of supply voltage**
- 33 .The medium employed for extinction of arc in air circuit breaker is
a) SF₆
b) Oil
c) **Air**
d) Water.
- 34 .Which of the following circuit breakers is preferred for EHT application
a) Air blast circuit breakers
b) Minimum oil circuit breakers
c) Bulk oil circuit breakers
d) **SF₆ oil circuit breakers.**
- 35 .For high voltage, ac circuit breakers, the rated short circuit current is passed for
a) 0.01 sec
b) 0.1 sec
c) **3 seconds**
d) 20 seconds
- 36 .A circuit breaker is
a) power factor correcting device
b) a device to neutralize the effect of transients
c) a waveform correcting device
d) **a current interrupting device.**